
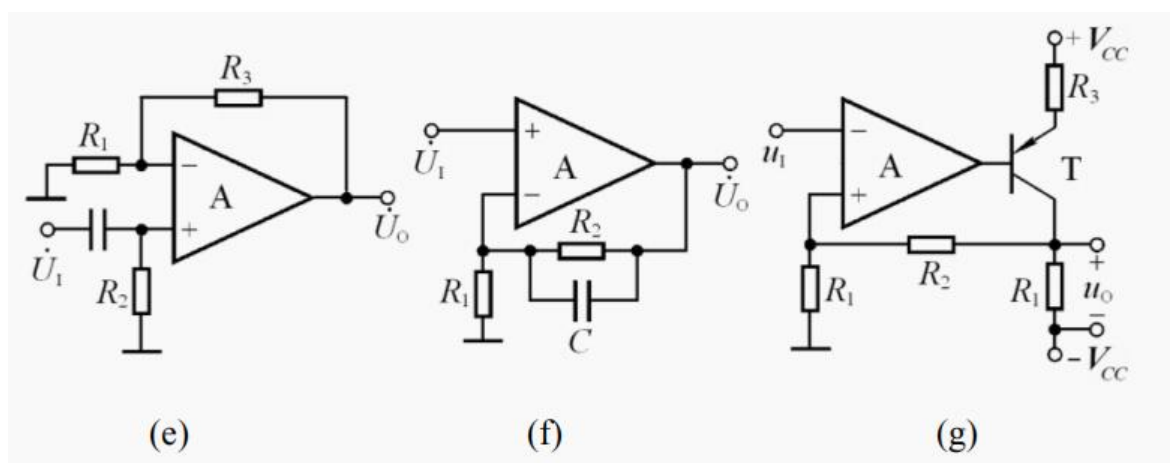
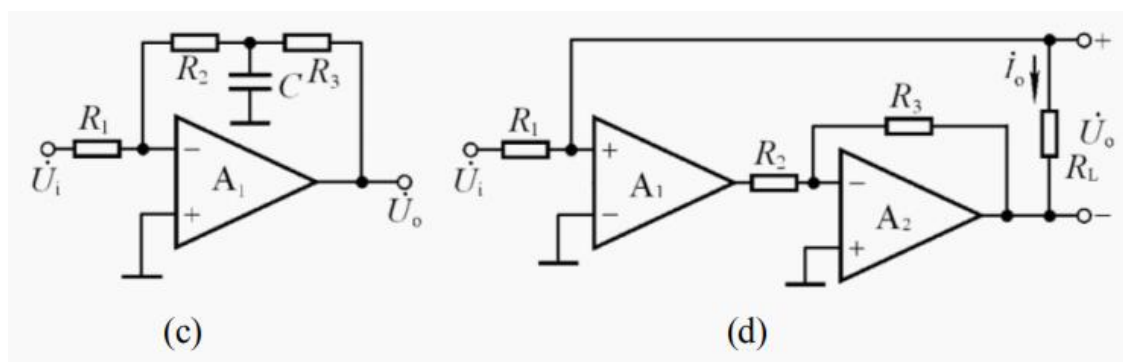



Homework 6

◇ 反馈电路及判断: 教材 P318--6.4/ 6.5/ 6.6/ 6.7 (共 4 题)

6.4 判断图 P6.4 所示各电路中: 是否引入了反馈? 是直流反馈还是交流反馈? 是正反馈还是负反馈? 设图中所有电容对交流信号均可视为短路。

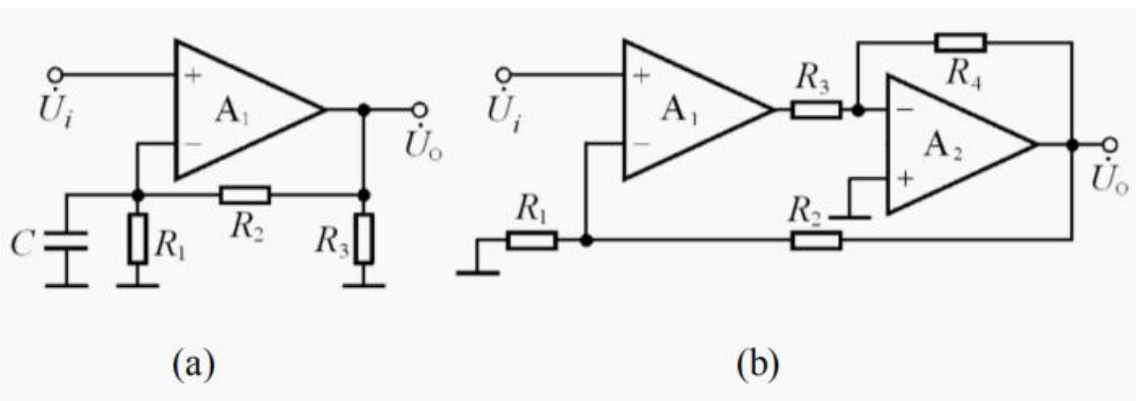
6.4 Judge whether feedback is introduced into each amplifier circuit as shown in figure p6.4? Is it DC feedback or AC feedback? Is it positive feedback or negative feedback? It is assumed that all capacitor to AC signals can be regarded as short circuit.




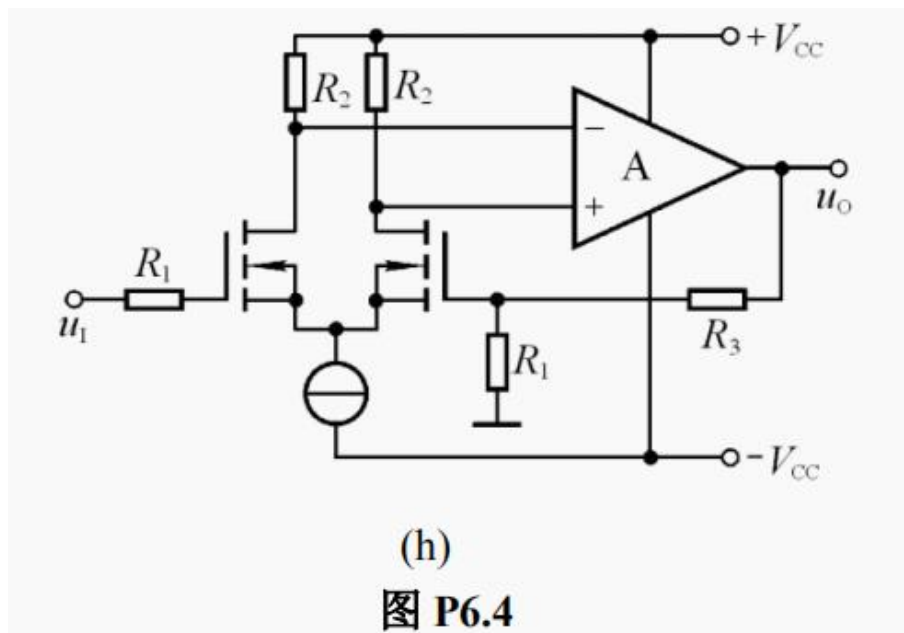

6.5 电路如图 P6.5 所示，要求同题 6.4。

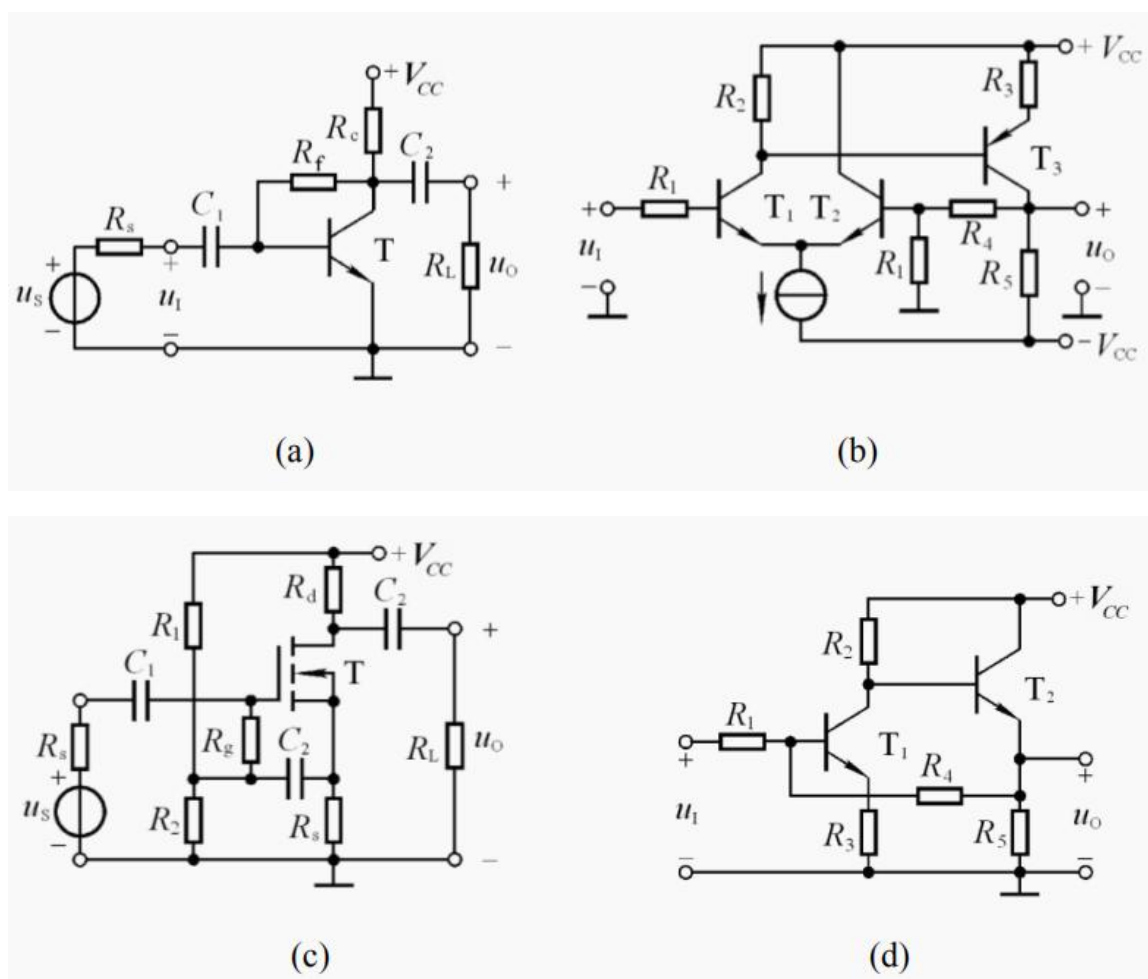6.5 Judge whether feedback is introduced into each amplifier circuit as shown in figure p6.5? Is it DC feedback or AC feedback? Is it positive feedback or negative feedback? It is assumed that all capacitor to AC signals can be regarded as short circuit.



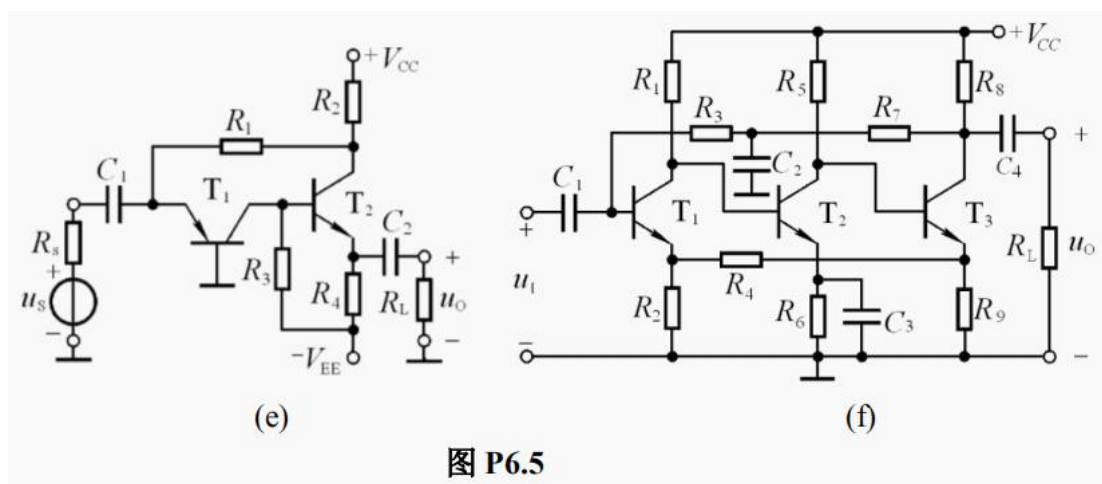

6.6 分别判断图 6.4 (d)~(h)所示各电路中引入了哪种组态的交流负反馈。

6.6 Determine the type of AC negative feedback in each amplifier circuit as shown in Fig. P6.4 (d) - (h).

6.7 分别判断图 P6.5 (a) 、(b) 、(e) 、(f) 所示各电路中引入了哪种组态的交流负反馈。

6.7 Determine the type of AC negative feedback in each amplifier circuit as shown in Fig. P 6.5 (a), (b), (e) and (f).