


Homework 9

◇ Sine-wave oscillator: P471: 8.6/8.7/8.8/8.10/8.11/8.12

8.6 电路如图 P8.6 所示, 试求解: (1) R_W 的下限值; (2) 振荡频率的调节范围。

8.6 An oscillating circuit is shown in figure p8.6, R_2 can be adjusted from 0 to $100\text{k}\Omega$, ask:

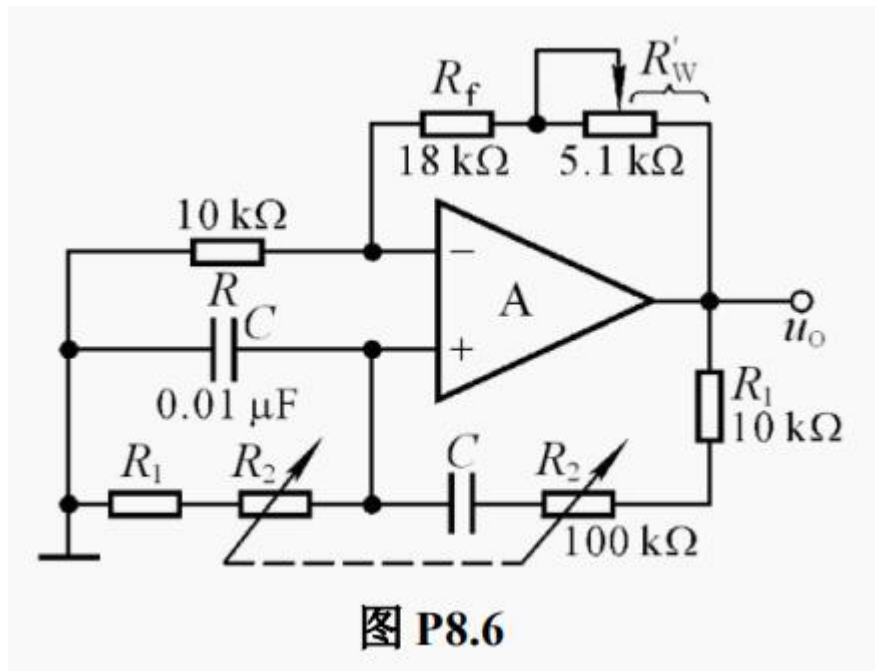- (1) The lower limit value of R_W to oscillate;
- (2) The range of oscillation frequency.




8.7 电路如图 P8.7 所示, 稳压管起稳幅作用, 其稳压值为 $\pm 6V$ 。试估算:

- (1) 输出电压不失真情况下的最大有效值;
- (2) 振荡频率。

8.7 An oscillating circuit is shown in figure p8.7. The working voltage of voltage regulator D_Z is $\pm 6V$. Please estimate:

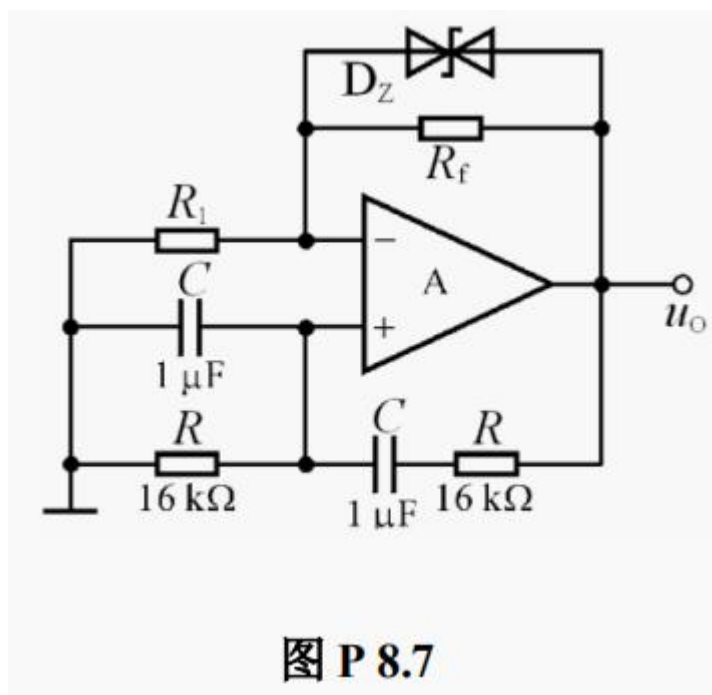- (1) The maximum effective value of the output voltage without distortion;
- (2) The oscillation frequency.




8.8 电路如图 P8.8 所示。


- (1) 为使电路产生正弦波振荡，标出集成运放的“+”和“-”；并说明电路是哪种正弦波振荡电路。
- (2) 若 R_1 短路，则电路将产生什么现象？
- (3) 若 R_1 断路，则电路将产生什么现象？
- (4) 若 R_f 短路，则电路将产生什么现象？
- (5) 若 R_f 断路，则电路将产生什么现象？

8.8 The circuit is shown in figure p8.8.

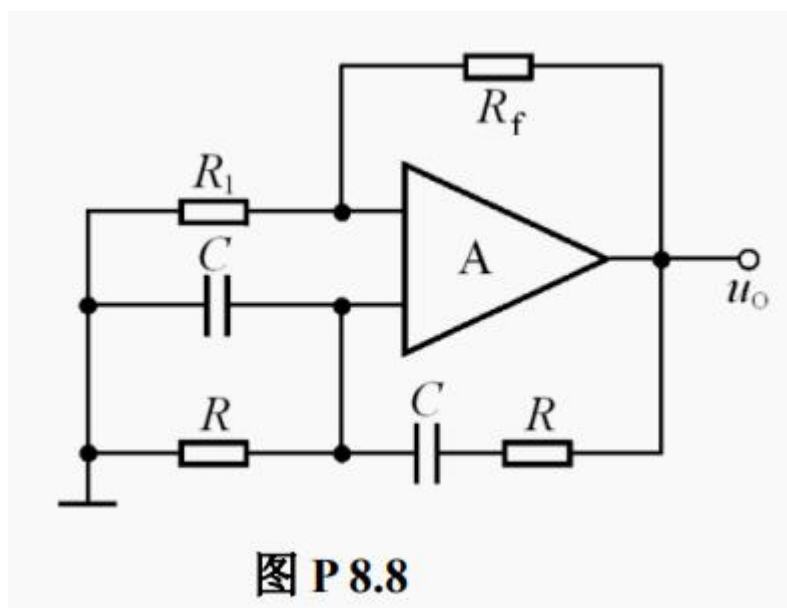- (1) In order to generate the sine-wave oscillation, mark the "+" "-" of the integrated operational amplifier and judge the type of the oscillation circuit?
- (2) If R_1 is short circuited, what will happen in the circuit?
- (3) If R_1 is broken, what will happen in the circuit?
- (4) If R_f is short circuited, what will happen in the circuit?
- (5) If R_f is broken, what will happen in the circuit?



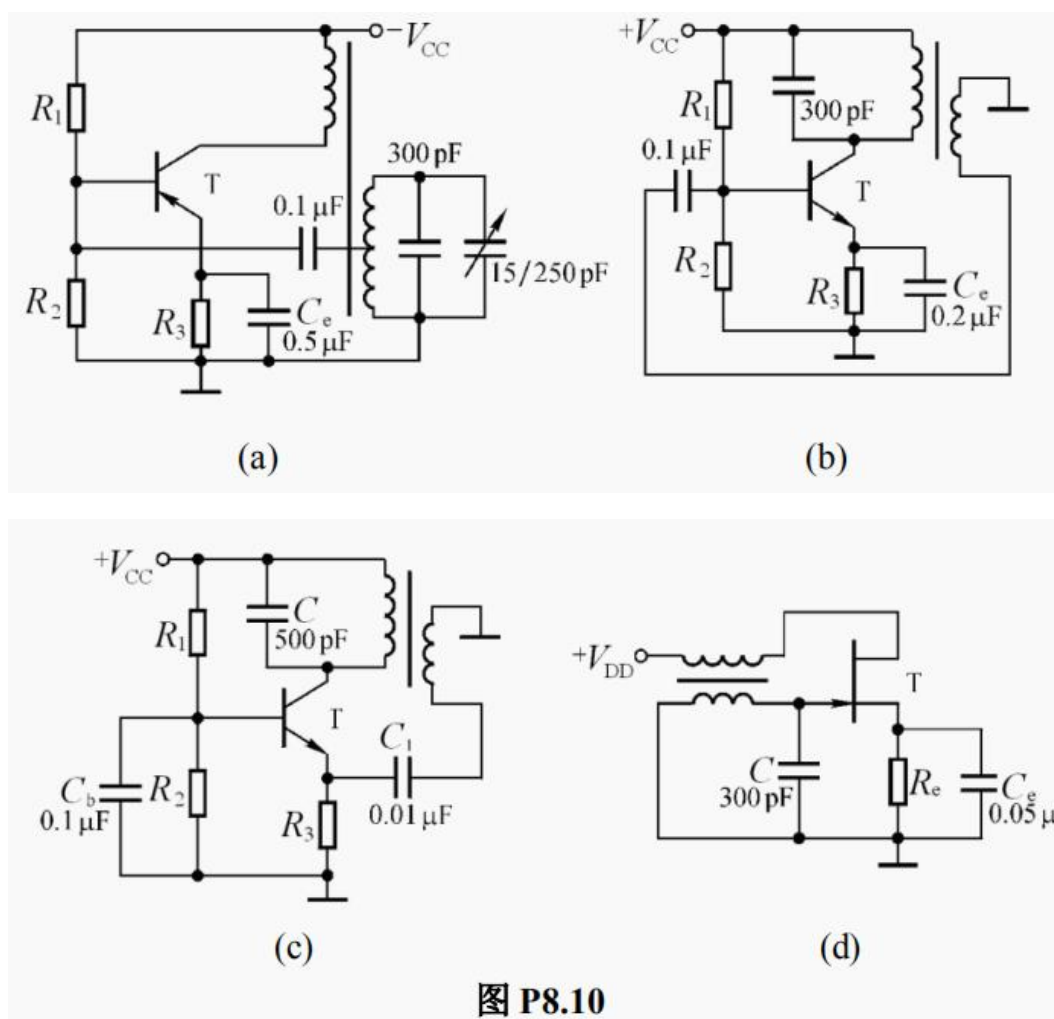8.10 分别标出图 P8.10 所示各电路中变压器的同名端，使之满足正弦波振荡的相位条件。
 8.10 Please mark the dotted terminal of the mutual inductors in each circuit to generate the sine-wave oscillation as shown in figure p8.10.



8.11 分别判断图 P8.11 所示各电路是否可能产生正弦波振荡。

8.11 Judge whether the circuits shown in figure p8.11 are able to generate sine-wave oscillation.

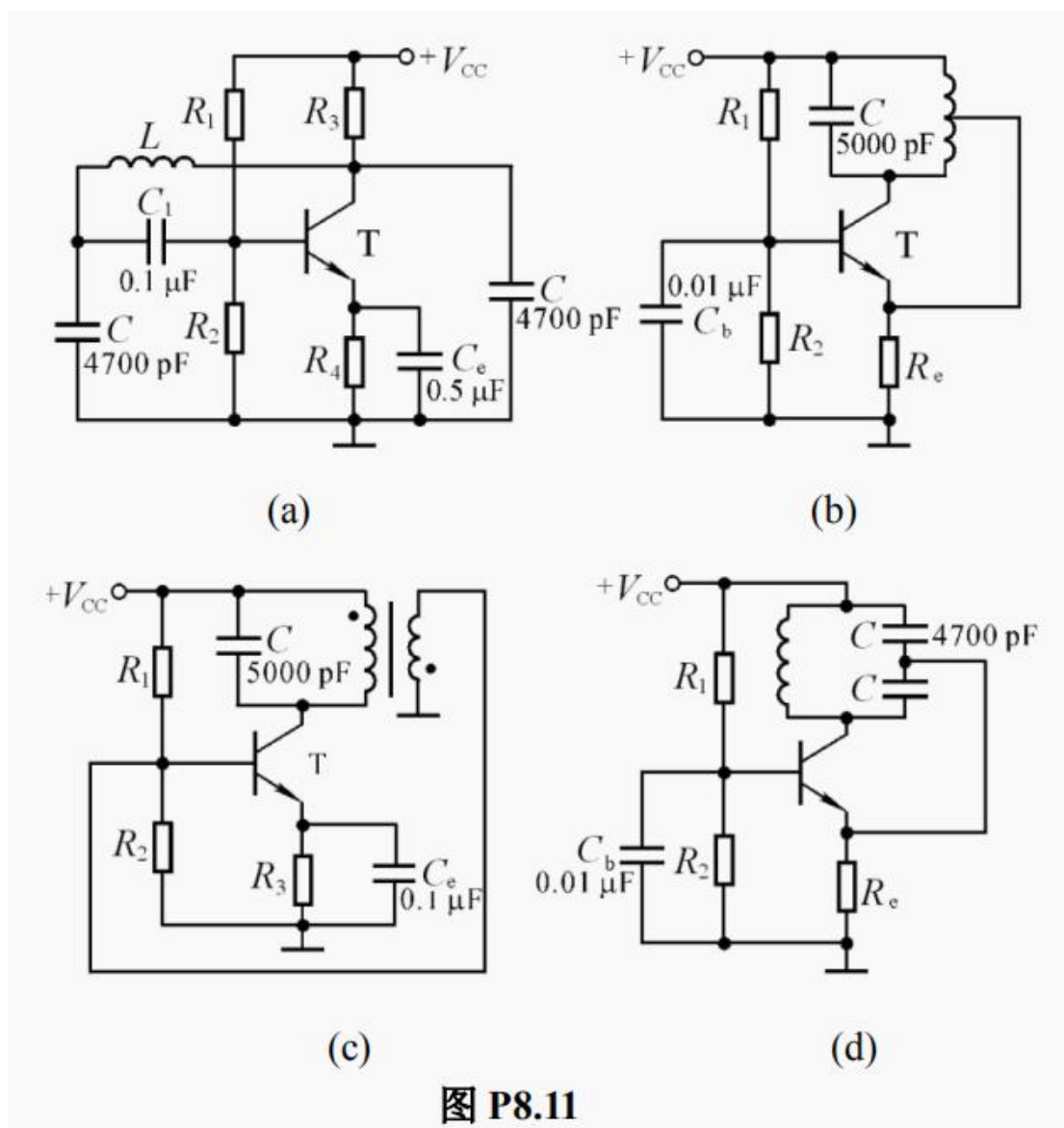


图 P8.11

8.12 改正图 P8.11(b)、(c)所示两电路中的错误，使之有可能产生正弦波振荡。

8.12 Correct the errors in the circuits shown in figure p8.11 (b) and figure p8.11 (c) to make it able to generate sine-wave oscillation.