


2.3 Stabilizing the quiescent working point Q

稳定放大电路工作点Q

Many factors can affect the quiescent working point Q:

1. Aging 老化
2. Fluctuation of supply voltage V_{CC}
3. Temperature effect

Temperature effect

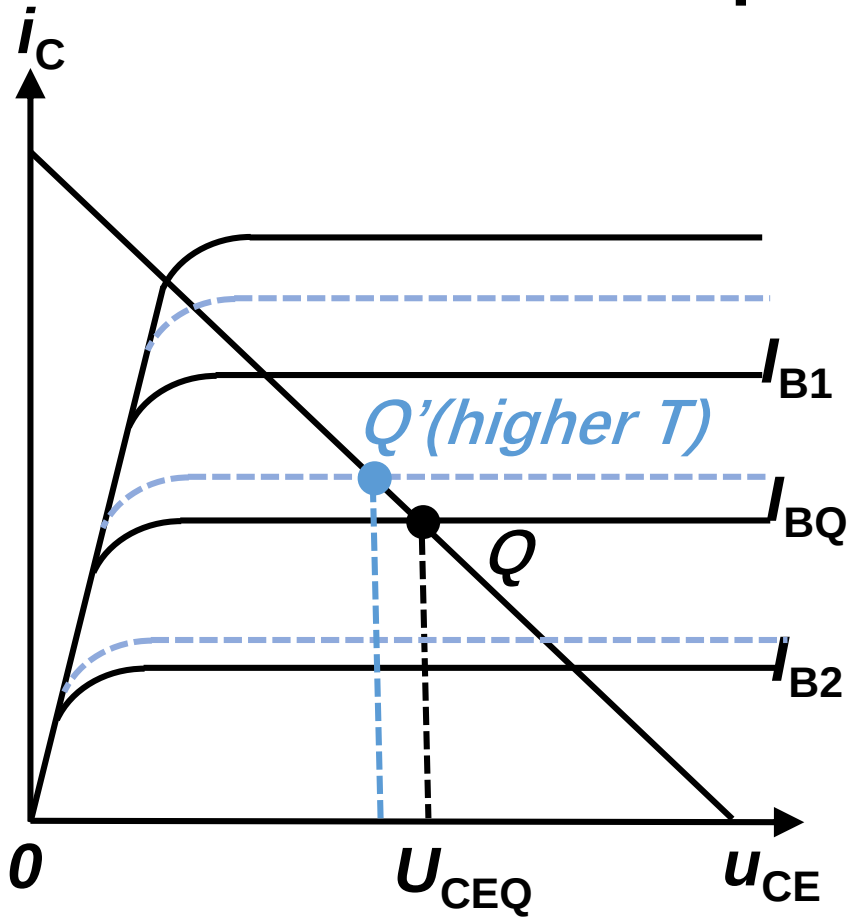

Temperature $\uparrow$:

For the same I_{BQ} value

$$I_{CQ} \uparrow \quad U_{CEQ} \downarrow \quad \beta \uparrow$$




Amplifier circuit is unstable

Quiescent working points change!


AC voltage gain changes!



2.3.1 Negative feedback to stabilize the quiescent working point Q

Direct coupling


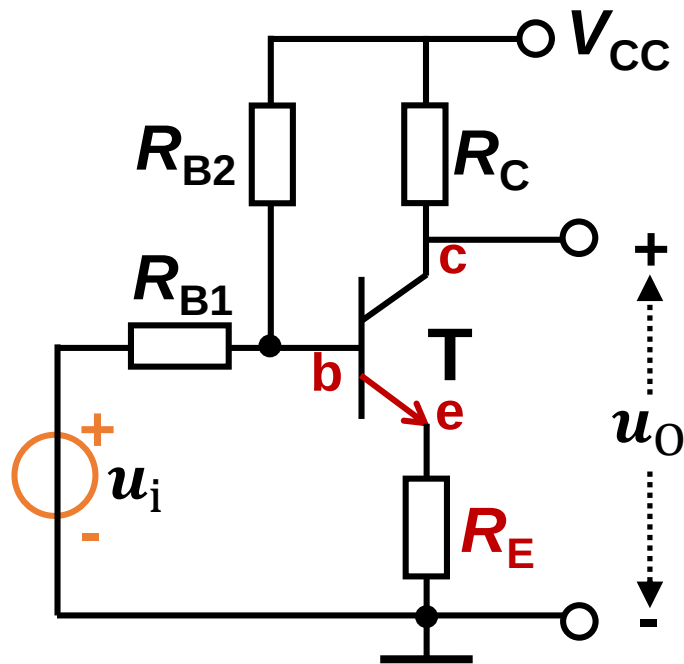


Resistance-capacitance coupling

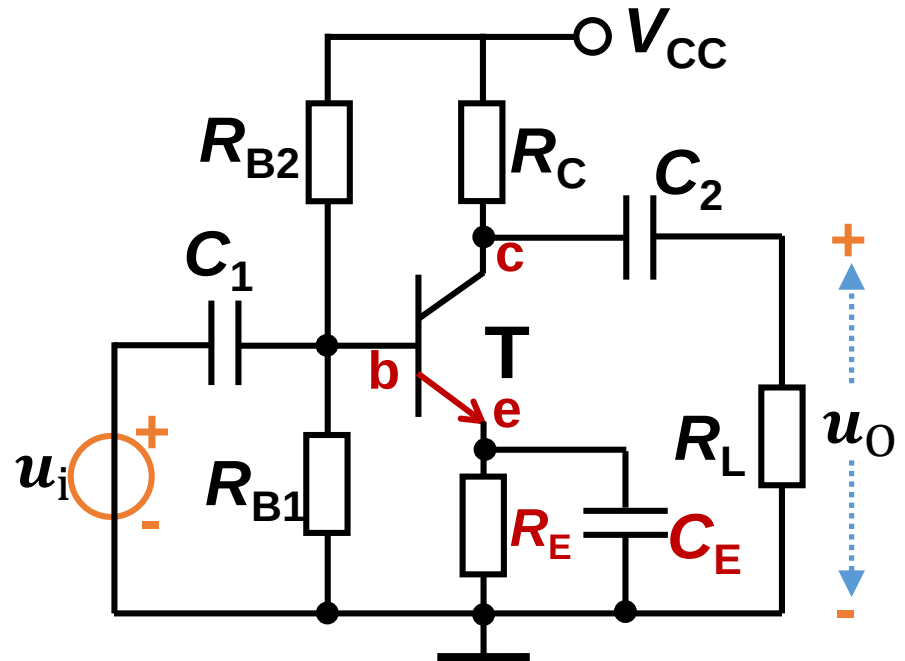

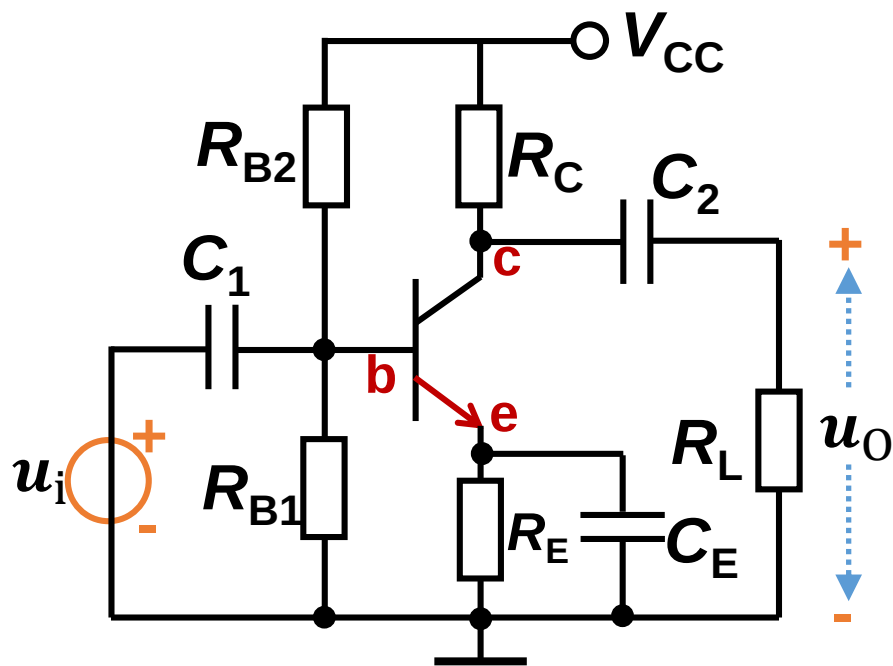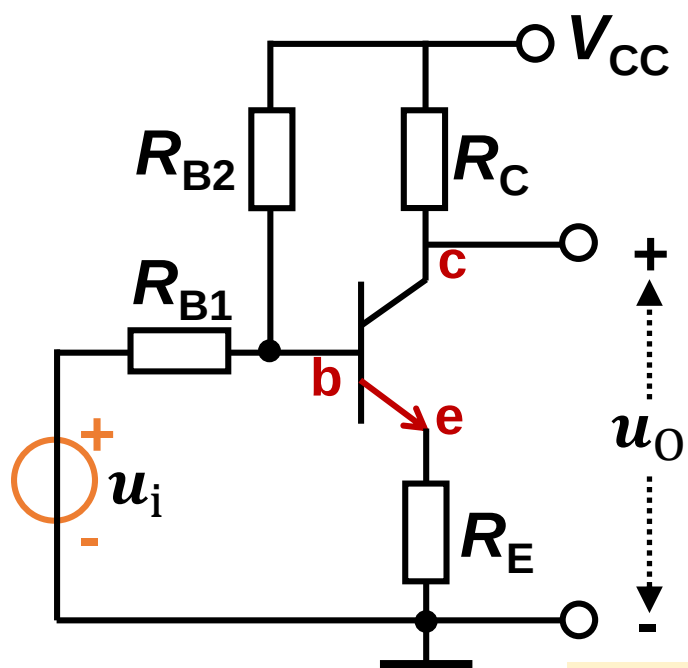

DC circuit

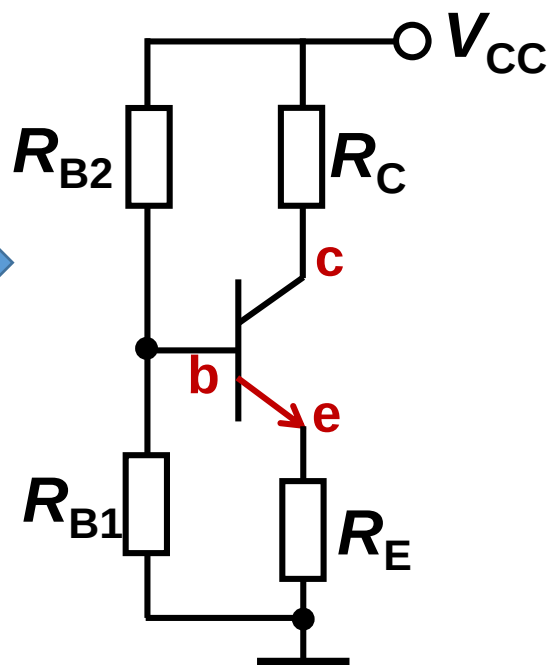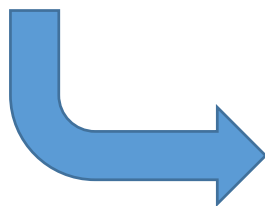

Working principle


$$I_2 = I_1 + I_{BQ}$$

Because I_{BQ} is very small


$$I_2 \text{ and } I_1 \gg I_{BQ}$$

$$I_2 \approx I_1 \text{ (Approximation)}$$
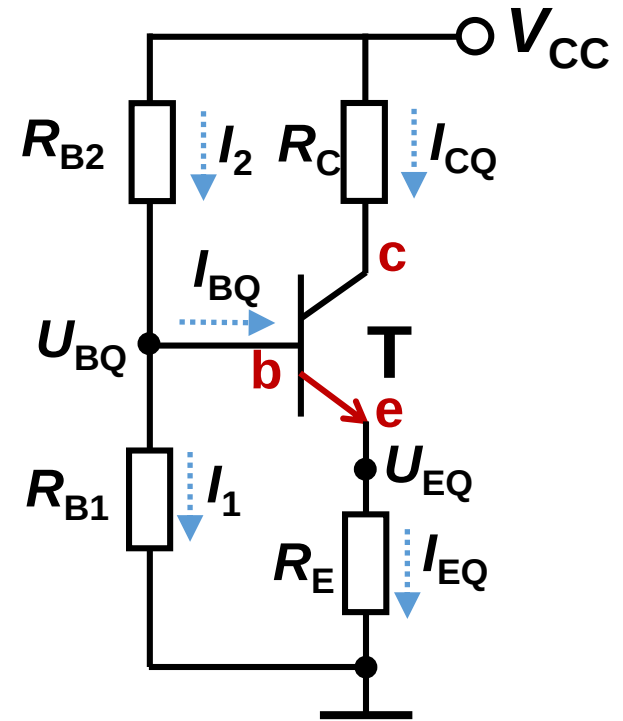
$$U_{BQ} \approx \frac{R_{B1}}{R_{B1} + R_{B2}} \cdot V_{CC}$$



Then U_{BQ} is unrelated to temperature

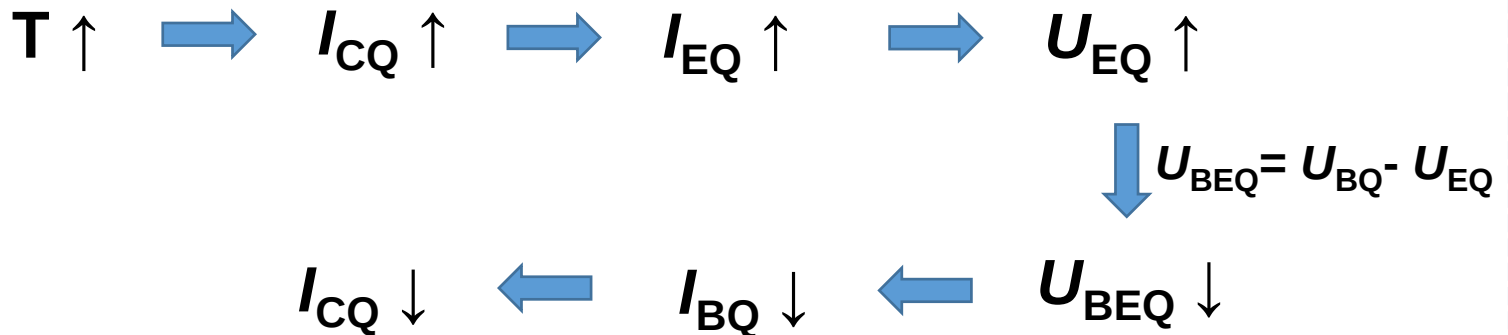



Feedback 反馈

R_E : Transport output signal (I_C) back to the input circuit, and in turn affect the input signal (U_{BEQ})

Negative Feedback 负反馈

The feedback make the variation of output signal smaller


DC Negative Feedback 直流负反馈

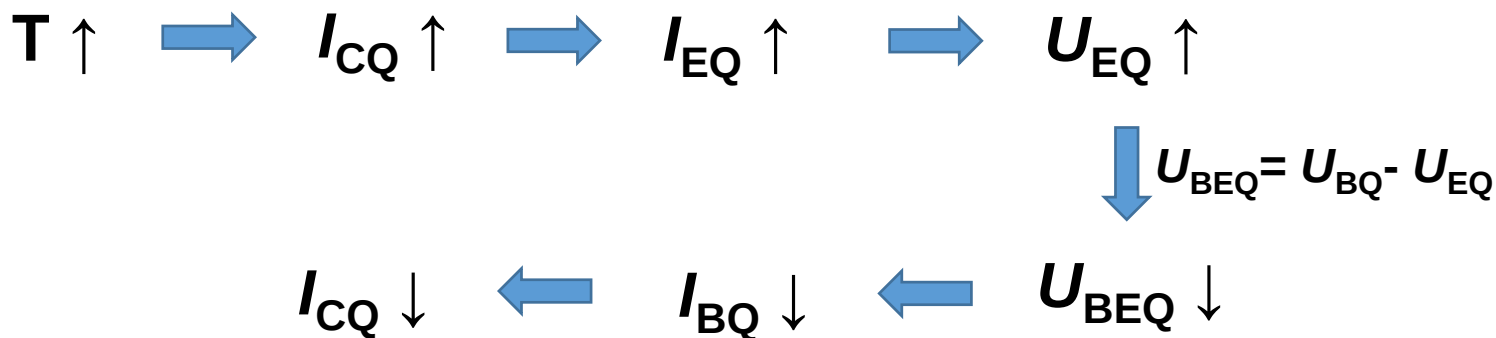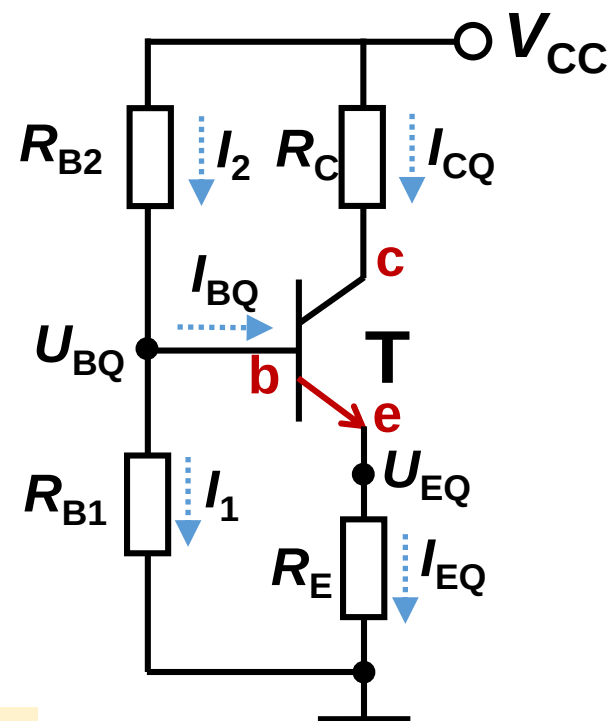

[Q1] As shown in the figure, $R_{B2}=39\text{k}\Omega$, $R_{B1}=10\text{k}\Omega$, $R_C=2.7\text{k}\Omega$, $R_E=1\text{k}\Omega$, $R_L=5.1\text{k}\Omega$ and $V_{CC}=15\text{V}$, transistor has $\beta=100$, $r_{bb'}=300\Omega$ and $U_{BEQ}=0.7\text{V}$, assume capacitors C_1 and C_2 have no resistance to AC signals, ask:

(1) Parameters of quiescent working point Q;

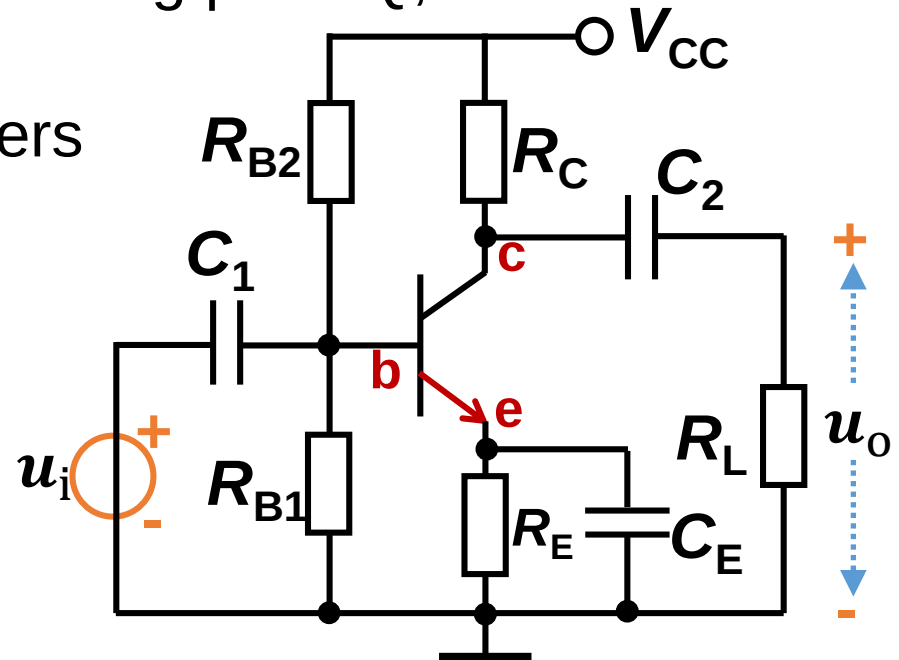(2) Dynamic working parameters A_u , R_i , R_o .



(1) Parameters of static working point Q

1st approach: estimation method

$$I_2, I_1 \gg I_{BQ} \rightarrow I_2 \approx I_1$$


$$U_{BQ} \approx \frac{R_{B1}}{R_{B1} + R_{B2}} \cdot V_{CC} = 3.06V$$

$$I_{EQ} = \frac{U_{EQ}}{R_E} = \frac{U_{BQ} - U_{BEQ}}{R_E} = 2.36mA$$


$$I_{BQ} = \frac{I_{EQ}}{\beta + 1} = 0.02mA$$


$$I_{CQ} = \beta \frac{I_{EQ}}{\beta + 1} = 2.34mA$$
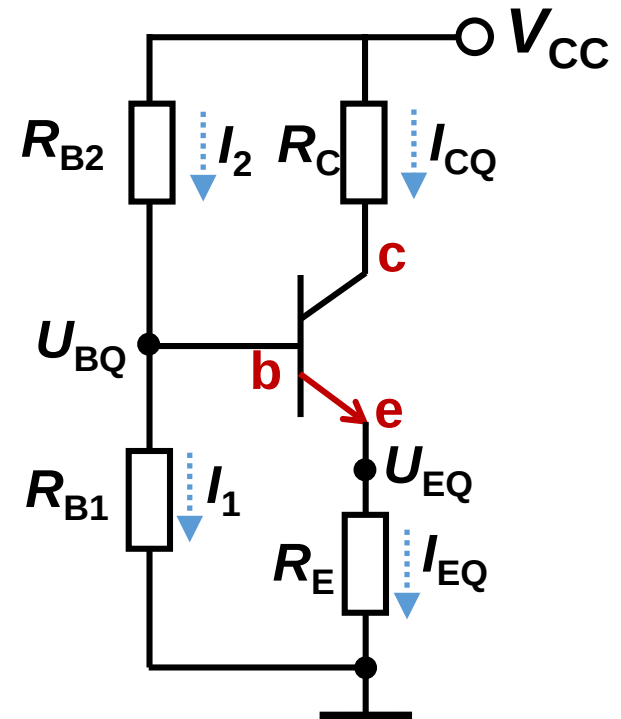
$$U_{CEQ} = V_{CC} - I_{CQ}R_C - I_{EQ}R_E = 6.32V$$




2nd approach: Thevenin's theorem 戴维南定理

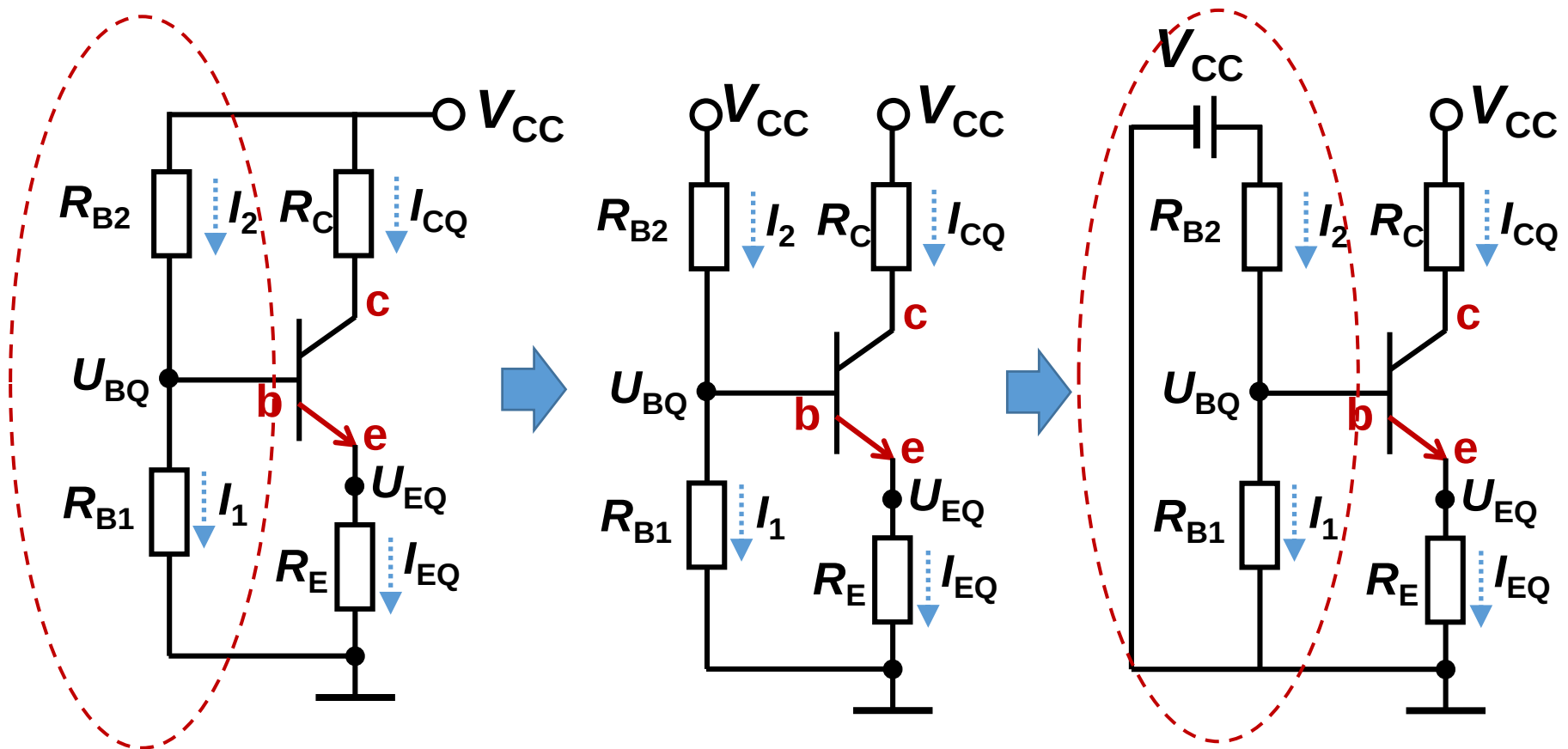

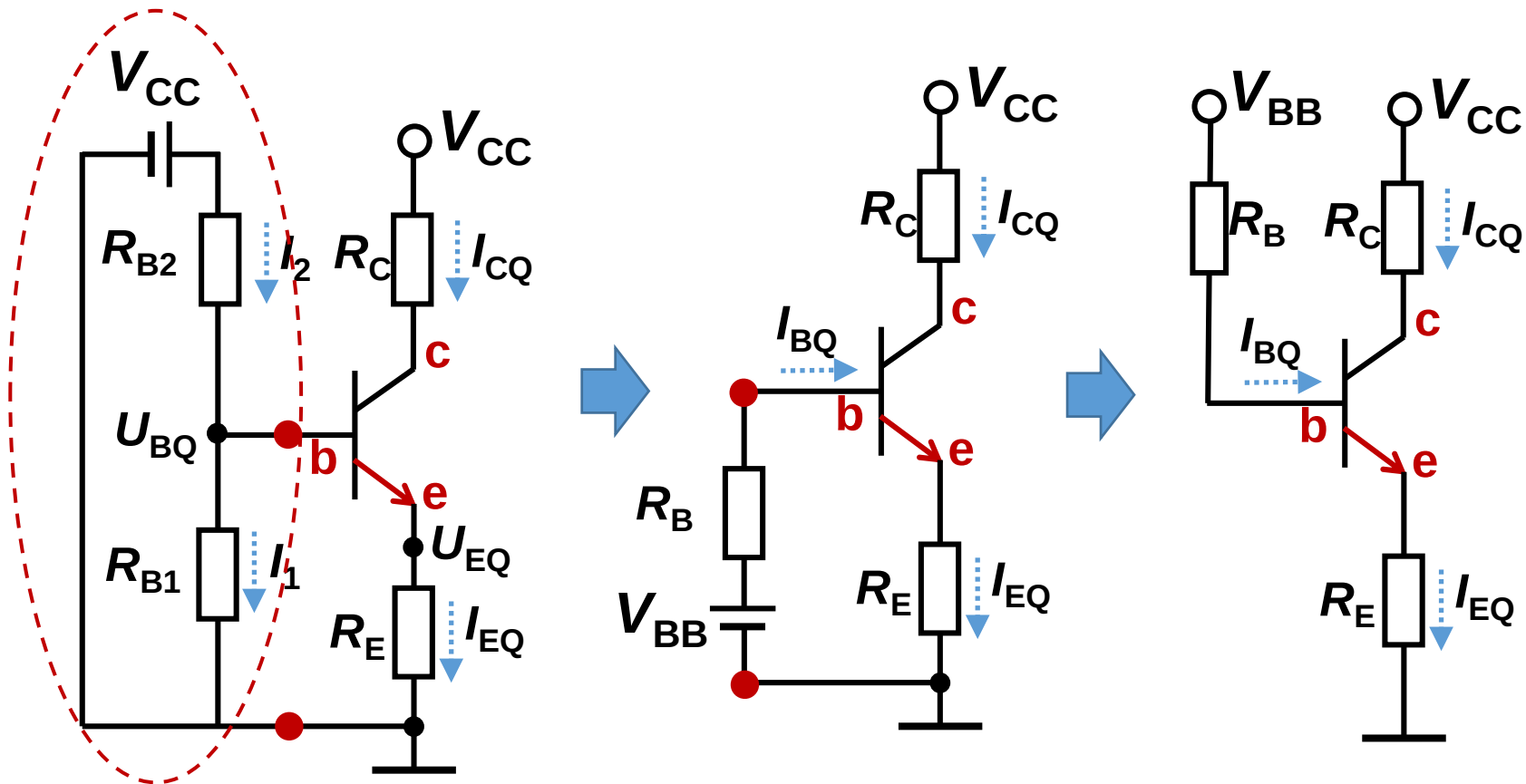

$$V_{BB} = \frac{R_{B1}}{R_{B1} + R_{B2}} \cdot V_{CC} = 3.06V \quad R_B = R_{B1} || R_{B2} = 7.96k\Omega$$

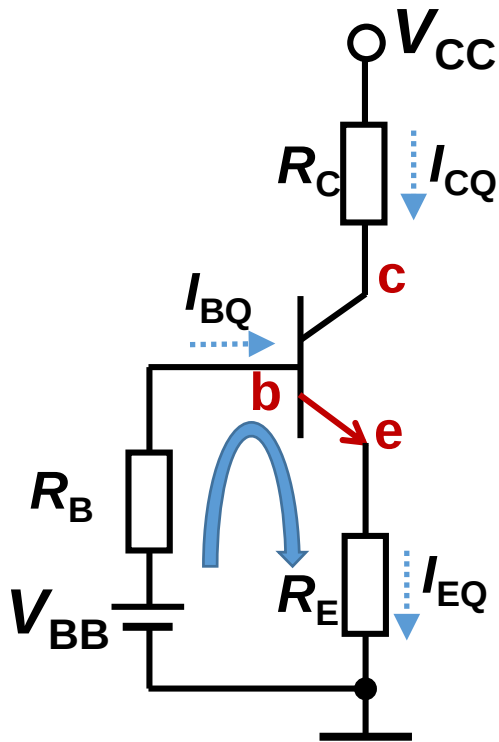

$$V_{BB} = \frac{R_{B1}}{R_{B1} + R_{B2}} \cdot V_{CC} = 3.06V$$


$$R_B = R_{B1} || R_{B2} = 7.96k\Omega$$

$$\begin{cases} V_{BB} - I_{BQ}R_B - U_{BEQ} - I_{EQ}R_E = 0 \\ I_{EQ} = (1 + \beta)I_{BQ} \end{cases}$$



$$I_{BQ} = \frac{V_{BB} - U_{BEQ}}{R_B + (1 + \beta)R_E}$$

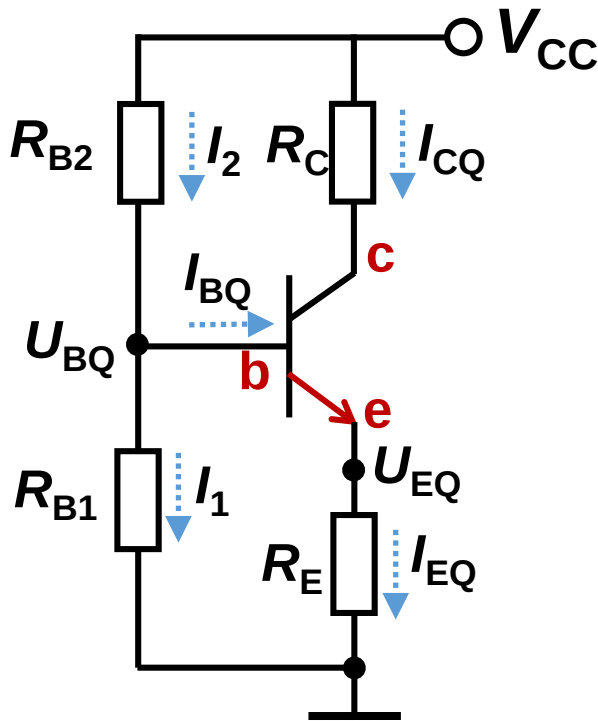The 3rd approach: A violent approach 暴力求解法





$$\begin{cases} V_{CC} - I_2 R_{B2} - I_1 R_{B1} = 0 \\ U_{BEQ} + I_{EQ} R_E - I_1 R_{B1} = 0 \\ I_2 = I_1 + I_{BQ} \\ I_{EQ} = (1 + \beta) I_{BQ} \end{cases}$$




$$I_{BQ} = \frac{\frac{R_{B1}}{R_{B1} + R_{B2}} \cdot V_{CC} - U_{BEQ}}{R_{B1} || R_{B2} + (1 + \beta) R_E}$$



(2) A_u , R_i , R_o

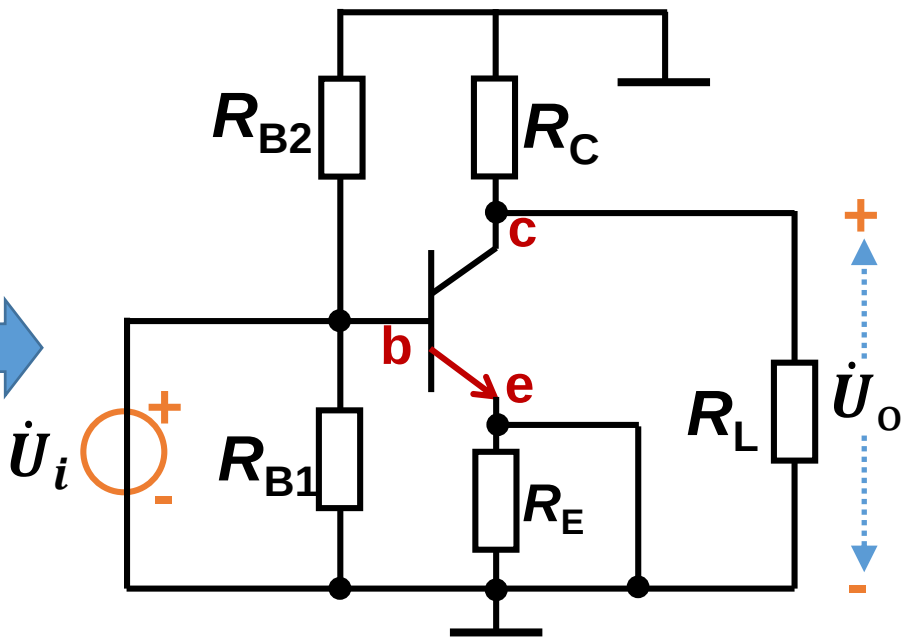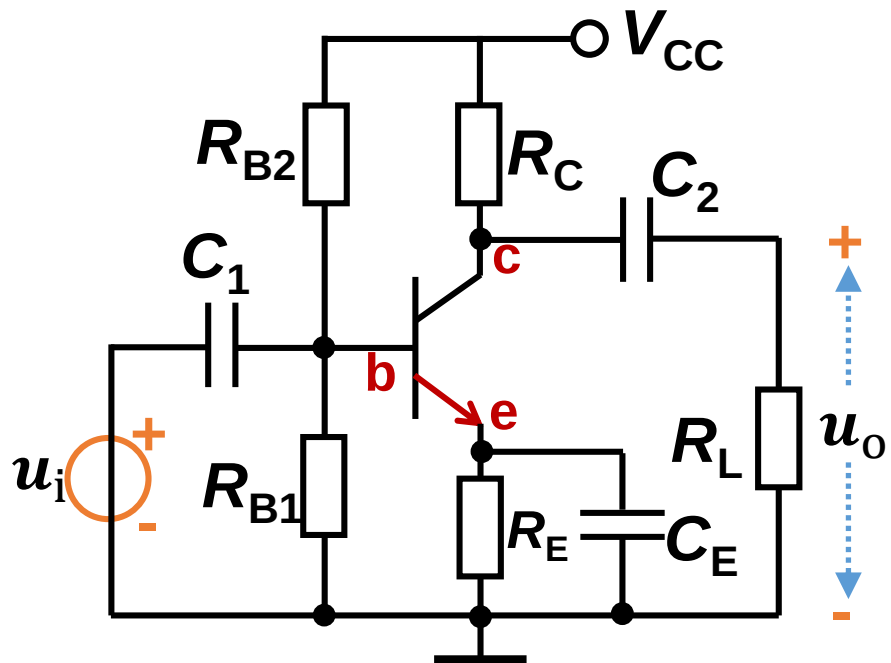

1st step: get AC circuit.

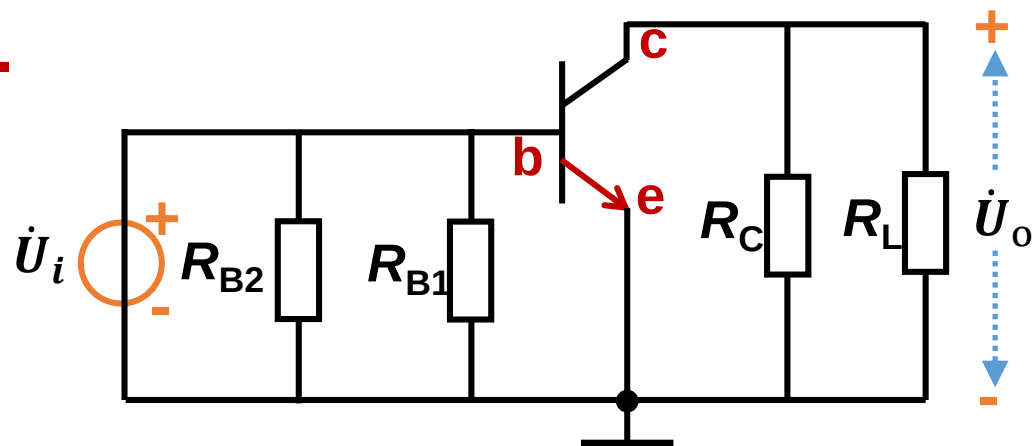


2nd step: get h-model.

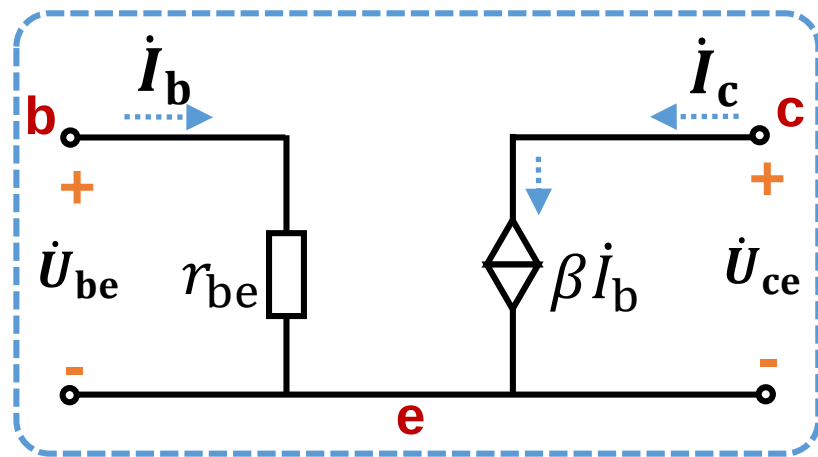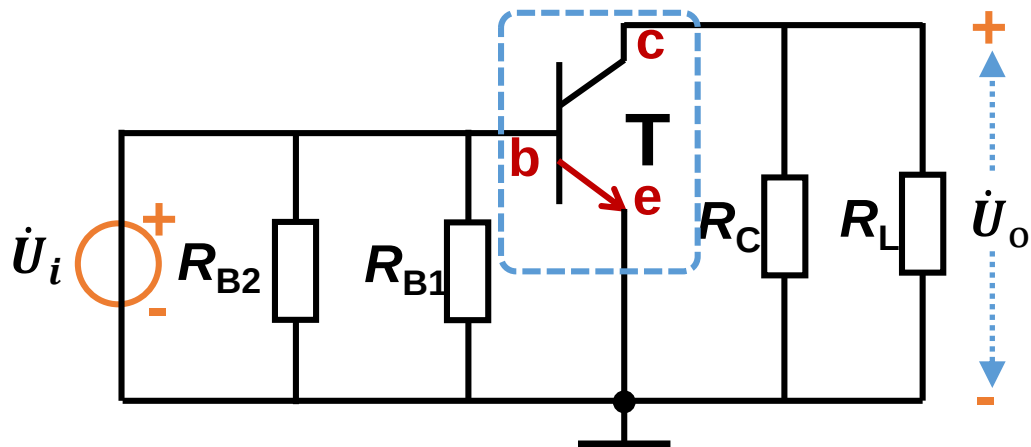


$$R_B = R_{B1} || R_{B2} = 7.96 \text{ k}\Omega$$

$$r_{be} = r_{bb'} + \beta \frac{U_T}{|I_{CQ}|}$$

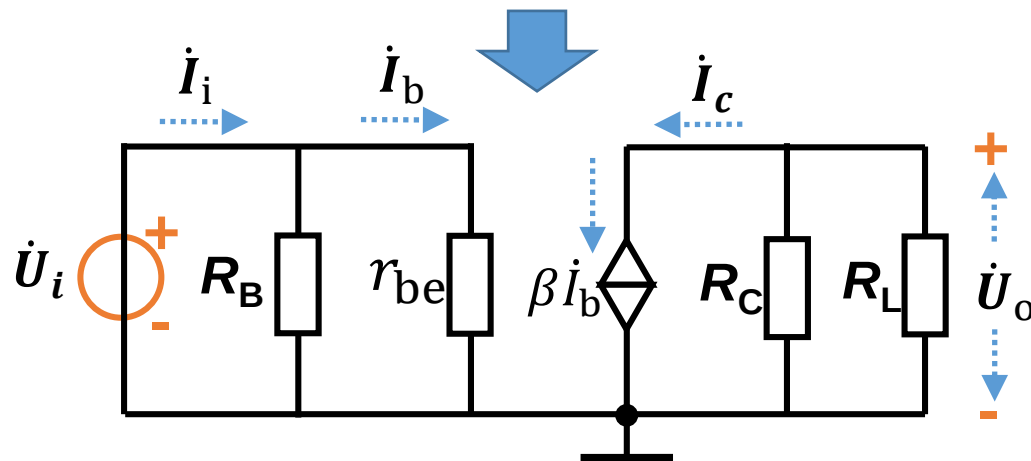
$$= 300 + 100 \frac{0.026}{0.00234} \approx 1.4 \text{ k}\Omega$$



Voltage gain:
$$\dot{A}_u = -\frac{\beta R_L'}{r_{be}} = -\frac{\beta (R_L || R_C)}{r_{be}} \approx -126$$

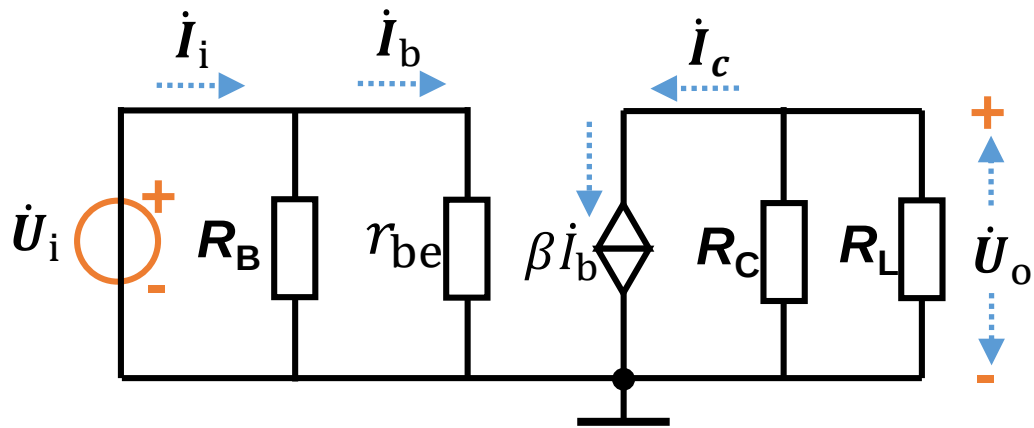

Input resistance: $R_i = R_B || r_{be} = 1.2 \text{ k}\Omega$

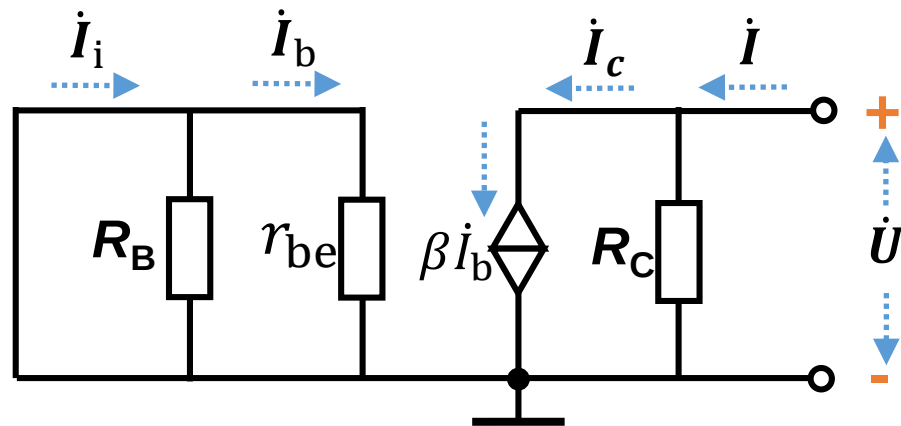


Output resistance: $R_o = R_C = 2.7 \text{ k}\Omega$

[Q2] Same parameters as Q1: $R_{B2}=39\text{k}\Omega$, $R_{B1}=10\text{k}\Omega$, $R_C=2.7\text{k}\Omega$, $R_E=1\text{k}\Omega$, $R_L=5.1\text{k}\Omega$ and $V_{CC}=15\text{V}$, transistor has $\beta=100$, $r_{bb'}=300\Omega$ and $U_{BEQ}=0.7\text{V}$, assume capacitors C_1 and C_2 have no resistance to AC signals, ask :


(1) Parameters of quiescent working point Q;



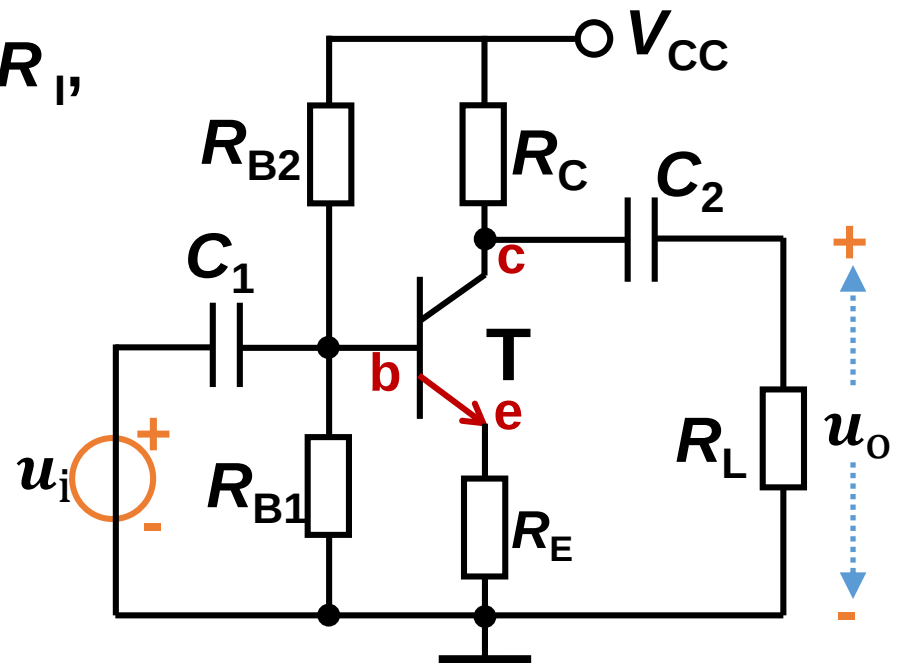
(2) Dynamic parameters A_u , R_i , R_o .

Ans: (1) The DC circuit in Question 2 is the same as Question 1. So the quiescent working point is the same.



(2) Answer:

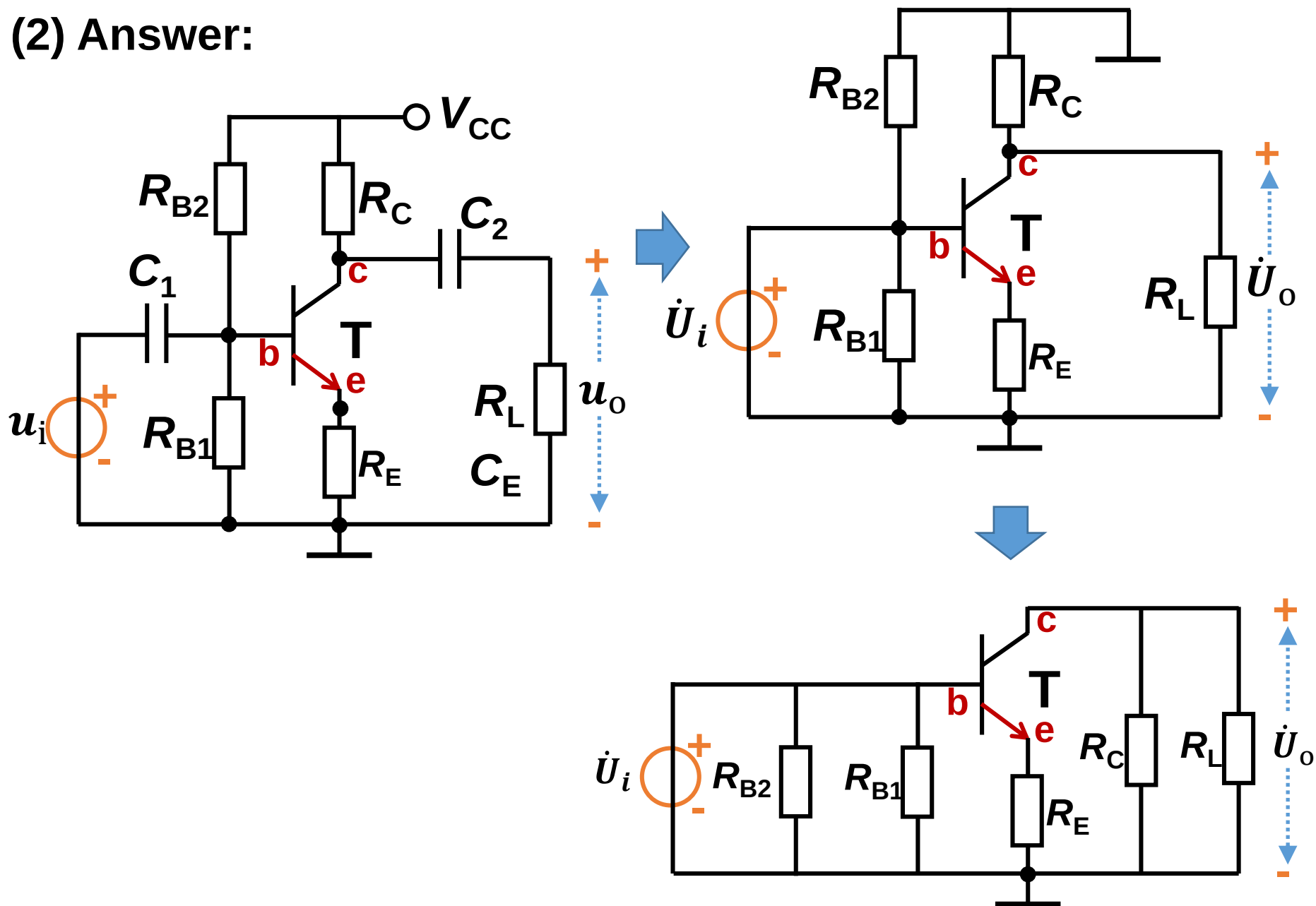


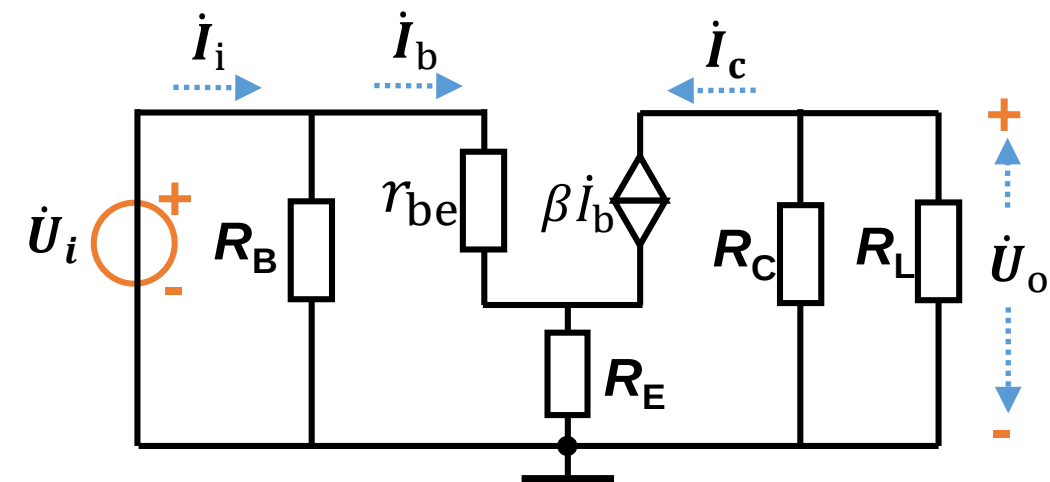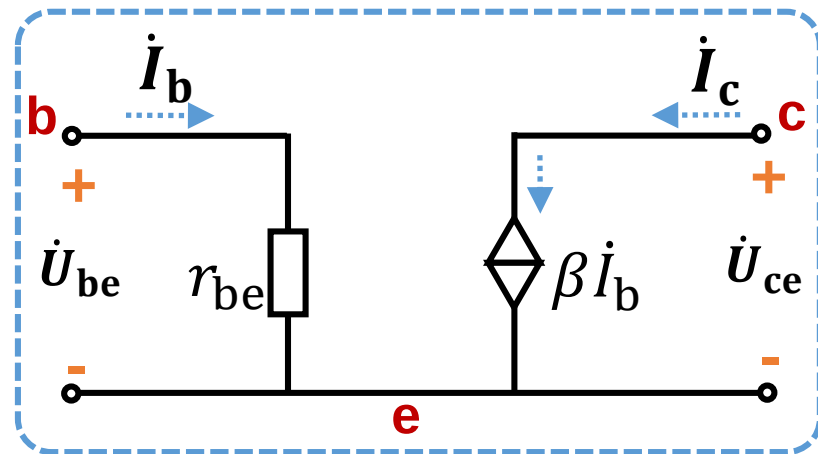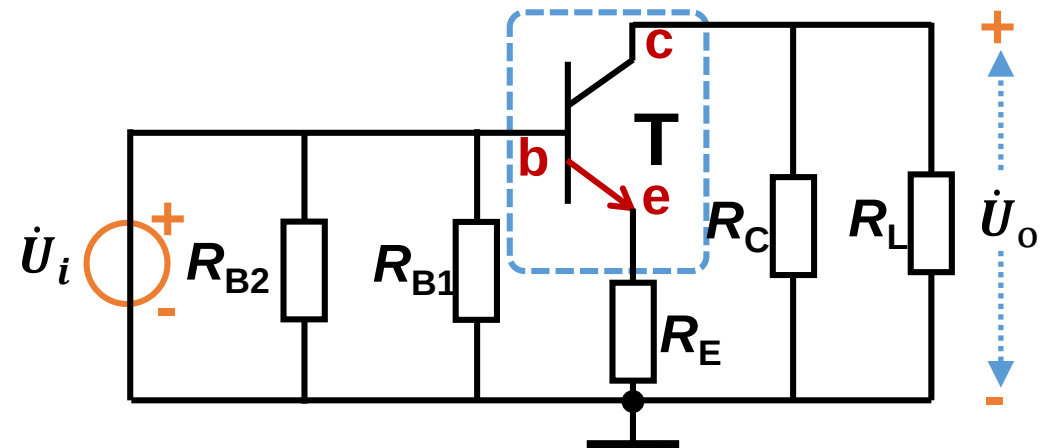

$$R_B = R_{B1} || R_{B2} = 7.96 \text{ k}\Omega$$

$$r_{be} = r_{bb'} + \beta \frac{U_T}{|I_{CQ}|}$$
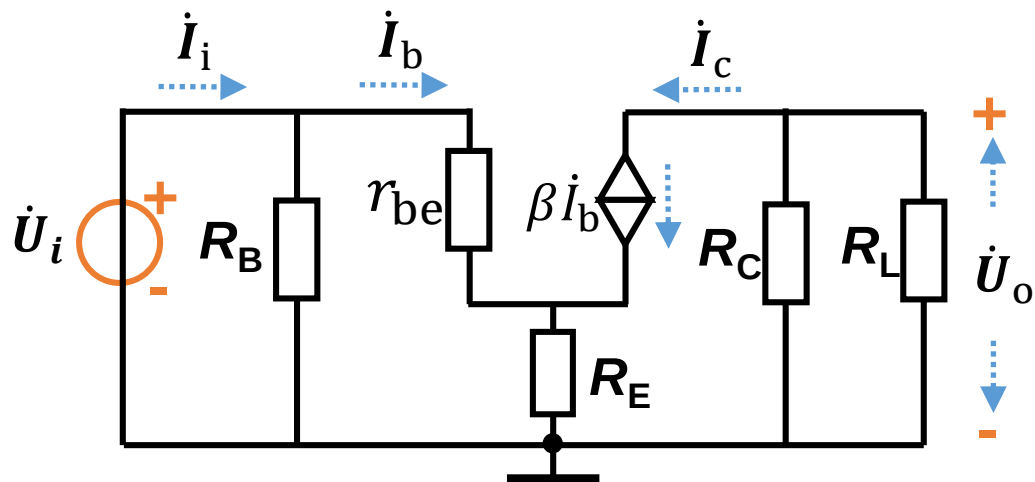
$$= 300 + 100 \frac{0.026}{0.00234} \text{ k}\Omega \approx 1.4 \text{ k}\Omega$$



Voltage gain: $\dot{A}_u = \frac{\dot{U}_o}{\dot{U}_i}$

$$\dot{U}_i = \dot{I}_b r_{be} + (\dot{I}_b + \beta \dot{I}_b) R_E$$

$$\dot{U}_o = -\dot{I}_c (R_C || R_L) = -\beta \dot{I}_b (R_C || R_L)$$


$$\dot{A}_u = -\frac{\beta (R_C || R_L)}{r_{be} + (1 + \beta) R_E} = -1.72$$

Input resistance: $R_i = \frac{\dot{U}_i}{\dot{I}_i}$

$$\dot{U}_i = (\dot{I}_i - \dot{I}_b) R_B$$

$$\dot{U}_i = \dot{I}_b r_{be} + (\dot{I}_b + \beta \dot{I}_b) R_E$$
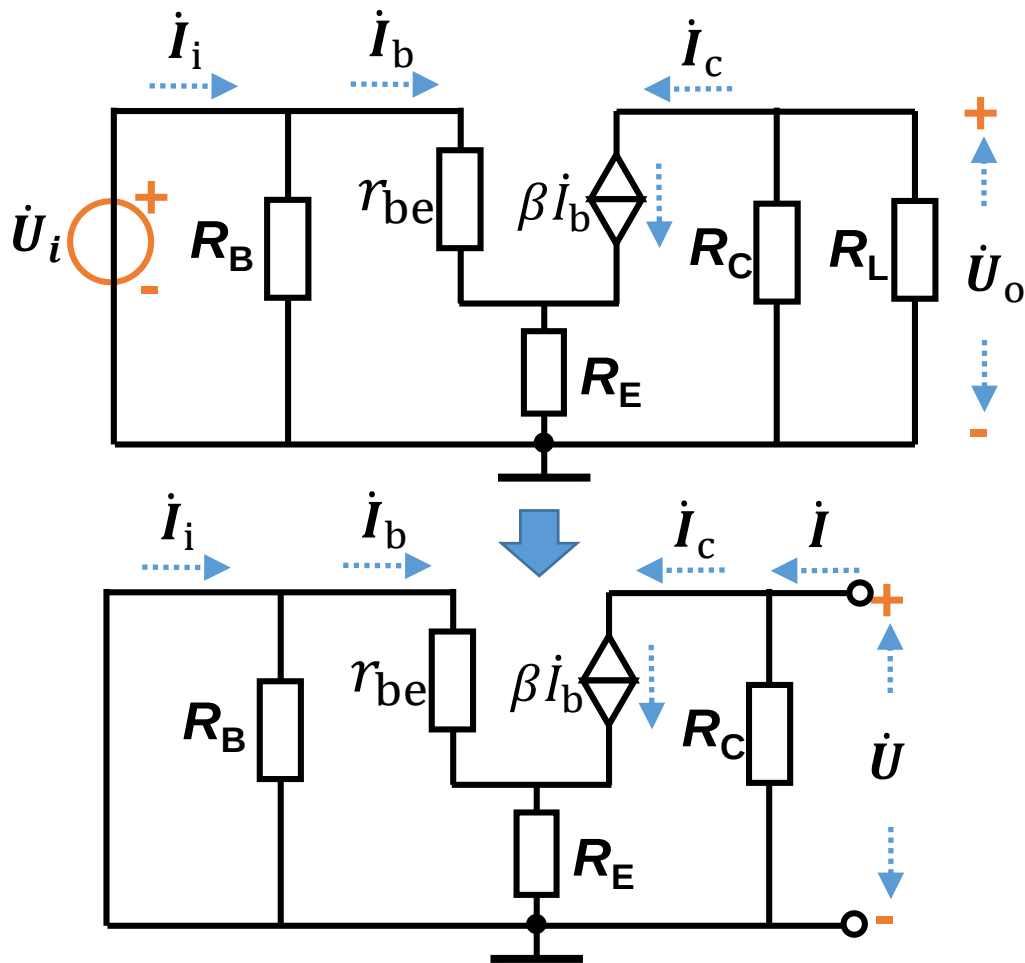
$$R_i = R_B \frac{r_{be} + (1 + \beta) R_E}{R_B + r_{be} + (1 + \beta) R_E} = 7.38 \text{ k}\Omega$$



Output resistance:

$$R_o = \frac{\dot{U}}{\dot{I}} \bigg|_{R_L=\infty, \dot{U}_i=0}$$

$$\dot{I}_b r_{be} + (\dot{I}_b + \beta \dot{I}_b) R_E = 0$$

$$\dot{I}_b = 0$$

$$\dot{I}_c = 0$$

$$R_o = R_C$$

Summary


Common-emitter amplifier

- a) Can amplify the voltage signal
- b) There is 180° phase difference between u_o and u_i
- c) Can amplify the current and power
具有电流放大能力和功率放大能力。
- d) Low input resistance and high output resistance (compared with common-collector and common-base amplifier). 具有低的输入电阻和高的输出电阻 (相比于其它接法: 共集和共基)。


2.4 Common-collector amplifier 共集极放大电路

The output voltage is from emitter (发射极), is also called emitter follower (射极输出器)

Direct coupling

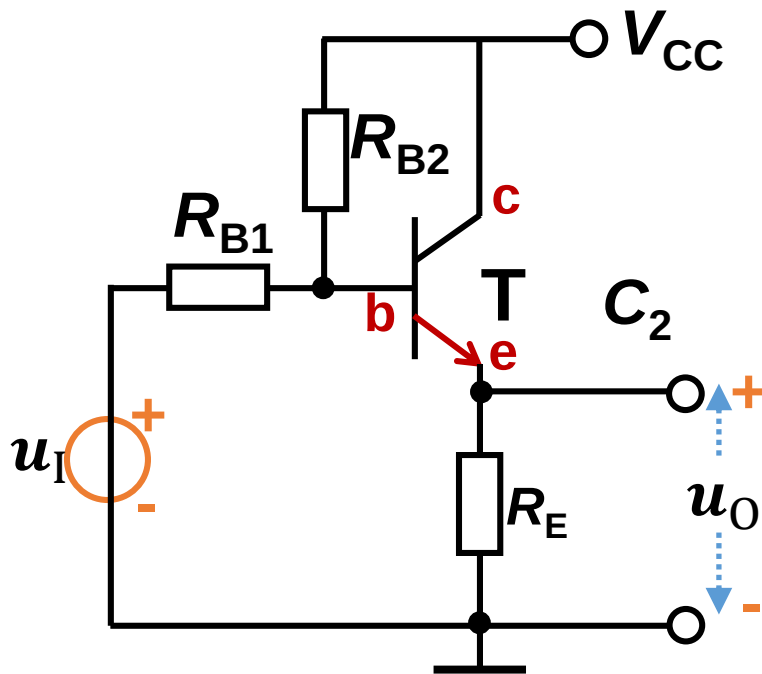


RC coupling

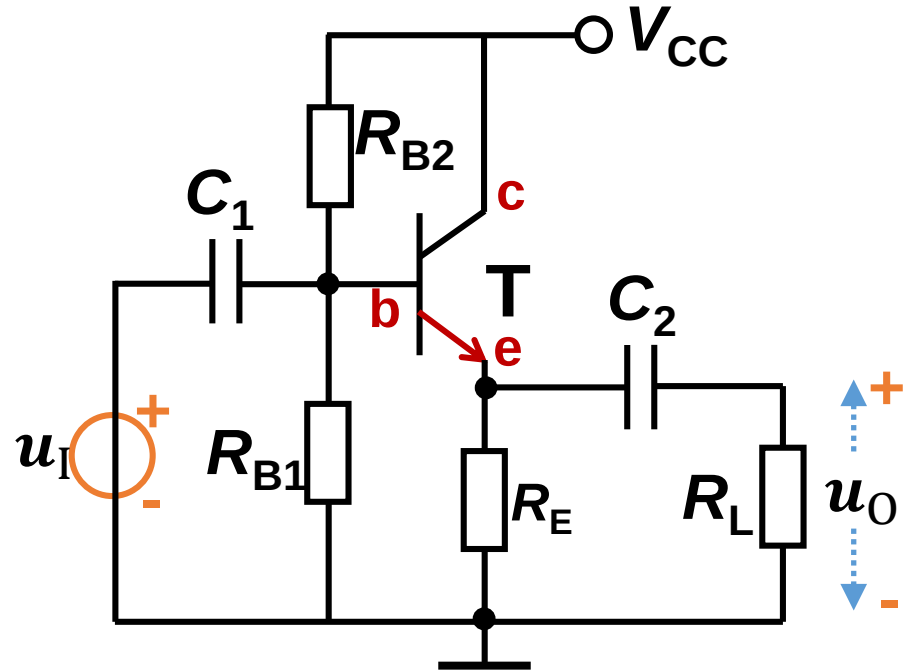


Q: Why is called common-collector?

Analyze DC circuits 静态分析

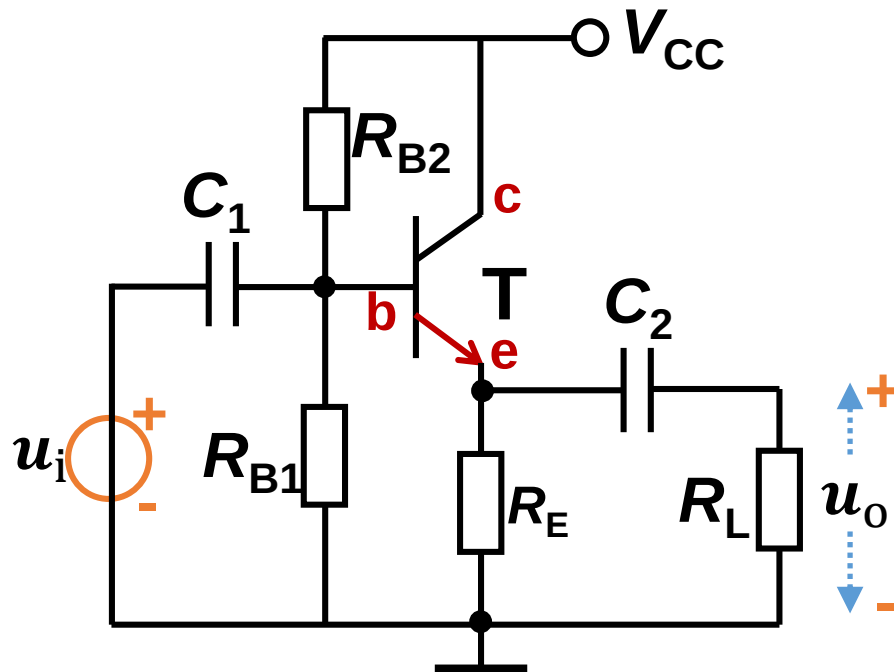


DC circuit

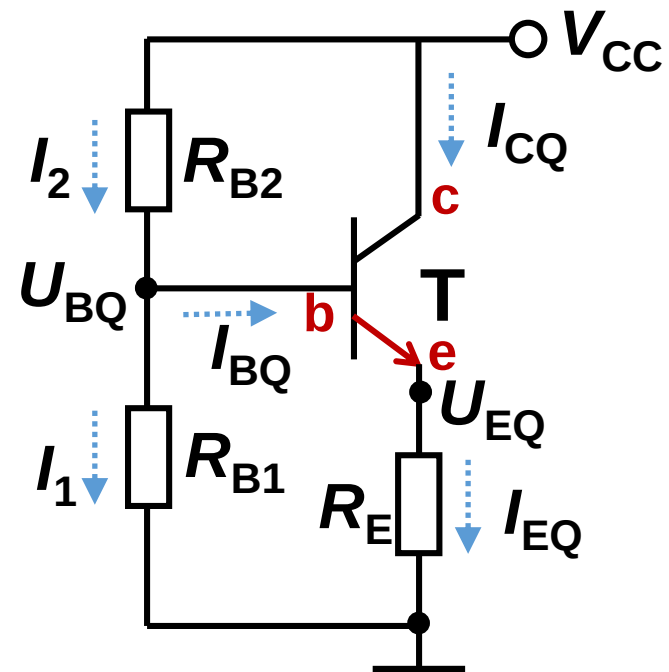

Estimation method 估算法

DC circuit

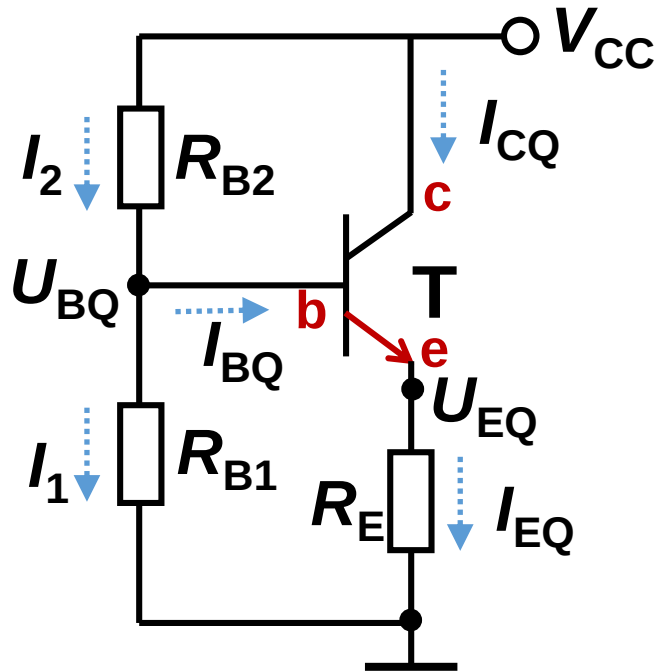

$$I_2, I_1 \gg I_{BQ}$$

$$U_{BQ} \approx \frac{R_{B1}}{R_{B1} + R_{B2}} \cdot V_{CC}$$


$$I_{EQ} = \frac{U_{EQ}}{R_E} = \frac{U_{BQ} - U_{BEQ}}{R_E}$$

$$I_{BQ} = \frac{I_{EQ}}{\beta + 1}$$


$$I_{CQ} = \beta \frac{I_{EQ}}{\beta + 1}$$

$$U_{CEQ} = V_{CC} - I_{EQ} R_E$$

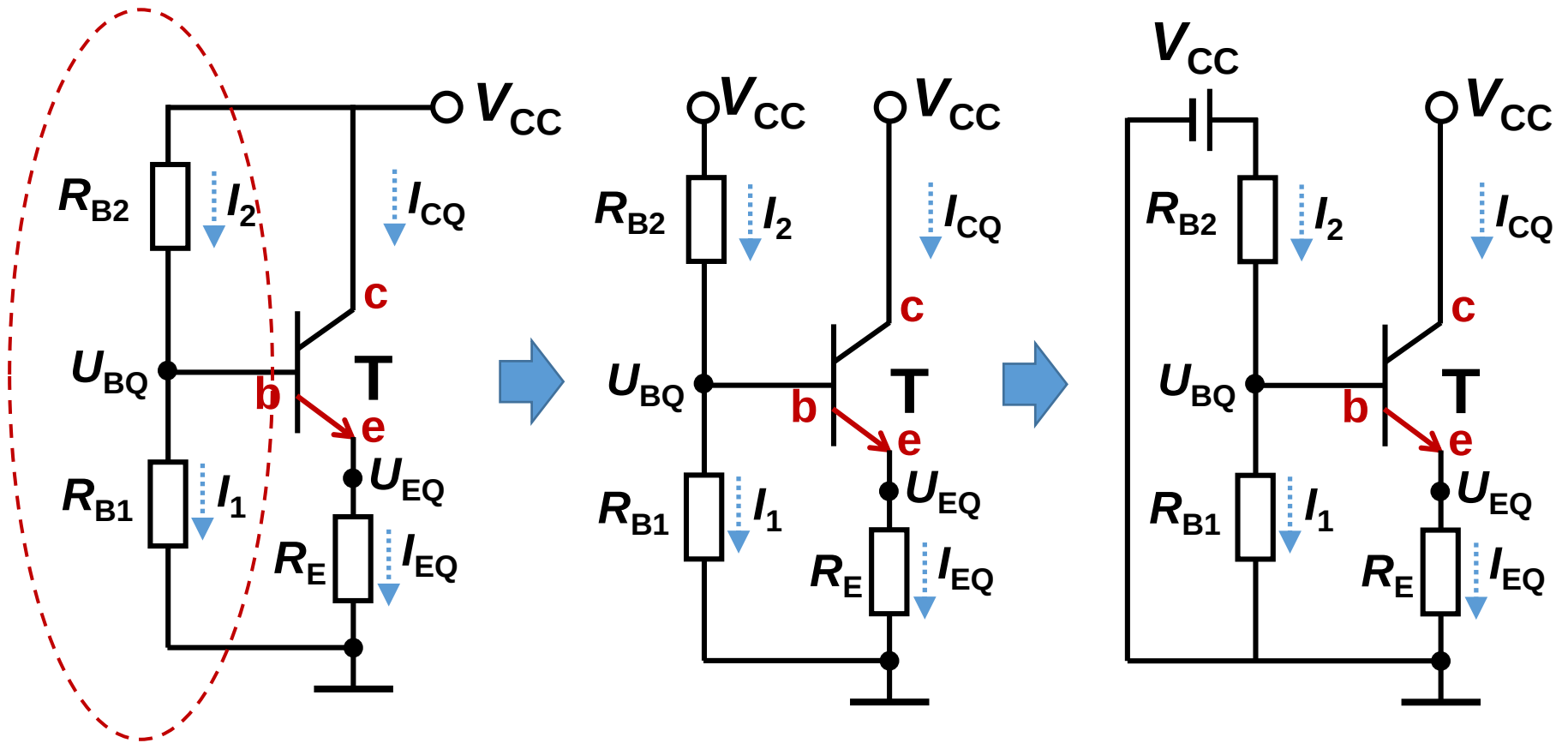Another approach: Thevenin's theorem 戴维南定理




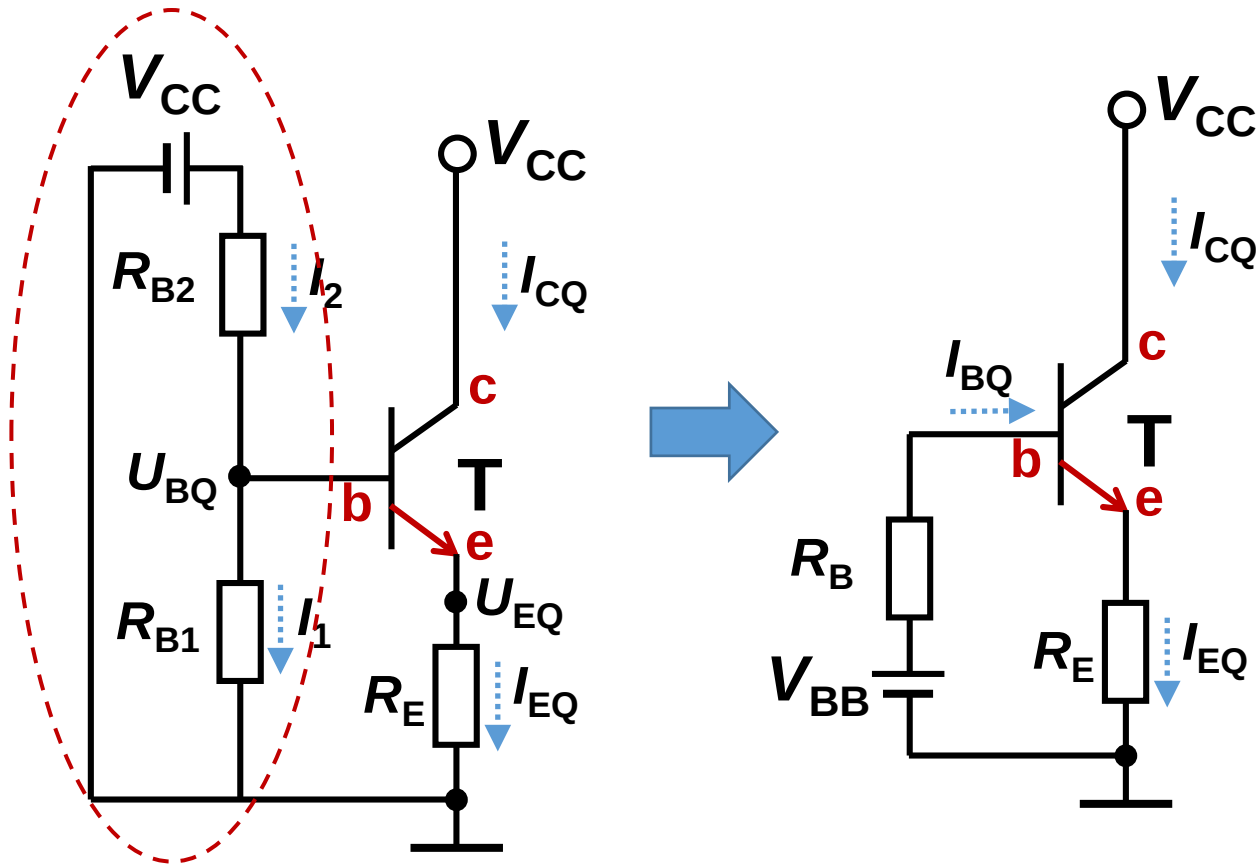Another approach: Thevenin's theorem 戴维南定理



$$V_{BB} = \frac{R_{B1}}{R_{B1} + R_{B2}} \cdot V_{CC}$$

$$R_B = R_{B1} || R_{B2}$$

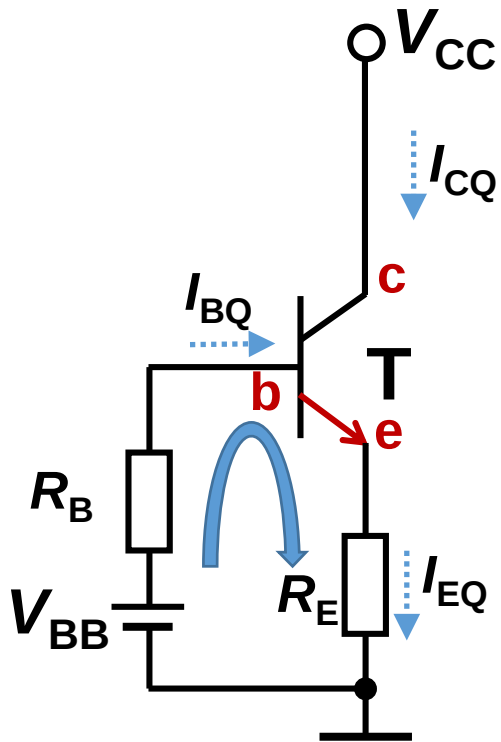


$$V_{BB} = \frac{R_{B1}}{R_{B1} + R_{B2}} \cdot V_{CC}$$

$$R_B = R_{B1} || R_{B2}$$

$$\begin{cases} V_{BB} - I_{BQ}R_B - U_{BEQ} - I_{EQ}R_E = 0 \\ I_{EQ} = (1 + \beta)I_{BQ} \end{cases}$$

$$I_{BQ} = \frac{V_{BB} - U_{BEQ}}{R_B + (1 + \beta)R_E}$$

The 3rd approach: 暴力求解法

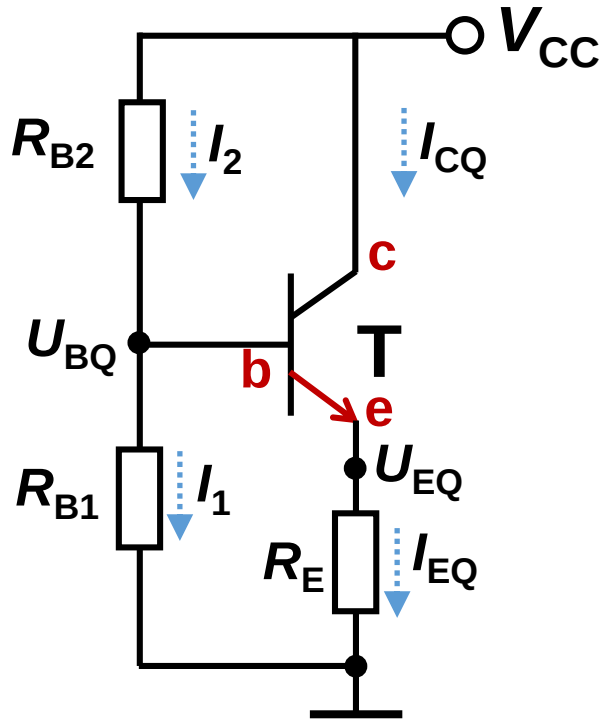



$$\left\{ \begin{array}{l} V_{CC} - I_2 R_{B2} - I_1 R_{B1} = 0 \\ U_{BEQ} + I_{EQ} R_E - I_1 R_{B1} = 0 \\ I_2 = I_1 + I_{BQ} \\ I_{EQ} = (1 + \beta) I_{BQ} \end{array} \right.$$

$$I_{BQ} = \frac{V_{BB} - U_{BEQ}}{R_B + (1 + \beta) R_E}$$


Dynamic analysis/ Analyze AC circuits 动态分析



AC circuit

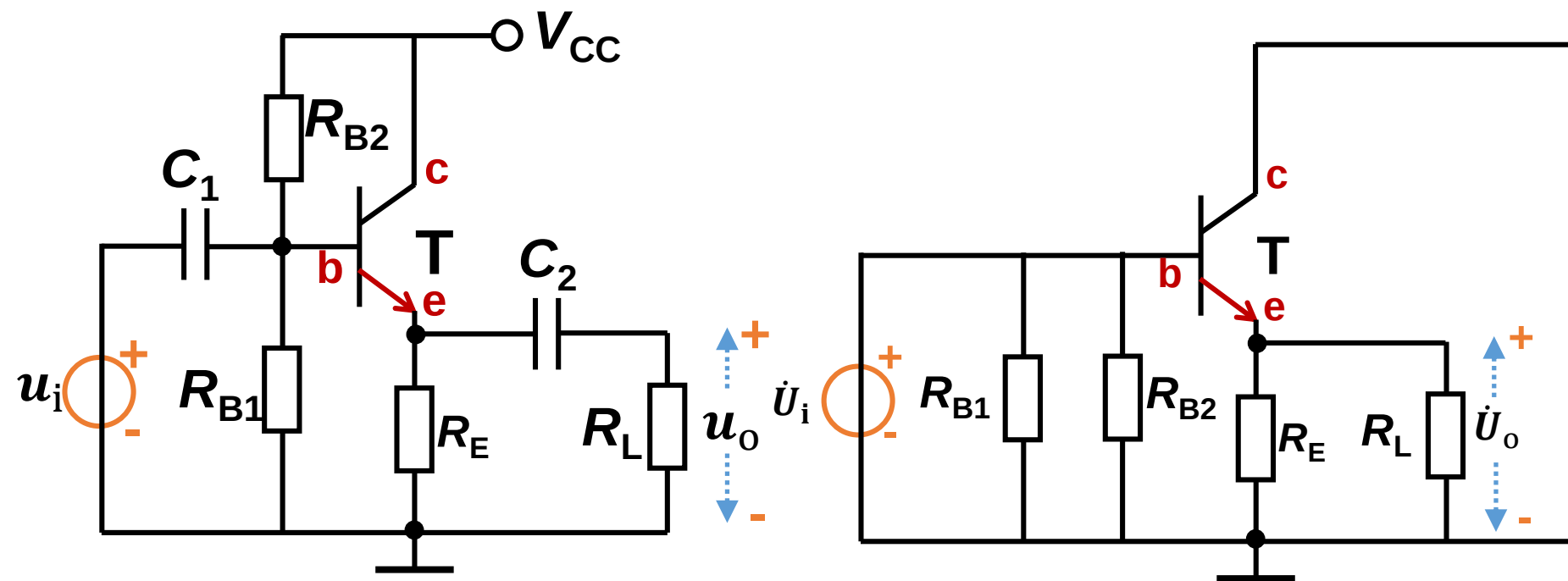

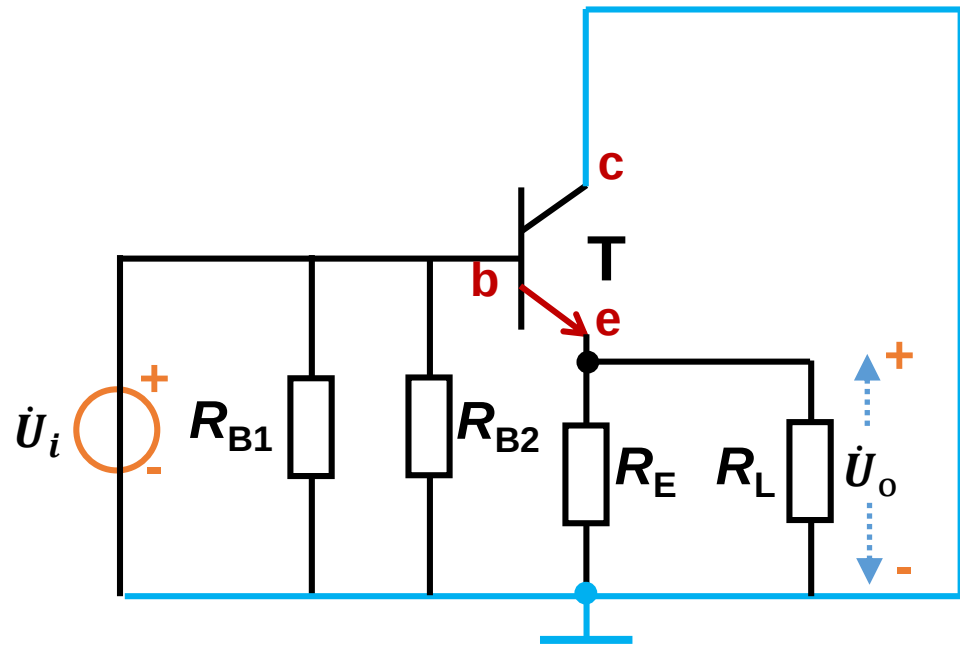



Common-collector!

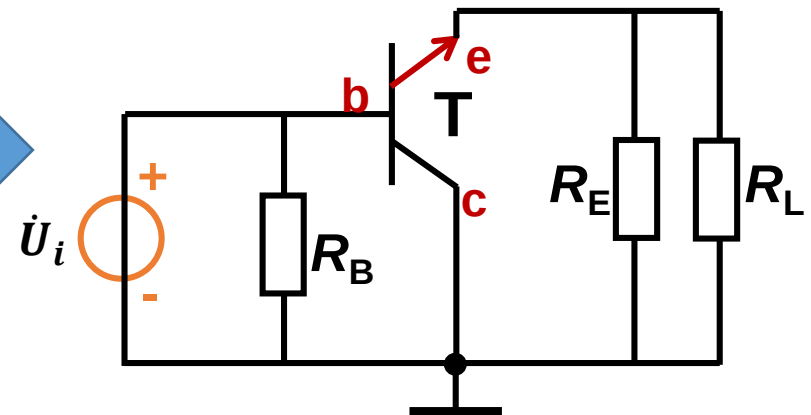

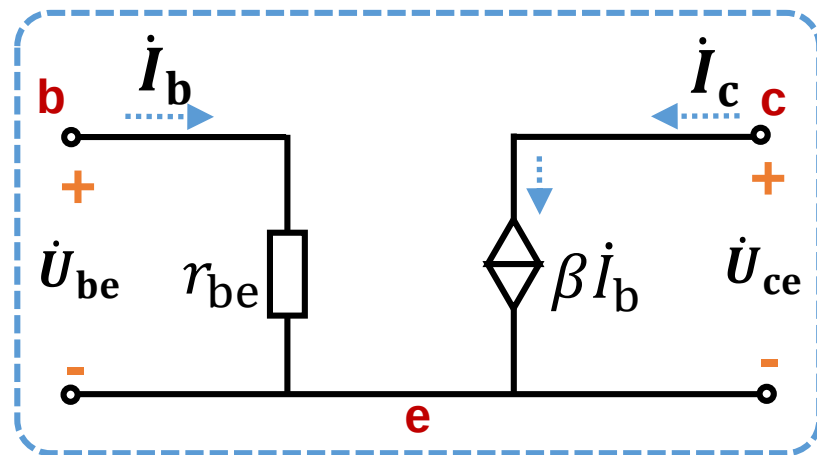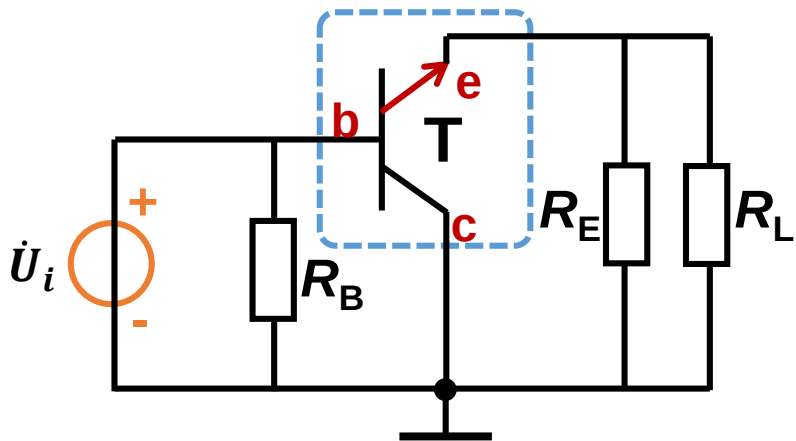

h-model

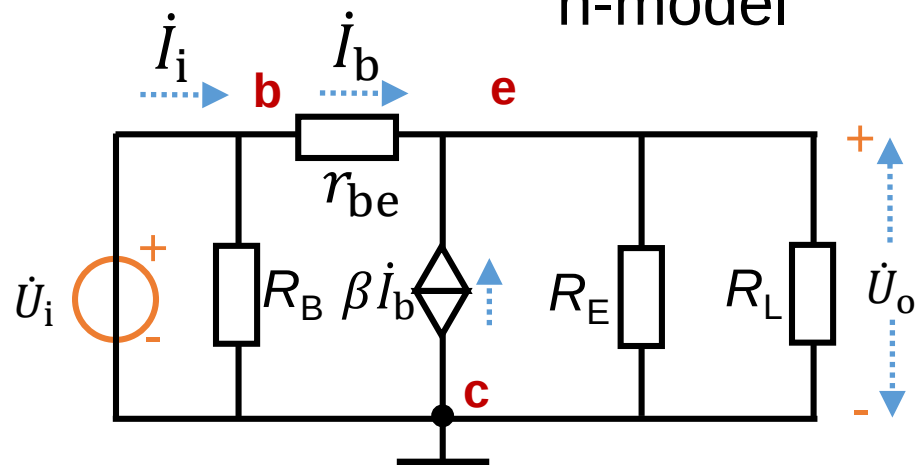

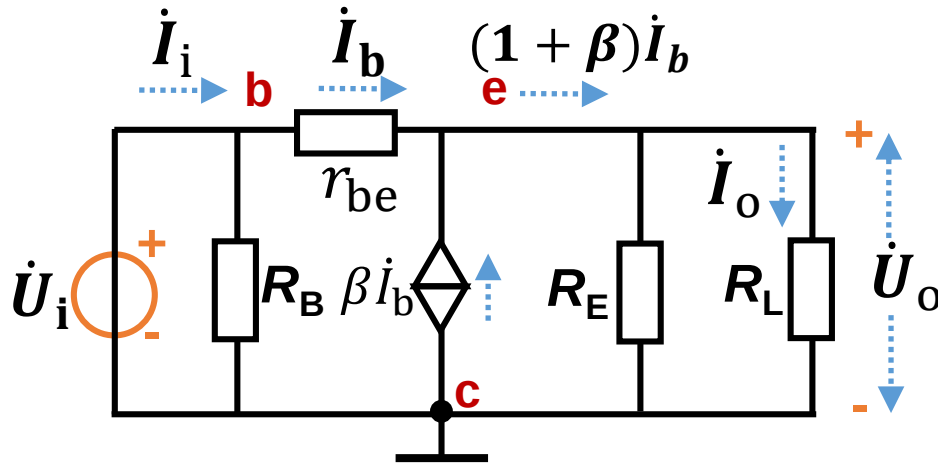

Voltage gain: $\dot{A}_u = \frac{\dot{U}_o}{\dot{U}_i}$

$$\dot{U}_o = (\dot{I}_b + \beta \dot{I}_b)(R_E || R_L)$$

$$\dot{U}_i = \dot{I}_b r_{be} + (\dot{I}_b + \beta \dot{I}_b)(R_E || R_L)$$

$$\dot{A}_u = \frac{\dot{U}_o}{\dot{U}_i} = \frac{(1 + \beta)(R_E || R_L)}{r_{be} + (1 + \beta)(R_E || R_L)}$$

$$\dot{A}_u < 1$$

Can not amplify
voltage signal!

$$r_{be} \ll (1 + \beta)(R_E || R_L) \quad \dot{A}_u \approx 1$$

Current gain: $\dot{A}_i = \frac{\dot{I}_o}{\dot{I}_i}$

$$\dot{I}_i = \dot{I}_b + \dot{U}_i / R_B$$

$$= \dot{I}_b + \dot{I}_b \frac{R_i'}{R_B}$$

$$R_i' = r_{be} + (1 + \beta)(R_E || R_L)$$

$$\dot{I}_o = \frac{R_E}{R_L + R_E} (\dot{I}_b + \beta \dot{I}_b)$$

$$\dot{A}_i = \frac{R_E}{R_L + R_E} \frac{R_B}{R_i' + R_B} (1 + \beta)$$


R_E and R_L at same order

R_B and R_i' at same order

$$\dot{A}_i > 1$$

Can amplify current!

Can amplify power!


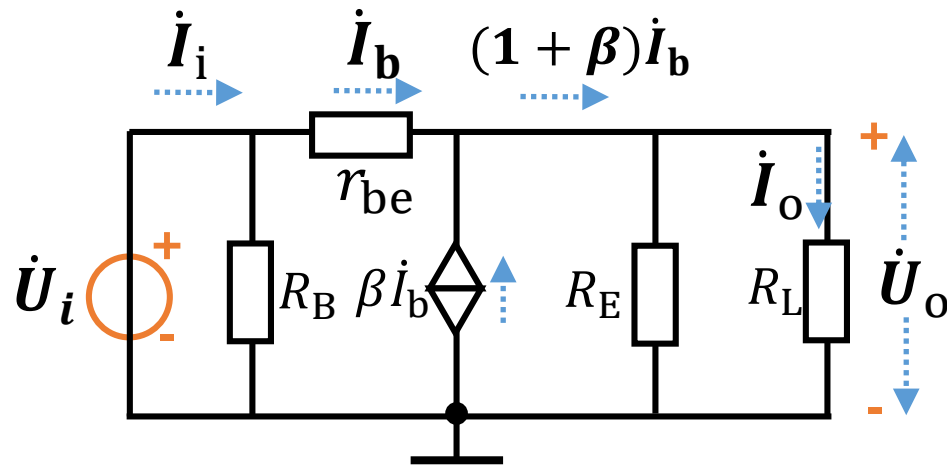


Input resistance: $R_i = \frac{\dot{U}_i}{\dot{I}_i}$

$$\dot{U}_i = \dot{I}_b r_{be} + (\dot{I}_b + \beta \dot{I}_b)(R_E || R_L)$$

$$\dot{I}_i = \dot{I}_b + \dot{U}_i / R_B$$

$$\begin{aligned} R_i = \frac{\dot{U}_i}{\dot{I}_i} &= R_B \frac{r_{be} + (1 + \beta)(R_E || R_L)}{R_B + r_{be} + (1 + \beta)(R_E || R_L)} \\ &= R_B || [r_{be} + (1 + \beta)(R_E || R_L)] \end{aligned}$$

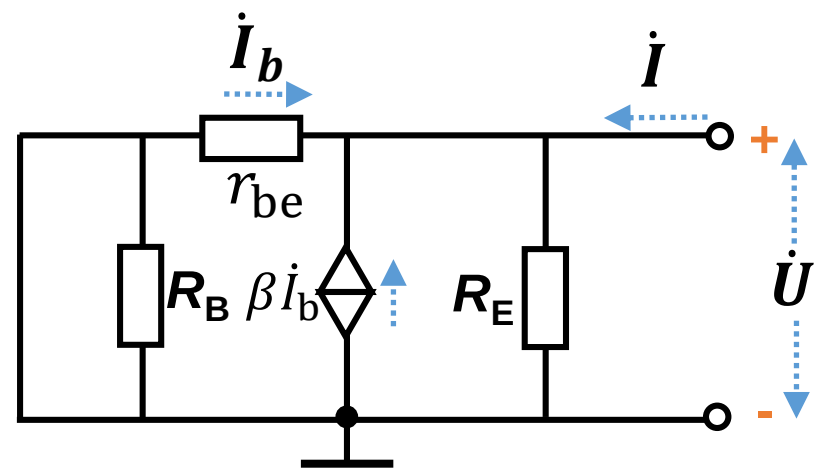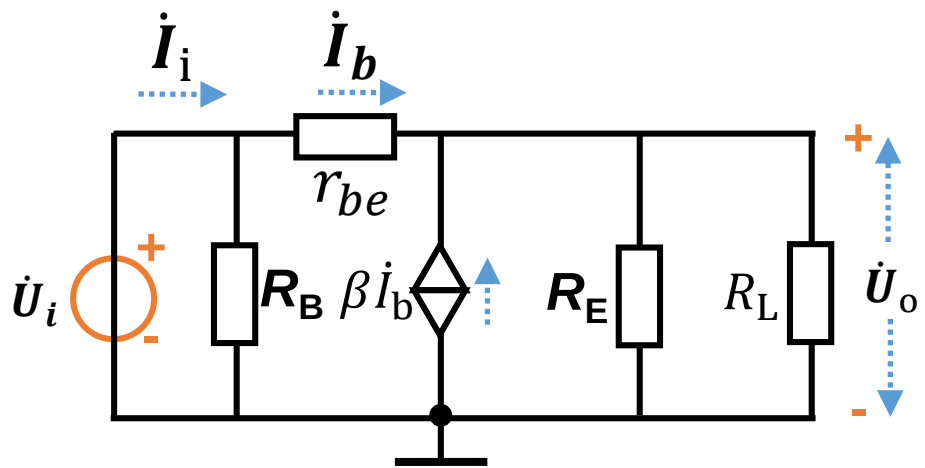

Output resistance: $R_o = \frac{\dot{U}}{\dot{I}} \big|_{R_L=\infty, \dot{U}_i=0}$

$$\dot{U} = -\dot{I}_b r_{be}$$

$$\dot{U} = (\dot{I} + \dot{I}_b + \beta \dot{I}_b) R_E$$

$$\dot{I} = -\frac{\dot{I}_b r_{be}}{R_E} - \dot{I}_b - \beta \dot{I}_b$$

$$R_o = \frac{\dot{U}}{\dot{I}} = \frac{r_{be}}{\frac{r_{be}}{R_E} + 1 + \beta} \approx \frac{r_{be}}{1 + \beta}$$

**Output resistance
is very small**

Summary

Common-collector amplifier

- a) $A_u \approx 1$: Can not amplify the voltage signal
- b) The phase of u_o and u_i are the same
- c) Can amplify the current and power
具有电流放大能力和功率放大能力。
- d) High input resistance and low output resistance

Application of Common-collector amplifier

a) Impedance transformation 阻抗变换


Used between high internal resistance source and low resistance load.

b) Input and output stage of multistage amplifier circuit


2.5 Common-base amplifier

共基极放大电路



Direct coupling

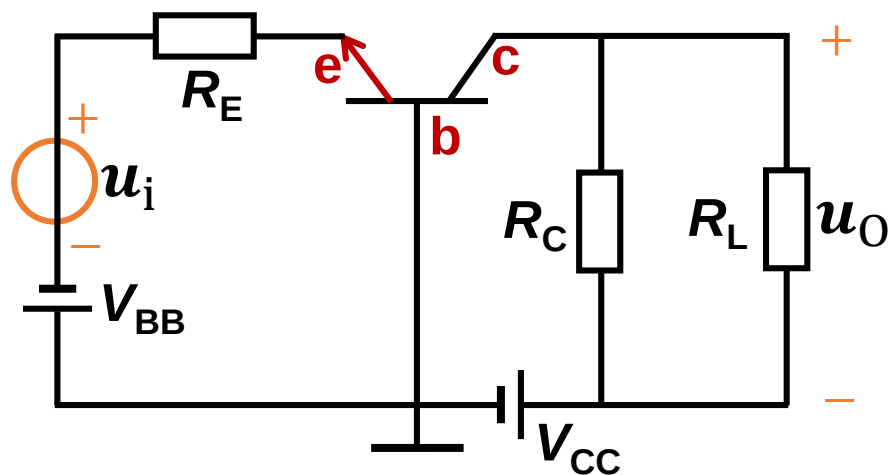



RC coupling

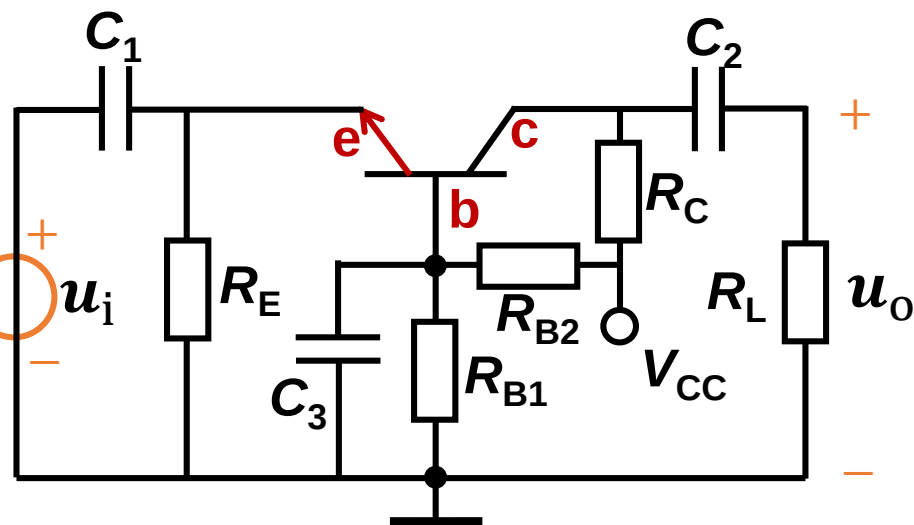


Analyze DC circuits

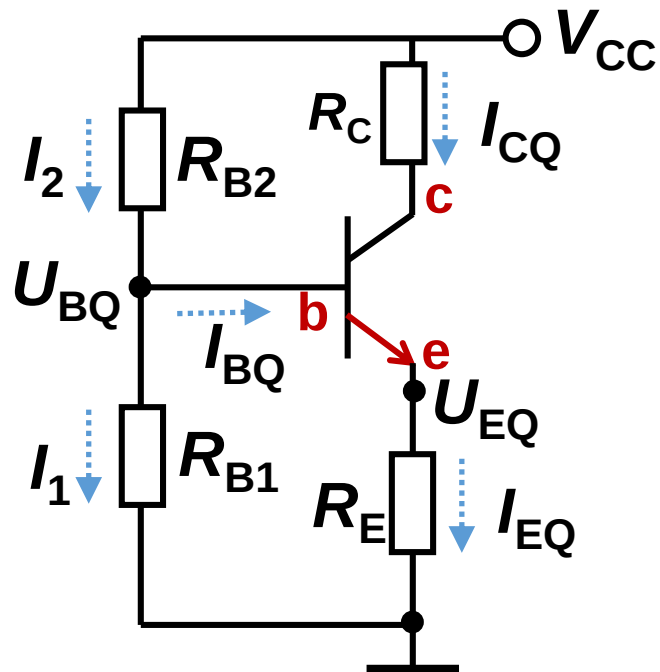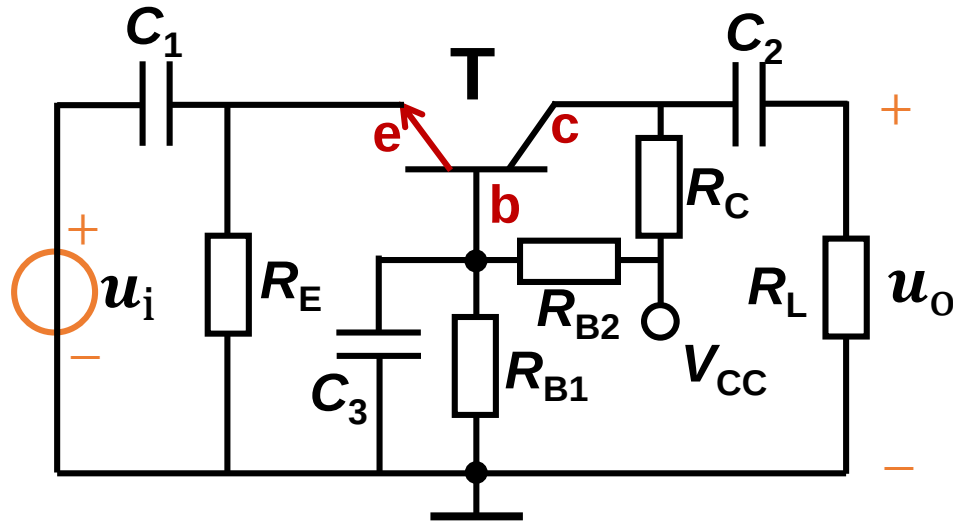


DC circuit


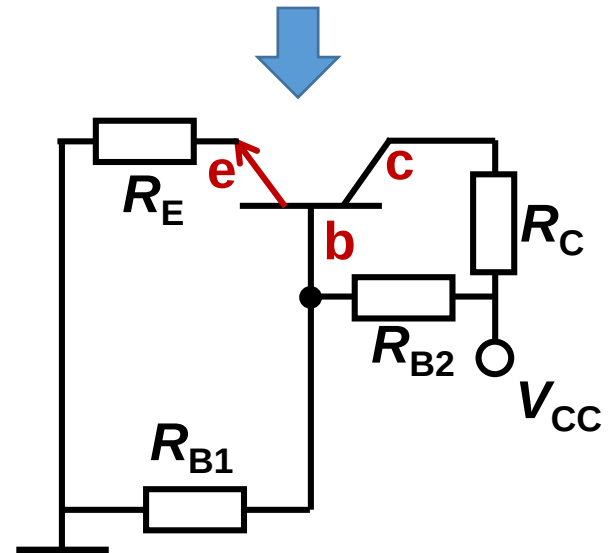
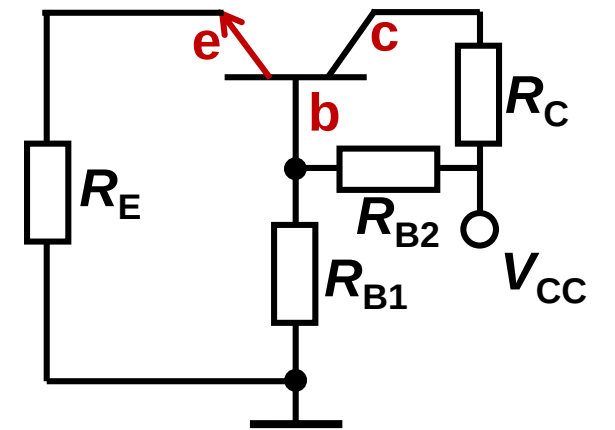


Dynamic analysis

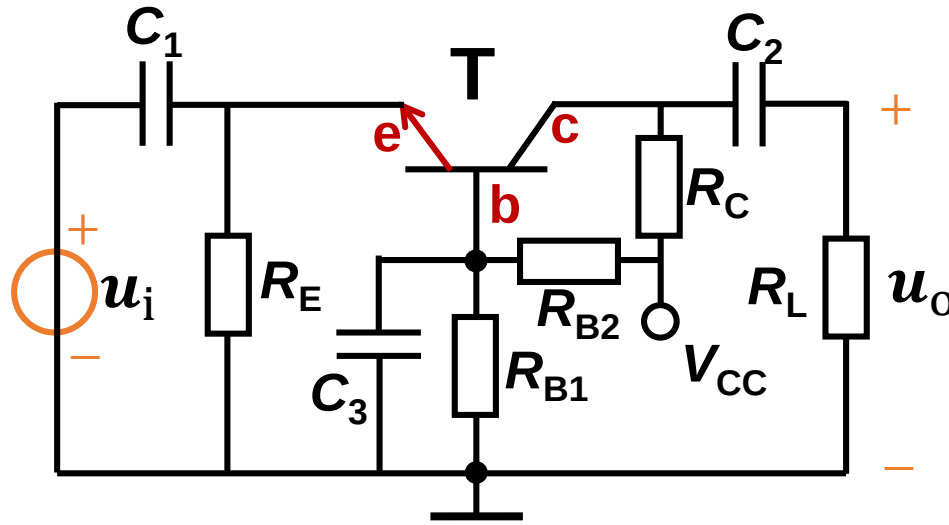

AC circuit

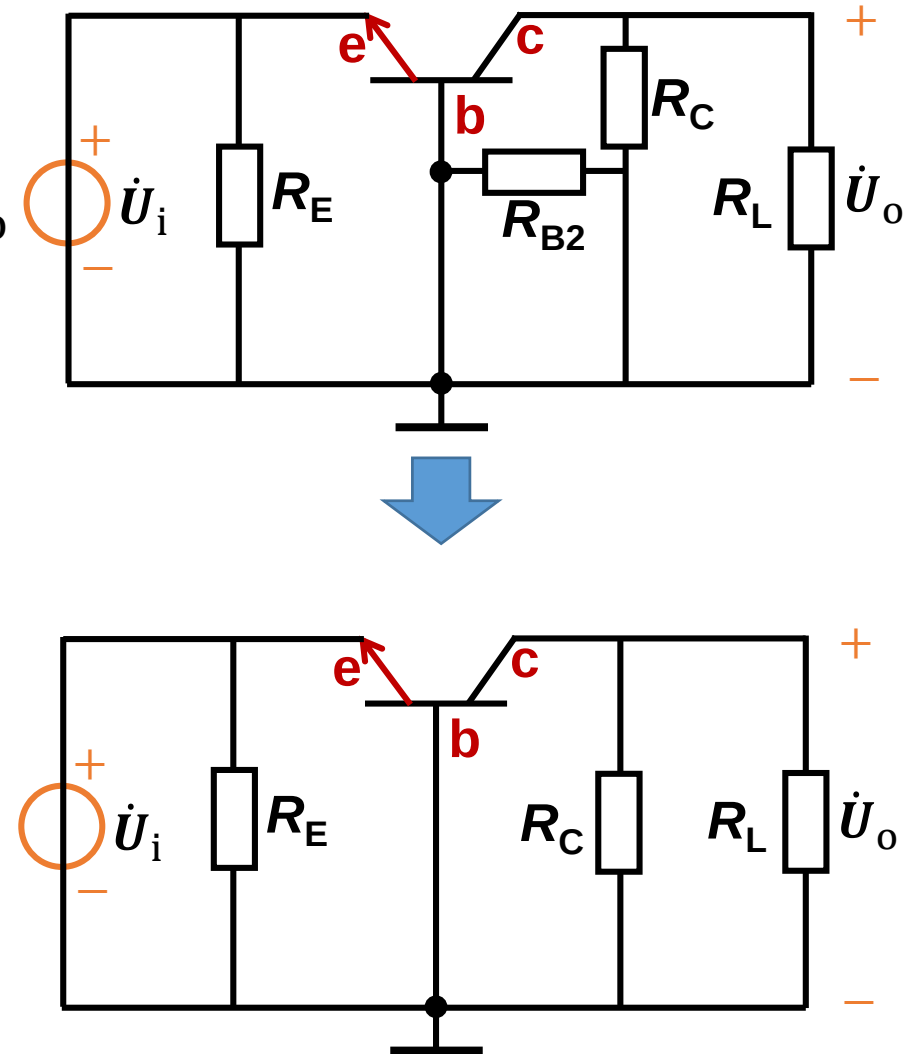

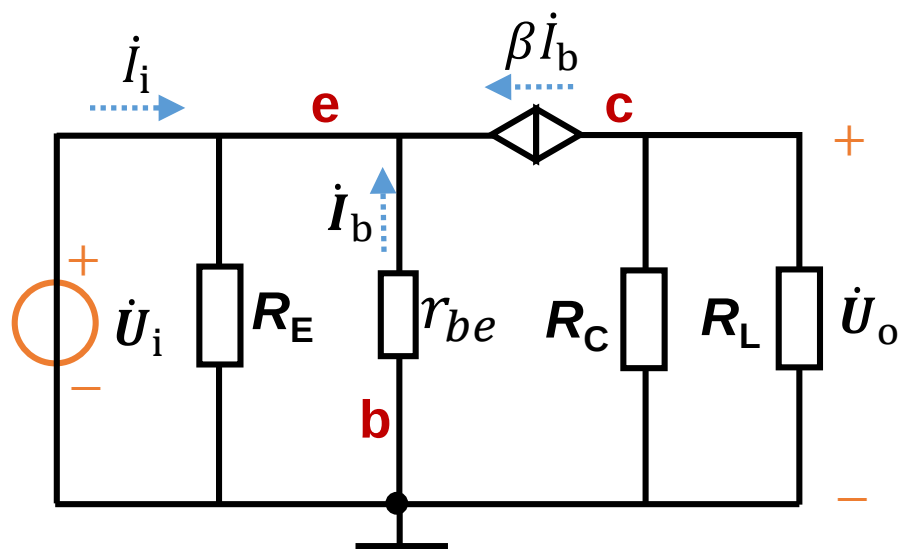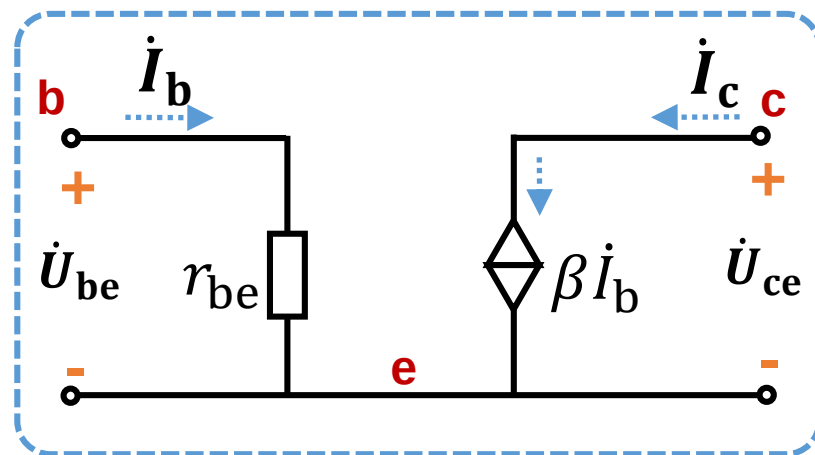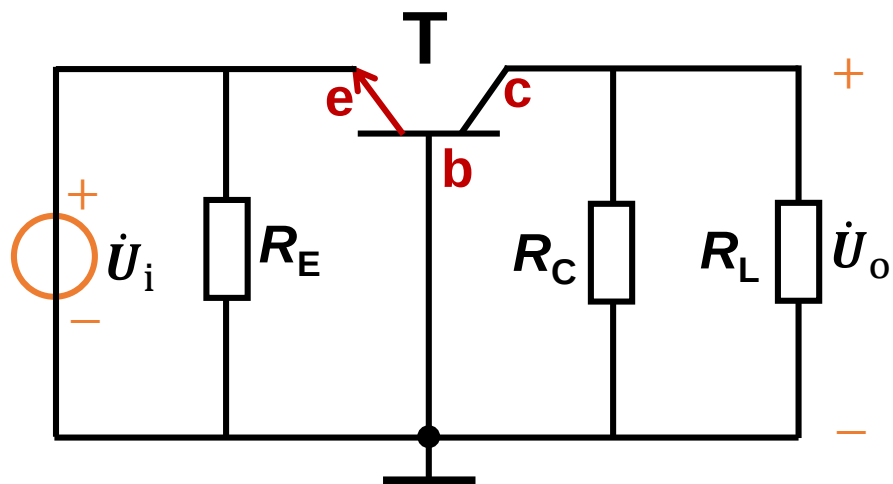

Voltage gain: $\dot{A}_u = \frac{\dot{U}_o}{\dot{U}_i}$


$$\dot{U}_o = -\beta \dot{I}_b (R_C || R_L)$$

$$\dot{U}_i = -\dot{I}_b r_{be}$$

$$\dot{A}_u = \frac{\dot{U}_o}{\dot{U}_i} = \frac{\beta (R_C || R_L)}{r_{be}}$$

$$\dot{A}_u > 1$$

Can amplify voltage

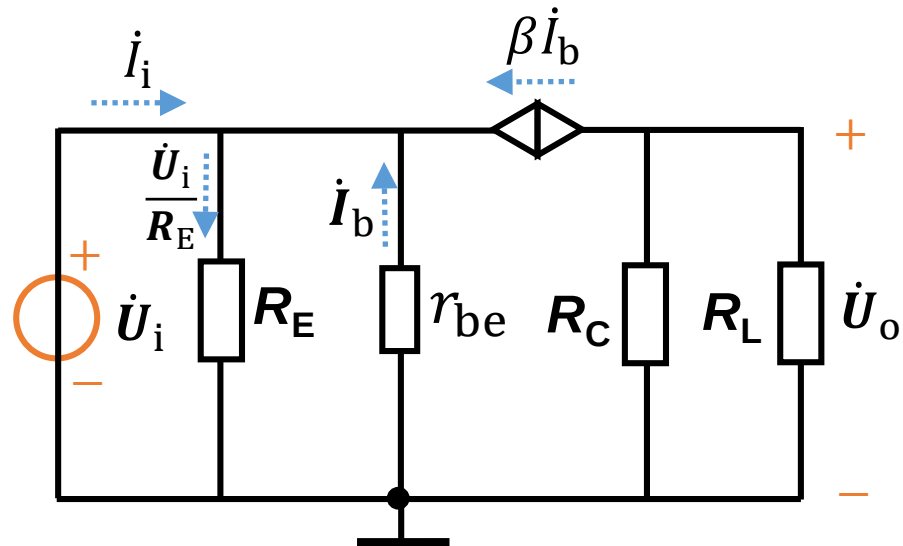


Input resistance: $R_i = \frac{\dot{U}_i}{\dot{I}_i}$

$$\dot{U}_i = -\dot{I}_b r_{be}$$

$$\dot{I}_i = -\dot{I}_b - \beta \dot{I}_b + \frac{\dot{U}_i}{R_E} = -\dot{I}_b - \beta \dot{I}_b - \frac{\dot{I}_b r_{be}}{R_E}$$

$$R_i = \frac{r_{be}}{1 + \beta + \frac{r_{be}}{R_E}}$$

Small input resistance

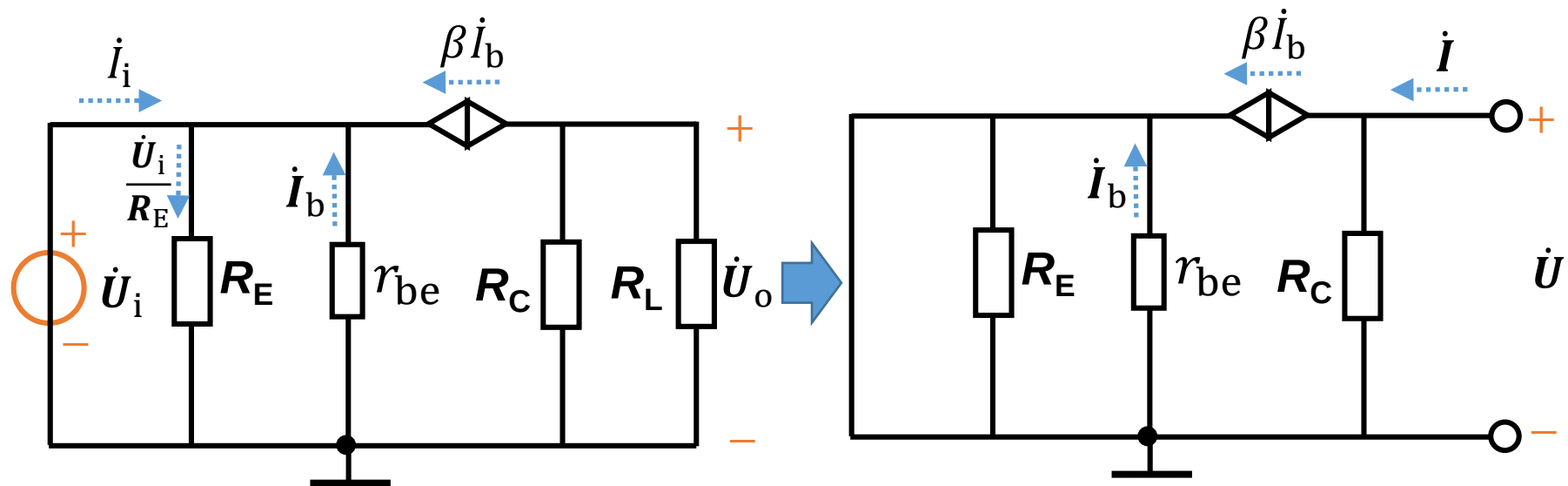


Output resistance:

$$R_o = \frac{\dot{U}}{\dot{I}} \bigg|_{R_L = \infty, \dot{U}_i = 0}$$

$$R_o = R_C$$

**Same as
common-emitter**

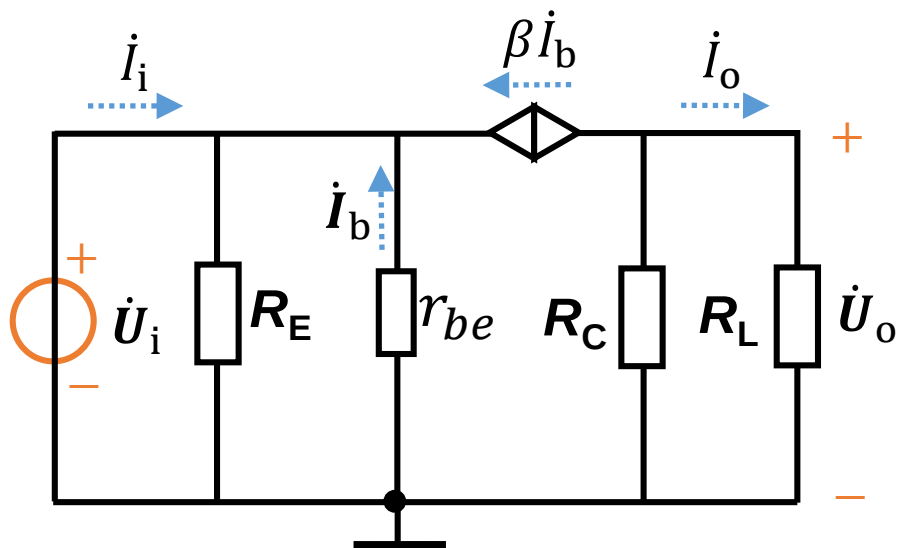

Current gain: $\dot{A}_i = \frac{\dot{I}_o}{\dot{I}_i}$

$$\dot{I}_o = -\frac{R_C}{R_C + R_L} \beta \dot{I}_b$$

$$\dot{I}_i = -\dot{I}_b - \beta \dot{I}_b - \frac{\dot{I}_b r_{be}}{R_E}$$

$$\begin{aligned} \dot{A}_i &= \frac{\dot{I}_o}{\dot{I}_i} \\ &= \frac{1}{1 + R_L/R_C} \frac{\beta}{(1 + \beta) + r_{be}/R_E} \end{aligned}$$

$$\dot{A}_i < 1$$

**Cannot amplify
current!!!**

Summary

Common-base amplifier

- a) $A_u > 1$: Can amplify voltage signal
- b) The phase of u_o and u_i are the same
- c) Cannot amplify the current
- d) Low input resistance and high output resistance

Compare of common -e, -c and -b amplifier

	Common-e	Common-c	Common-b
$\dot{A}_u$	High	<1	High
$\dot{A}_i$ No load resistor	β	$(1 + \beta)$	$\alpha = \beta / (1 + \beta)$
R_i	Medium	High	Low
R_o	High	Low	High
Bandwidth	Narrow	Medium	Wide

Low frequency
amplification circuit

High frequency
amplification circuit

Homework 2-2:


Refer to blackboard and QQ group

Hand in homework 2-1 and 2-2 together!

Deadline: 2022-03-22 11:59pm

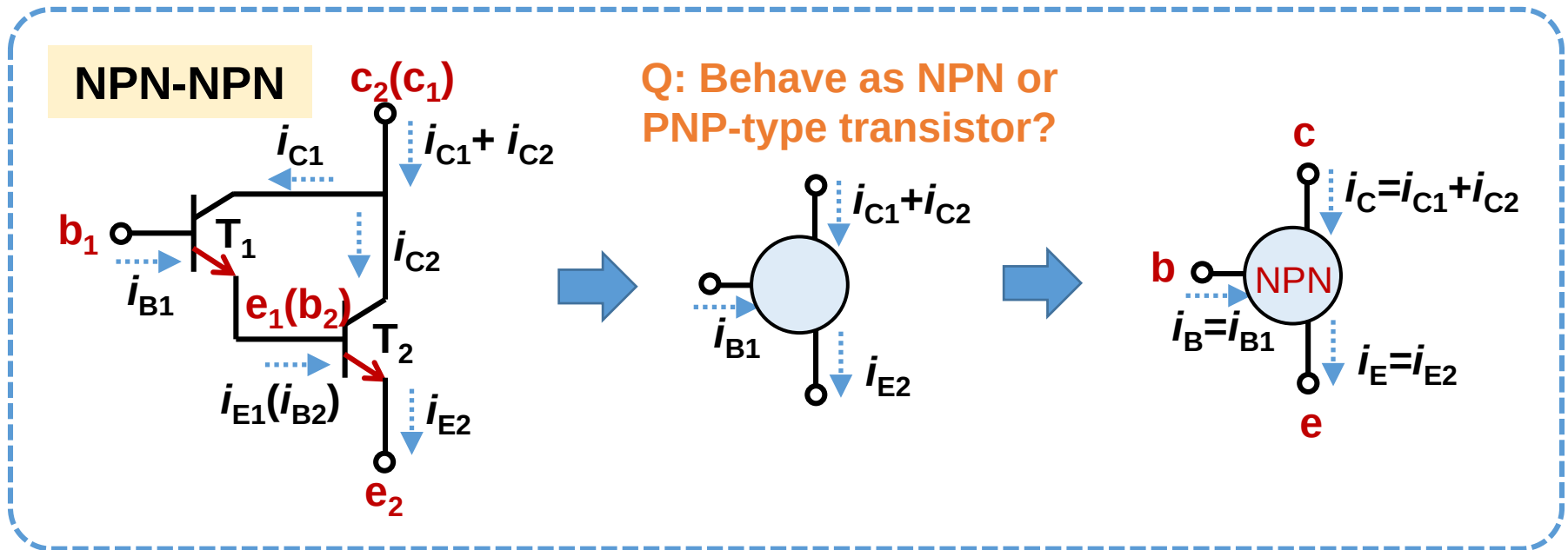2.6 Composite amplifier 复合管


Connect multiple amplifiers together to improve the voltage gain





NPN-NPN behaves as a **NPN-type** transistor

What's the current amplification factor i_C/i_B ?

NPN-NPN

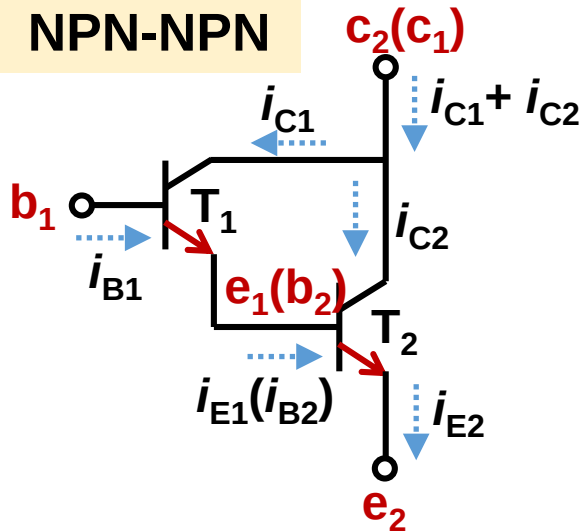

Q: Behave as NPN or PNP-type transistor?

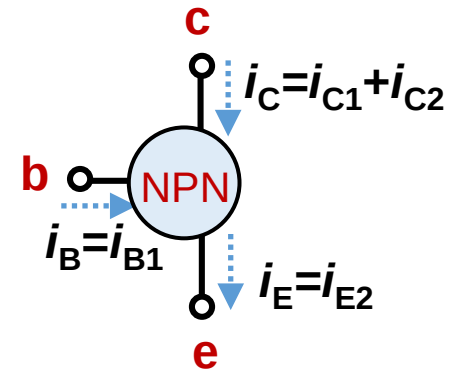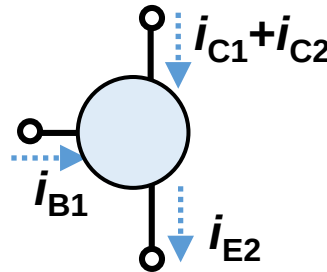

What's the current amplification factor i_C/i_B ?


$$i_B = i_{B1} \quad i_C = i_{C1} + i_{C2} = \beta_1 i_{B1} + \beta_2 i_{B2}$$

$$i_{B2} = i_{E1} = (\beta_1 + 1) i_{B1}$$


$$i_C = \beta_1 i_{B1} + \beta_2 (\beta_1 + 1) i_{B1}$$

$$\beta = \beta_1 \beta_2 + \beta_1 + \beta_2$$


PNP-PNP

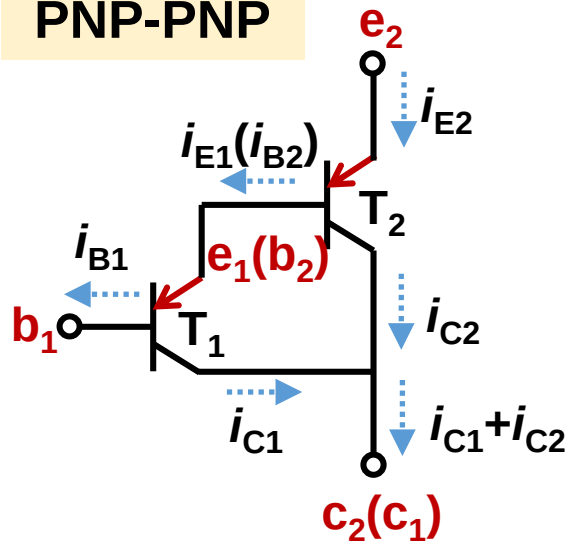

Q: Behave as NPN or PNP-type transistor?

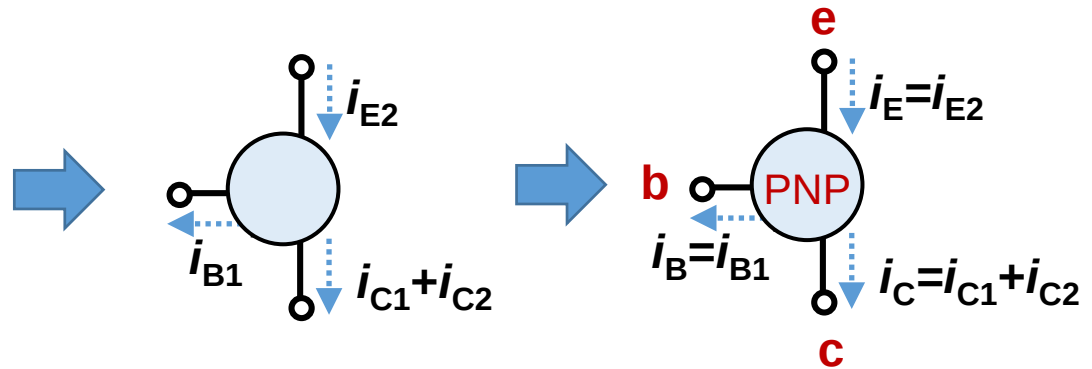

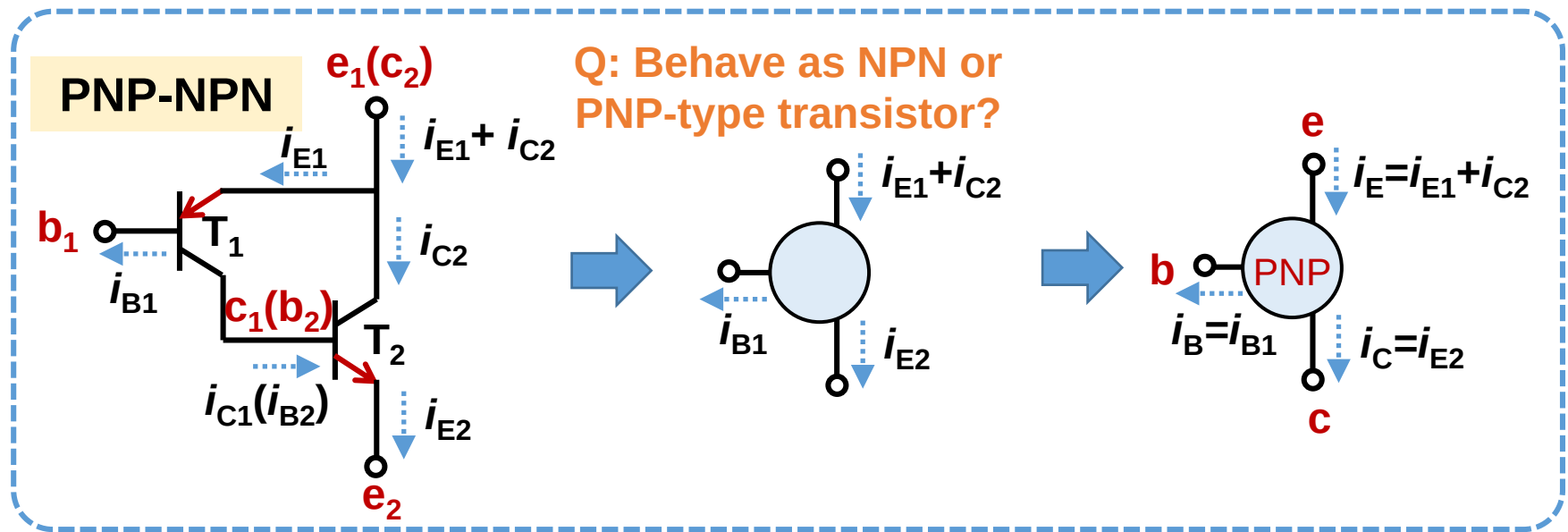PNP-PNP behaves as a **PNP-type** transistor



PNP-NPN behaves as a **PNP-type** transistor

The current amplification factor:


$$i_B = i_{B1} \quad i_C = i_{E2} = (\beta_2 + 1)i_{B2} \quad i_{B2} = i_{C1} = \beta_1 i_{B1}$$

$$i_C = \beta_1(\beta_2 + 1)i_{B1} = \beta_1(\beta_2 + 1)i_B$$

$$\beta = \beta_1(\beta_2 + 1)$$



NPN-PNP

Q: Behave as NPN or PNP-type transistor?

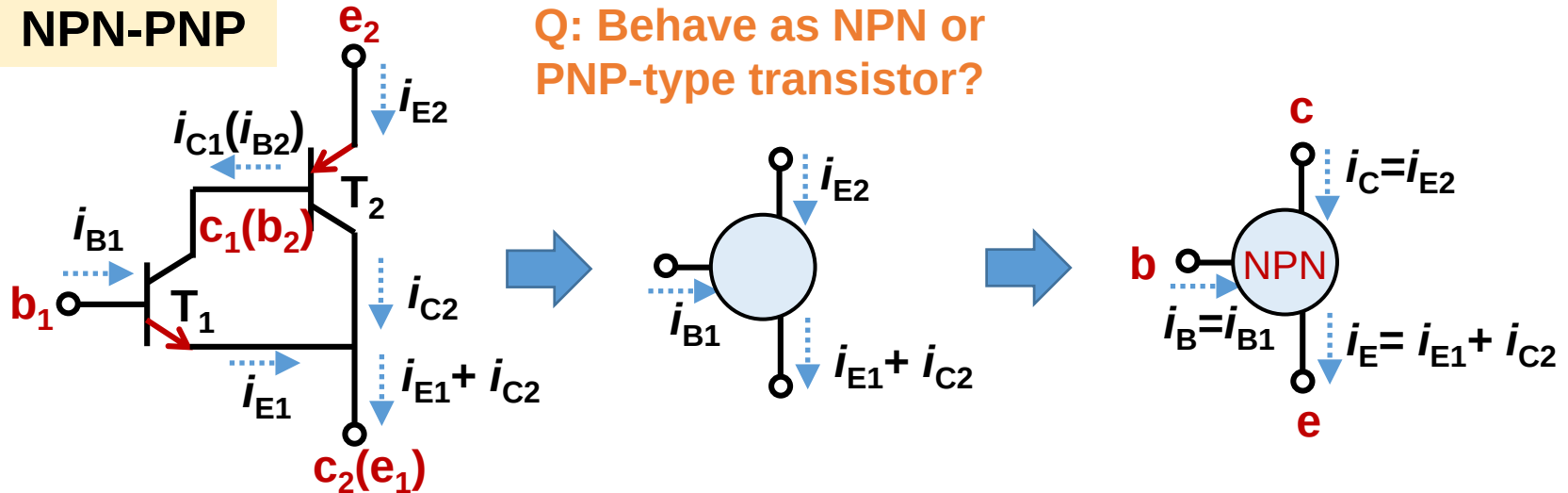

NPN-PNP behaves as a **NPN-type** transistor

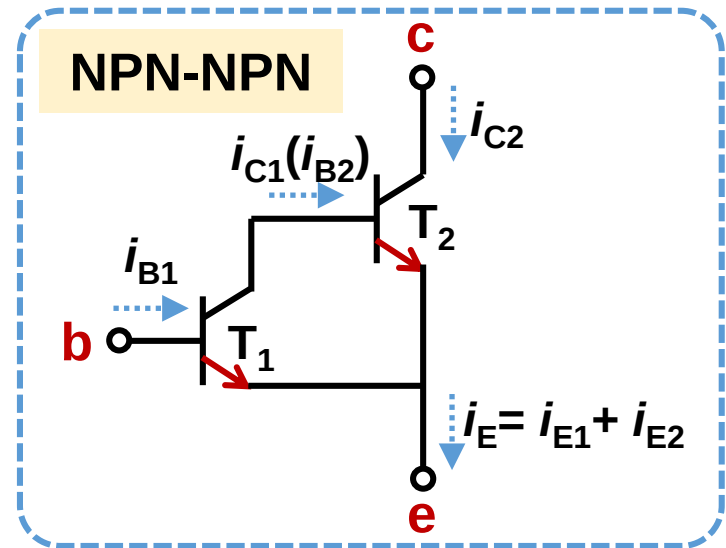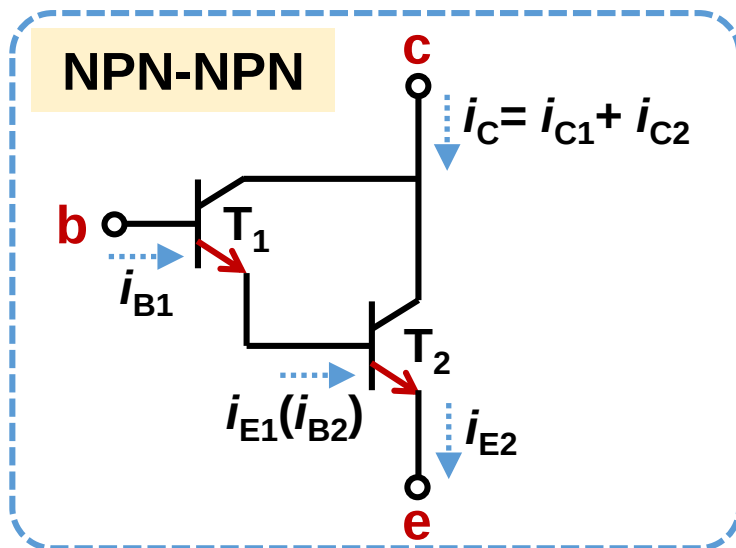The type of composite transistor is determined by T_1




Q: Can the configuration of right figure amplify the AC signal?

$$i_B = i_{B1} \quad i_C = i_{C2} = \beta_2 i_{B2} \quad i_{B2} = i_{C1} = \beta_1 i_{B1} \quad i_C = \beta_1 \beta_2 i_B$$

The operation region of Transistor T_1 is close to saturation region. **Dynamic range is very small.**



Base principle to build a composite transistor

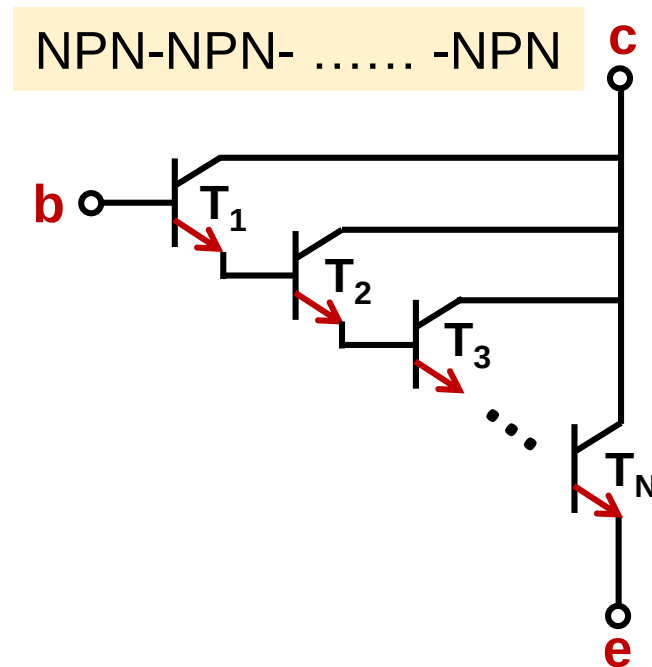1. Each transistor needs to work in the amplification region
2. Connect the emitter/collector of T_1 to the base of T_2 , connect the emitter/collector of T_2 to the base of T_3 ...



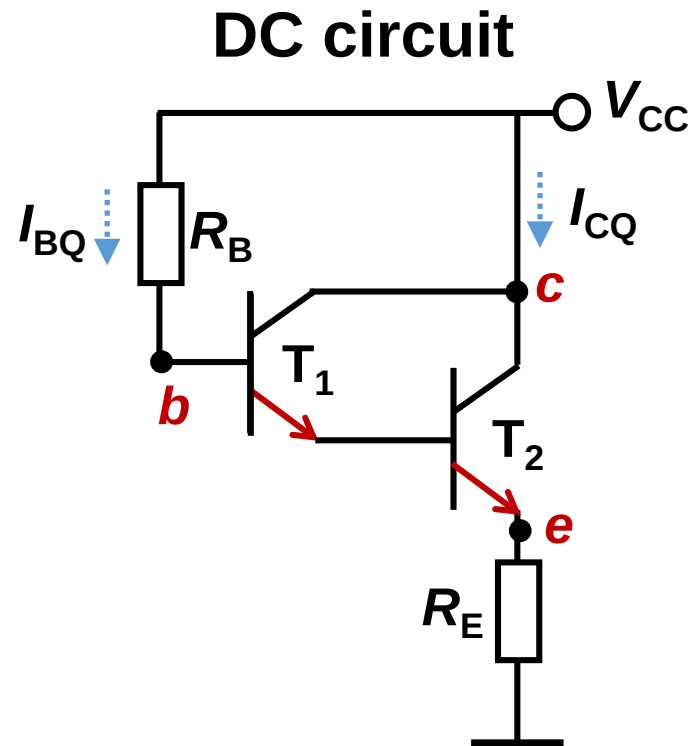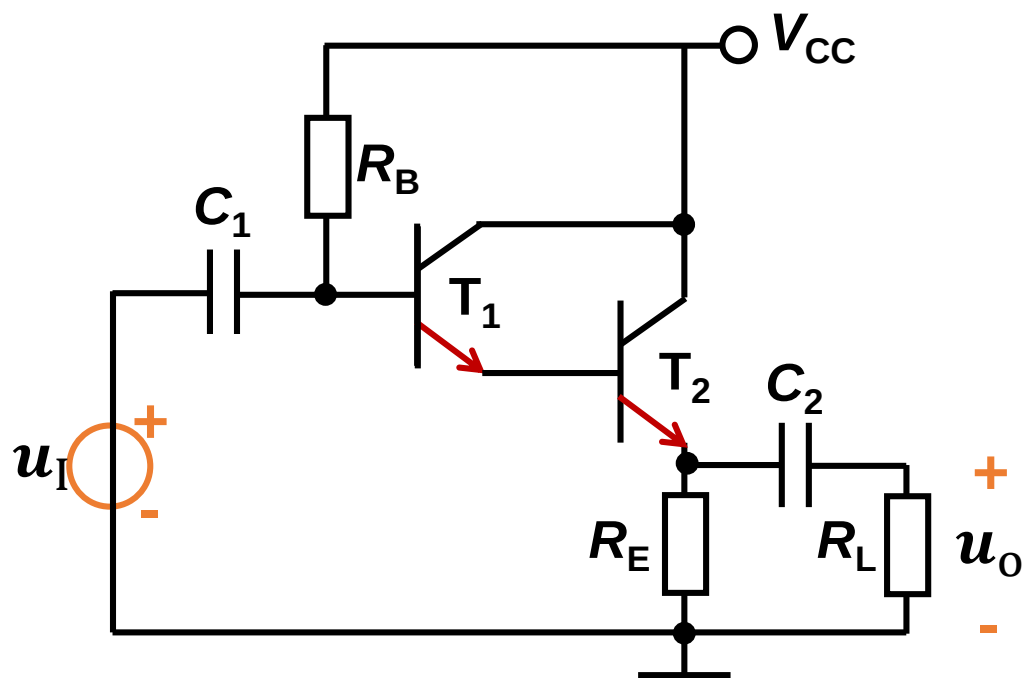2.6.2 Composite amplifier circuit

Common-collector composite amplifier circuit



Analyze DC circuits

Input circuit equation


$$V_{CC} = I_{BQ} R_B + U_{BEQ} + (I_{BQ} + I_{CQ}) R_E$$

$$\begin{cases} U_{BEQ} = U_{BEQ1} + U_{BEQ2} \text{ is known} \\ I_{CQ} = I_{CQ1} + I_{CQ2} = \beta_1 I_{BQ} + \beta_2 I_{BQ2} \\ I_{BQ2} = I_{E1} = (1 + \beta_1) I_{BQ} \end{cases}$$


$$I_{CQ} = I_{CQ1} + I_{CQ2} = \beta_1 I_{BQ} + \beta_2 (1 + \beta_1) I_{BQ}$$

$$I_{BQ} = \frac{V_{CC} - U_{BEQ}}{R_B + (1 + \beta_1 + \beta_2 + \beta_1 \beta_2) R_E}$$

I_{CQ} and I_{EQ}

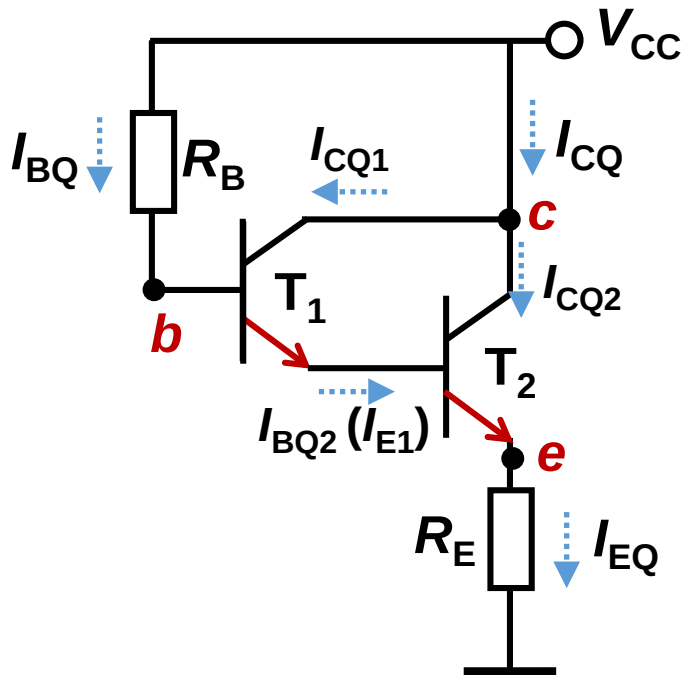

Analyze DC circuits

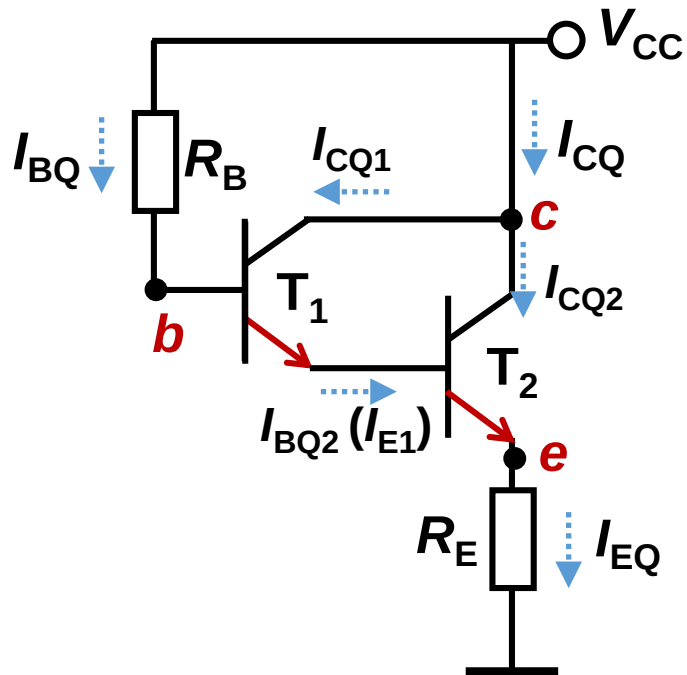





Output circuit equation




$$V_{CC} = U_{CEQ} + I_{EQ} R_E$$

↓

$$U_{CEQ}$$

Analyze AC circuits

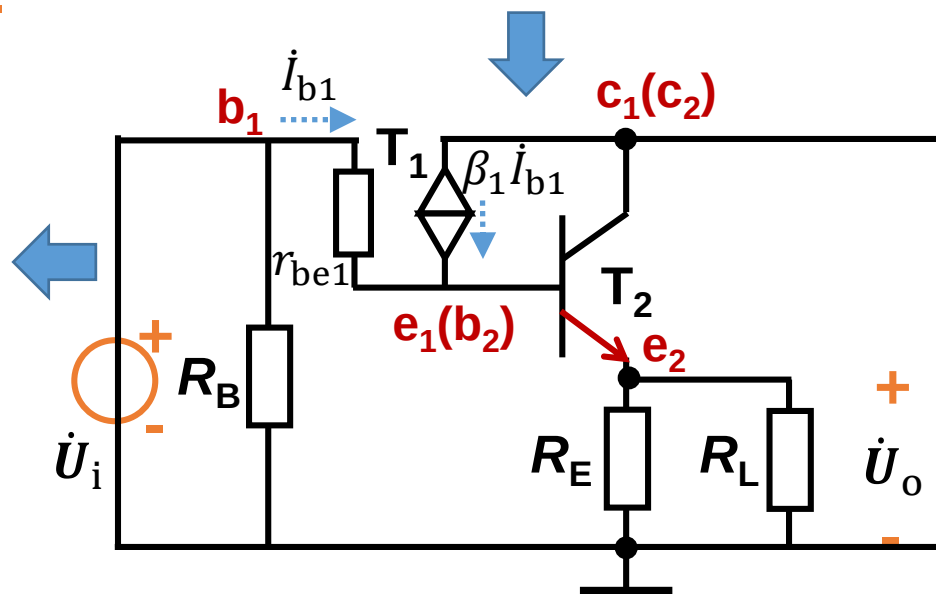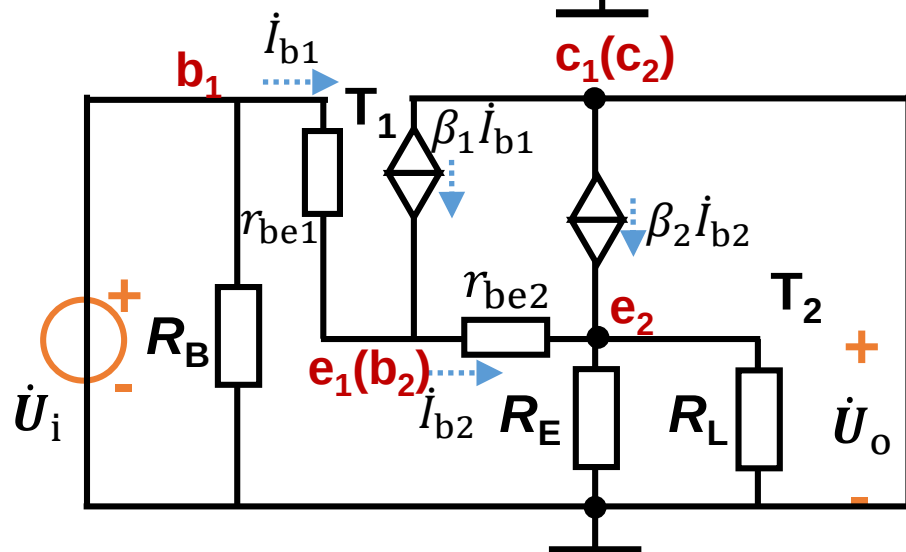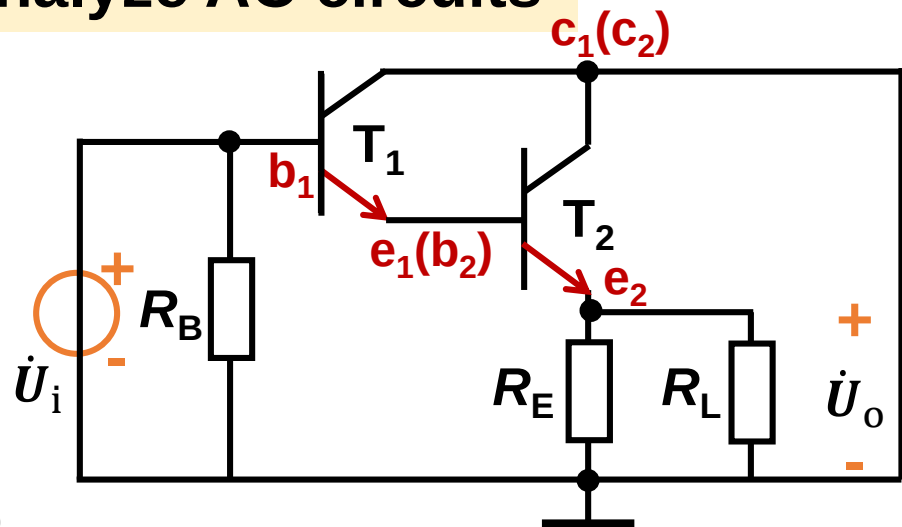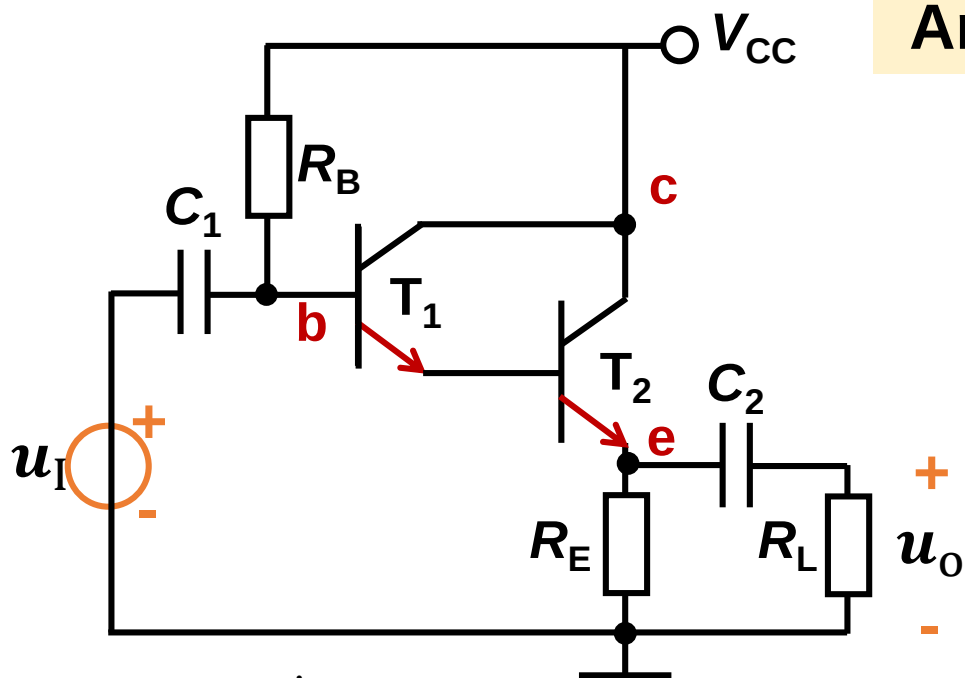

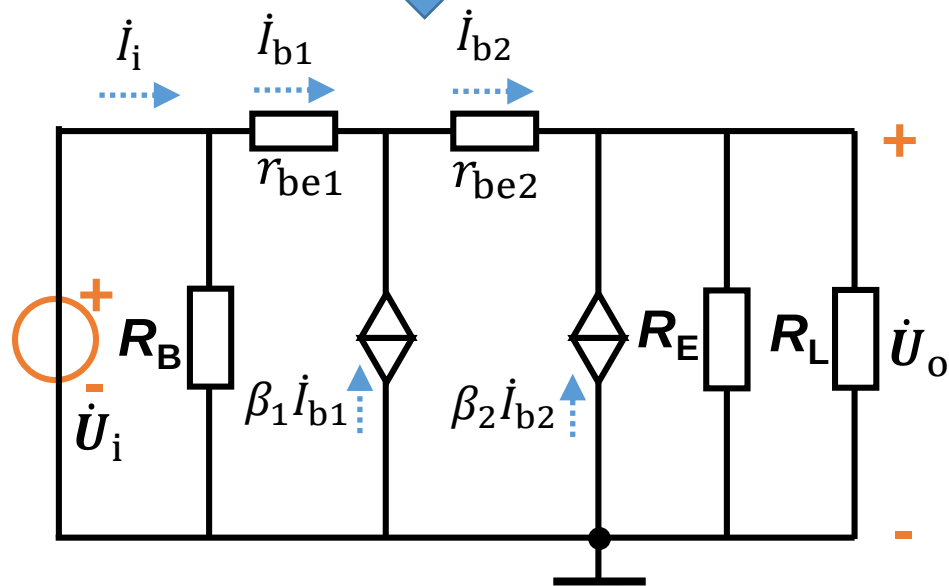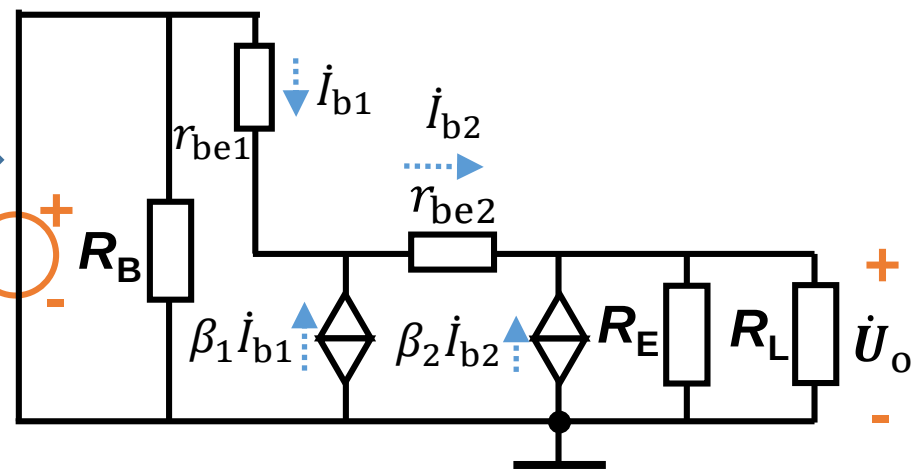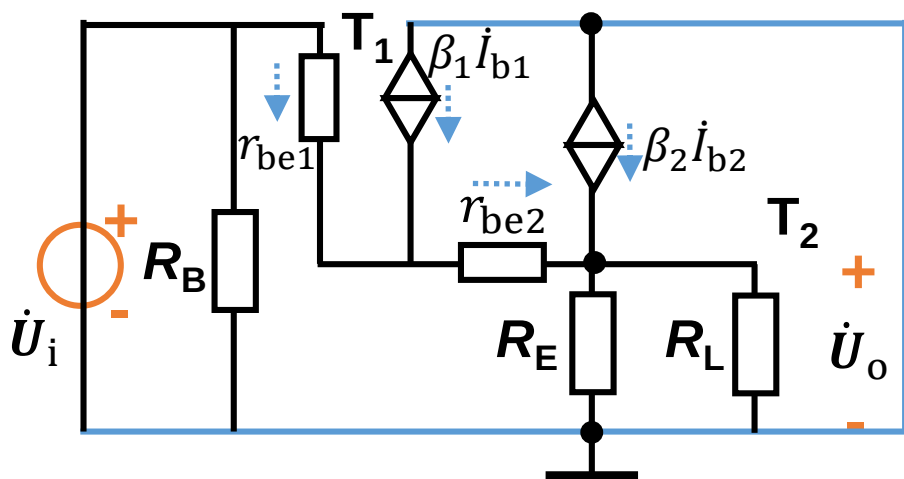


Voltage gain: $\dot{A}_u = \frac{\dot{U}_o}{\dot{U}_i}$

$$\dot{I}_{b2} = (1 + \beta_1) \dot{I}_{b1}$$

$$\begin{aligned} \dot{U}_o &= (1 + \beta_2) \dot{I}_{b2} (R_E || R_L) \\ &= (1 + \beta_1)(1 + \beta_2) \dot{I}_{b1} (R_E || R_L) \end{aligned}$$

$$\begin{aligned} \dot{U}_i &= \dot{I}_{b1} r_{be1} + \dot{I}_{b2} r_{be2} + \dot{U}_o \\ &= \dot{I}_{b1} r_{be1} + (1 + \beta_1) \dot{I}_{b1} r_{be2} + \dot{U}_o \end{aligned}$$

$$\dot{A}_u = \frac{\dot{U}_o}{\dot{U}_i} = \frac{1}{1 + \frac{r_{be1} + (1 + \beta_1) r_{be2}}{(1 + \beta_1)(1 + \beta_2)(R_E || R_L)}}$$

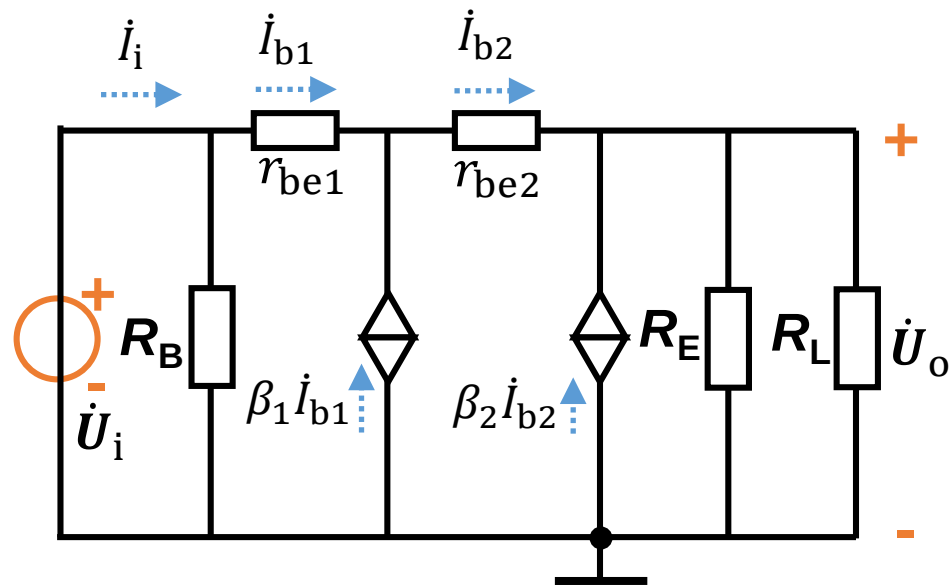

Input resistance: $R_i = \frac{\dot{U}_i}{\dot{I}_i}$

$$\dot{I}_{b2} = (1 + \beta_1) \dot{I}_{b1}$$


$$\begin{aligned} \dot{U}_o &= (1 + \beta_2) \dot{I}_{b2} (R_E \parallel R_L) \\ &= (1 + \beta_1)(1 + \beta_2) \dot{I}_{b1} (R_E \parallel R_L) \end{aligned}$$

$$\begin{aligned} \dot{U}_i &= \dot{I}_{b1} r_{be1} + \dot{I}_{b2} r_{be2} + \dot{U}_o \\ &= \dot{I}_{b1} r_{be1} + (1 + \beta_1) \dot{I}_{b1} r_{be2} + \dot{U}_o \end{aligned}$$

$$\dot{I}_i = \dot{I}_{b1} + \dot{U}_i / R_B$$

$$R_i = \frac{\dot{U}_i}{\dot{I}_i} = \frac{\dot{U}_i}{\dot{I}_{b1} + \dot{U}_i / R_B} = \frac{1}{\dot{I}_{b1} / \dot{U}_i + 1 / R_B}$$
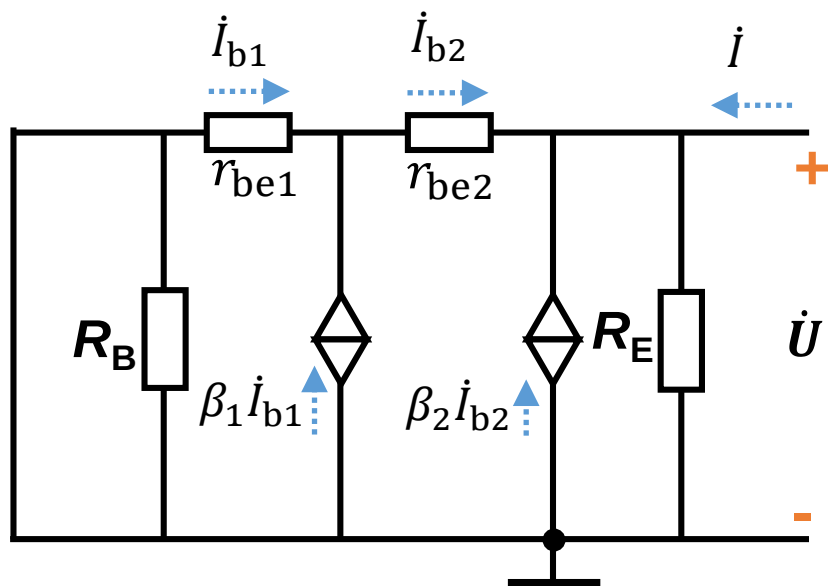
$$= R_B \parallel [r_{be1} + (1 + \beta_1) r_{be2} + (1 + \beta_1)(1 + \beta_2) (R_E \parallel R_L)]$$



Output resistance: $R_o = \frac{\dot{U}}{\dot{i}} \big|_{R_L=\infty, \dot{U}_i=0}$

$$\dot{I}_{b2} = (1 + \beta_1) \dot{I}_{b1}$$

$$\begin{aligned} \dot{U} &= -\dot{I}_{b1} r_{be1} - \dot{I}_{b2} r_{be2} \\ &= -\dot{I}_{b1} r_{be1} - (1 + \beta_1) \dot{I}_{b1} r_{be2} \end{aligned}$$

$$\begin{aligned} \dot{I} &= -(1 + \beta_2) \dot{I}_{b2} + \dot{U}/R_E \\ &= -(1 + \beta_2)(1 + \beta_1) \dot{I}_{b1} + \frac{\dot{U}}{R_E} \end{aligned}$$

$$\begin{aligned} R_o &= \frac{\dot{U}}{\dot{I}} = \frac{\dot{U}}{-(1 + \beta_2)(1 + \beta_1) \dot{I}_{b1} + \dot{U}/R_E} = \frac{1}{-(1 + \beta_2)(1 + \beta_1) \dot{I}_{b1}/\dot{U} + 1/R_E} \\ &= \frac{1}{\frac{(1 + \beta_2)(1 + \beta_1)}{r_{be1} + (1 + \beta_1) r_{be2}} + 1/R_E} \end{aligned}$$