

模拟电子技术基础

Analog Device

5 Frequency response of amplifier circuits 放大电路的频率响应

陈晓龙 Chen, Xiaolong

Department of Electrical and Electronic Engineering

5.0 Fundamentals of complex numbers

A , B , and C are complex numbers 复数: $A = \frac{B}{C}$

The amplitude of A : $|A| = \frac{|B|}{|C|}$


A can also be expressed as: $A = |A|e^{j\varphi}$

If $A=a+jb$ (a is real number 实数 and jb 虚数 is imaginary number), A can also be expressed as:

$$\left\{ \begin{array}{l} \text{Amplitude: } |A| = \sqrt{a^2 + b^2} \\ \text{Phase: } \varphi = \arctan\left(\frac{b}{a}\right) \end{array} \right.$$

5.1 Fundamental of frequency response

High frequency pass circuit 高通电路

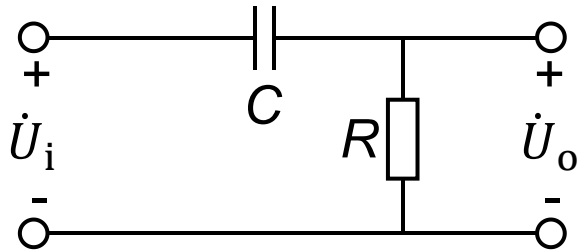

$$\dot{A}_u = |\dot{A}_u| e^{j\varphi}$$

$$|\dot{A}_u| = \frac{\frac{f}{f_L}}{\sqrt{1 + \frac{f^2}{f_L^2}}}$$


$$\varphi = 90^\circ - \arctan \frac{f}{f_L}$$

$$\dot{U}_o = \frac{R}{R + \frac{1}{j\omega C}} \dot{U}_i$$

$$\dot{A}_u = \frac{\dot{U}_o}{\dot{U}_i} = \frac{1}{1 + \frac{1}{j\omega RC}} = \frac{1}{1 + \frac{\omega_L}{j\omega}}, \quad \omega_L = \frac{1}{RC}$$

$$\dot{A}_u = \frac{\frac{f^2}{f_L^2}}{1 + \frac{f^2}{f_L^2}} + j \frac{\frac{f}{f_L}}{1 + \frac{f^2}{f_L^2}}, \quad f = \frac{\omega}{2\pi}, \quad f_L = \frac{\omega_L}{2\pi}$$

High frequency pass circuit 高通电路

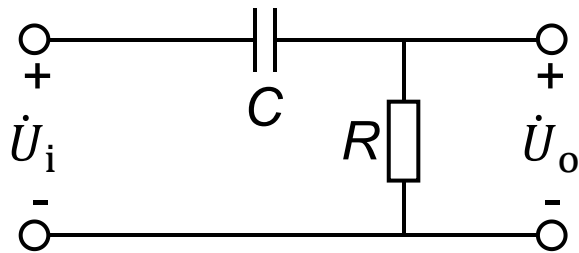

$$\dot{A}_u = |\dot{A}_u|e^{j\varphi}$$

Amplitude frequency characteristic


幅频特性

$$|\dot{A}_u| = \frac{\frac{f}{f_L}}{\sqrt{1 + \frac{f^2}{f_L^2}}}$$


Phase frequency characteristic

相频特性
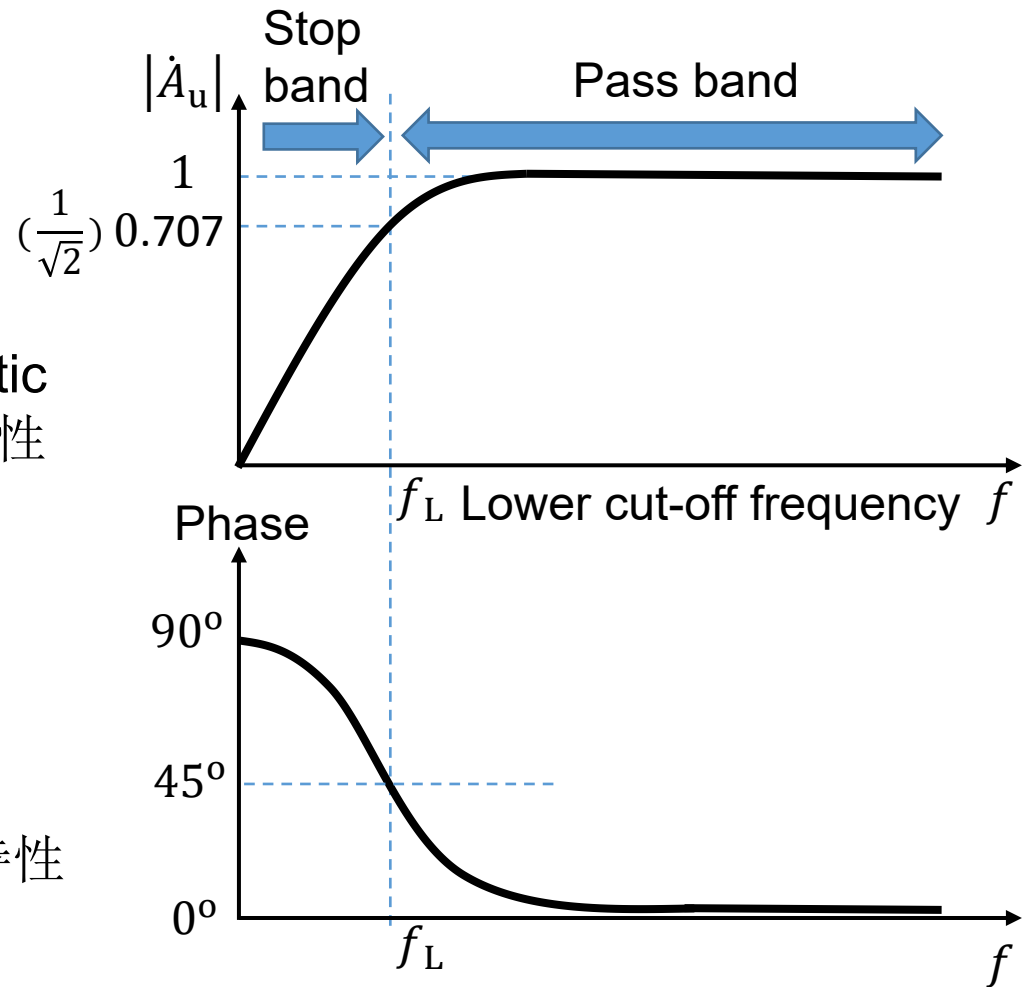
$$\varphi = 90^\circ - \arctan \frac{f}{f_L}$$



Low frequency pass circuit 低通电路

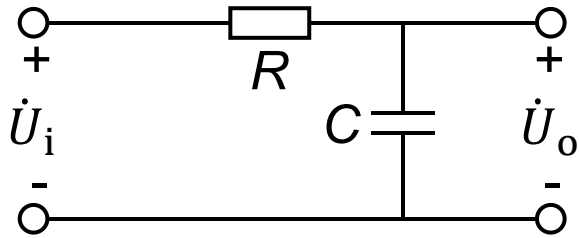



$$\dot{U}_o = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \dot{U}_i \quad \dot{A}_u = |\dot{A}_u| e^{i\varphi}$$

Amplitude frequency characteristic
幅频特性


$$|\dot{A}_u| = \frac{1}{\sqrt{1 + \frac{f^2}{f_H^2}}}, \quad f_H = \frac{1}{2\pi RC}$$

Phase frequency characteristic
相频特性


$$\varphi = -\arctan \frac{f}{f_H}$$

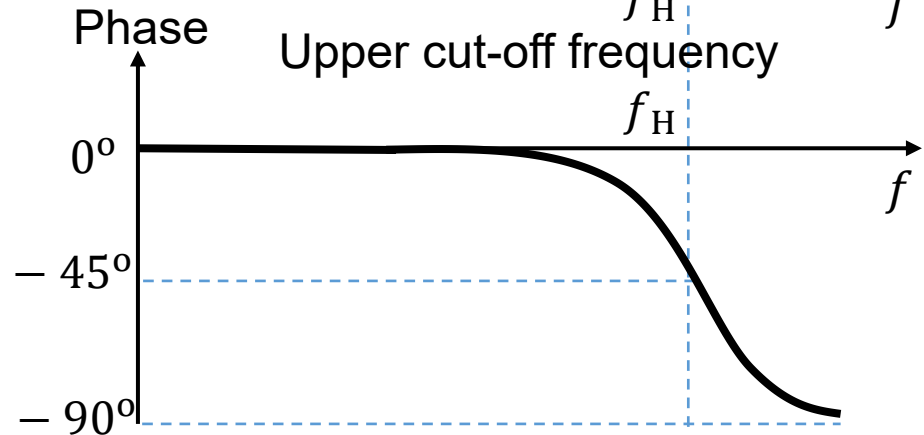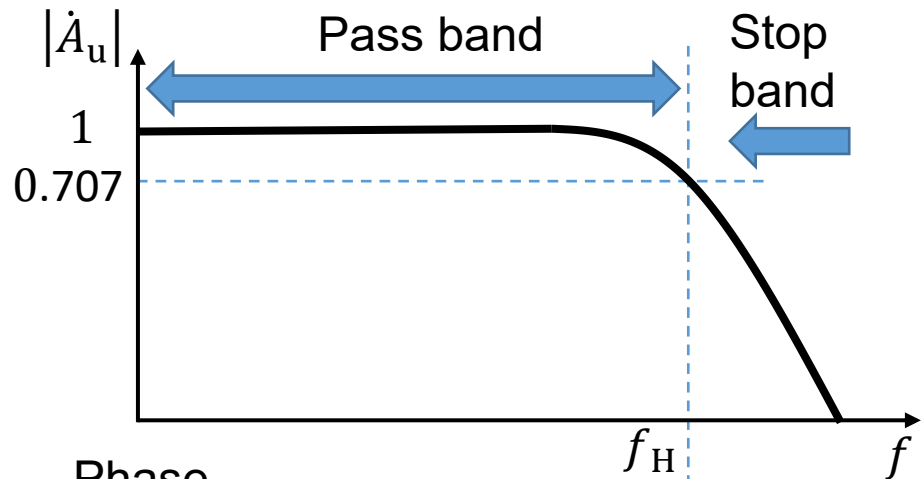

Bandwidth in amplifier circuit

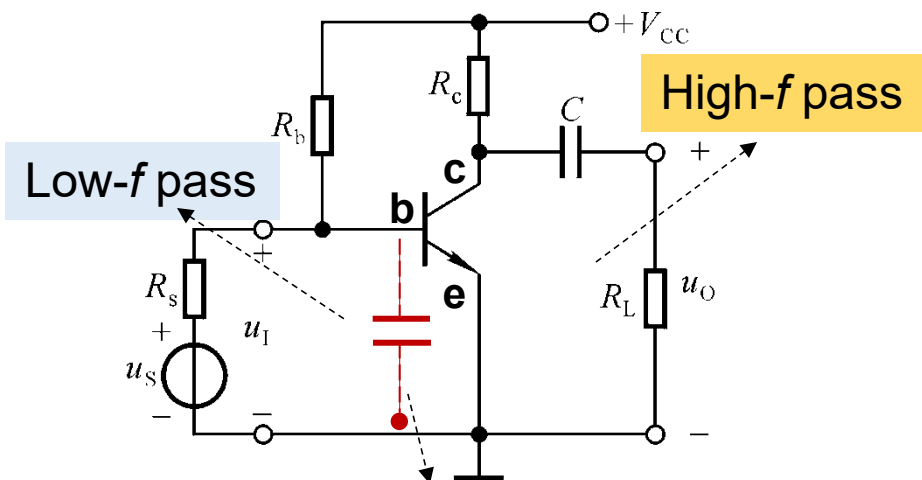



BE junction capacitor 结电容

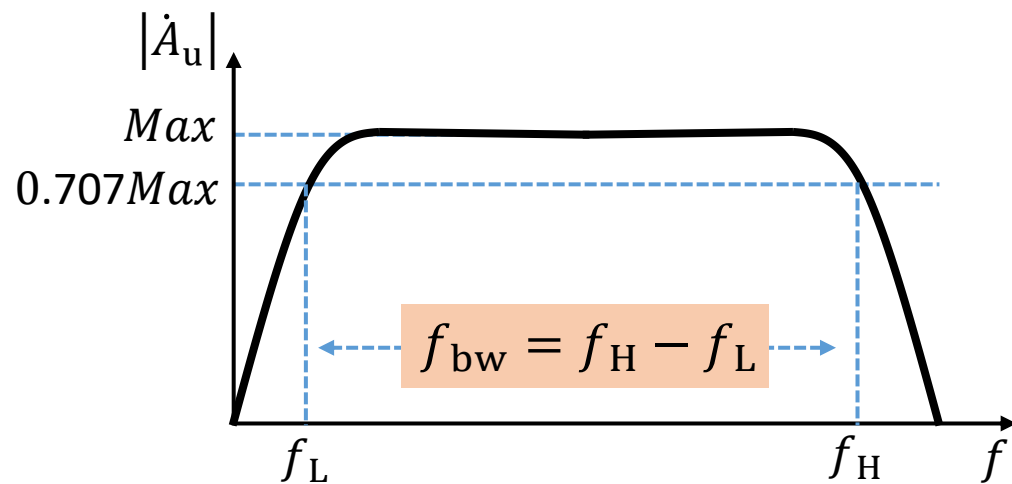


f_{bw} : bandwidth 通频带、带宽

5.2 The high frequency model of transistor


Hybrid - π model 混合 π 模型

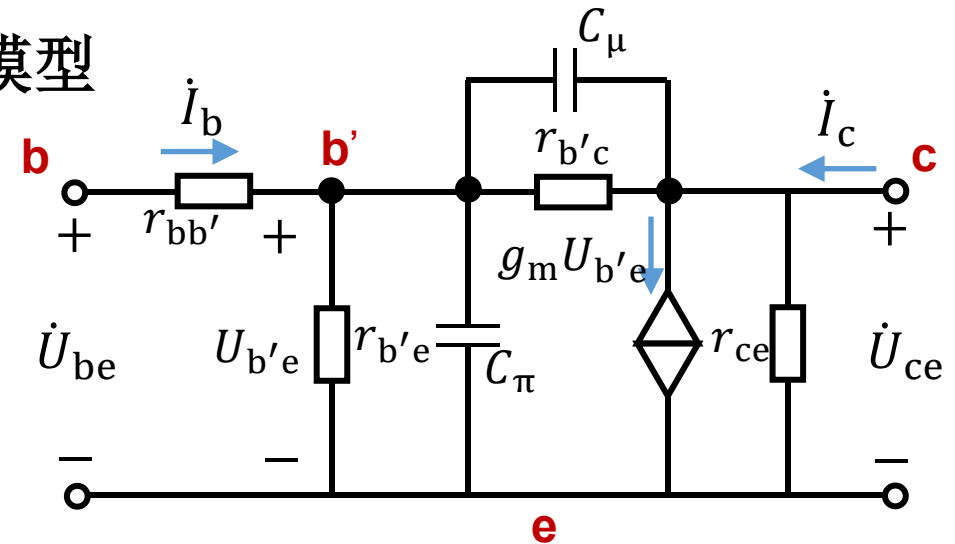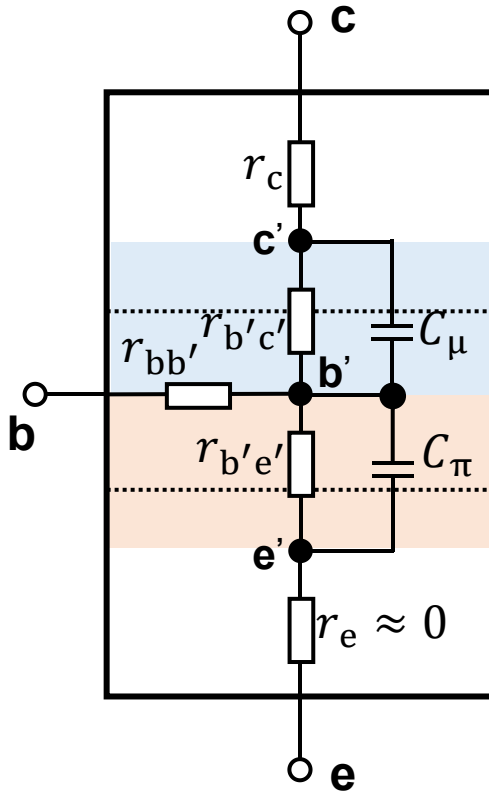


$r_{b'c}, r_{ce}$ are very large

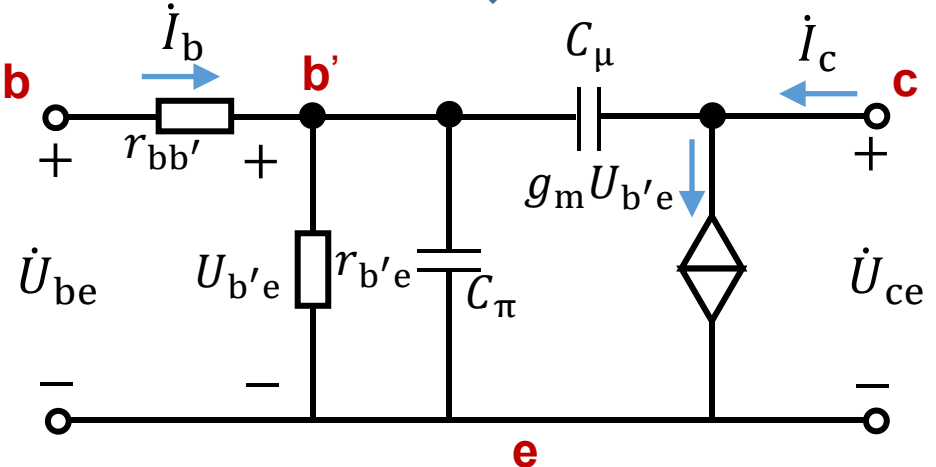

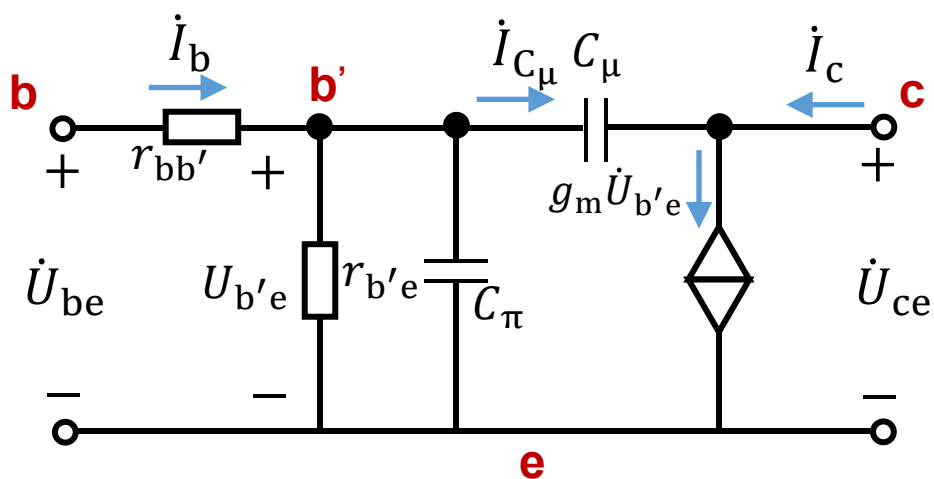Unilateralization of hybrid - π model 混合 π 模型单向化




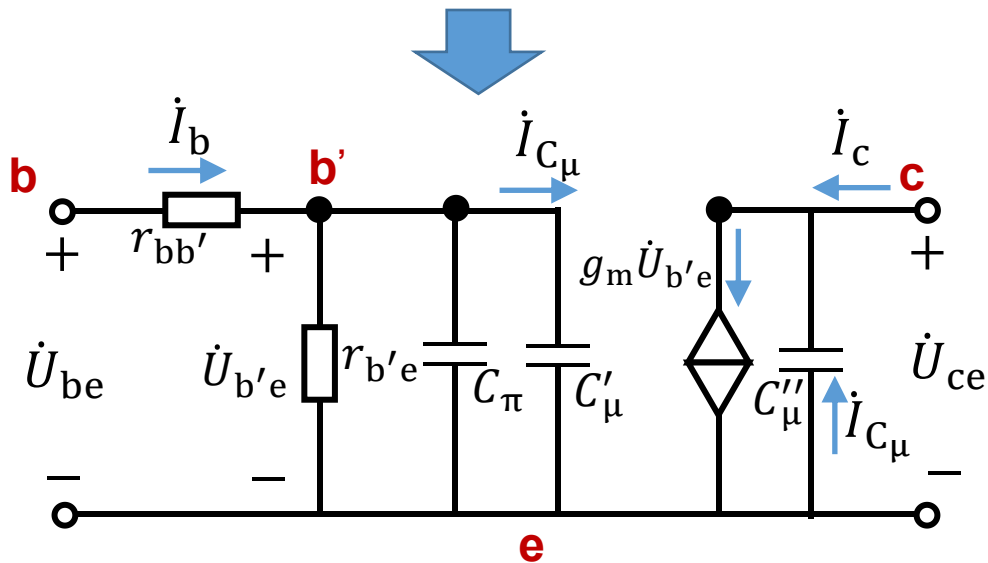
$$\left\{ \begin{array}{l} \dot{I}_{C_{\mu}} = \frac{\dot{U}_{b'e} - \dot{U}_{ce}}{X_{C_{\mu}}} \quad , \dot{K} = \frac{\dot{U}_{ce}}{\dot{U}_{b'e}} \\ \dot{I}_{C_{\mu}} = \frac{\dot{U}_{b'e}}{X_{C'_{\mu}}} \\ \dot{I}_{C_{\mu}} = - \frac{\dot{U}_{ce}}{X_{C''_{\mu}}} \end{array} \right.$$





$$\left\{ \begin{array}{l} X_{C'_\mu} = \frac{X_{C_\mu}}{(1 - \dot{K})} \\ X_{C''_\mu} = \frac{\dot{K}}{(\dot{K} - 1)} X_{C_\mu} \end{array} \right.$$

$$\left\{ \begin{array}{l} C'_\mu = (1 - \dot{K})C_\mu \\ C''_\mu = \frac{\dot{K} - 1}{\dot{K}}C_\mu \end{array} \right.$$

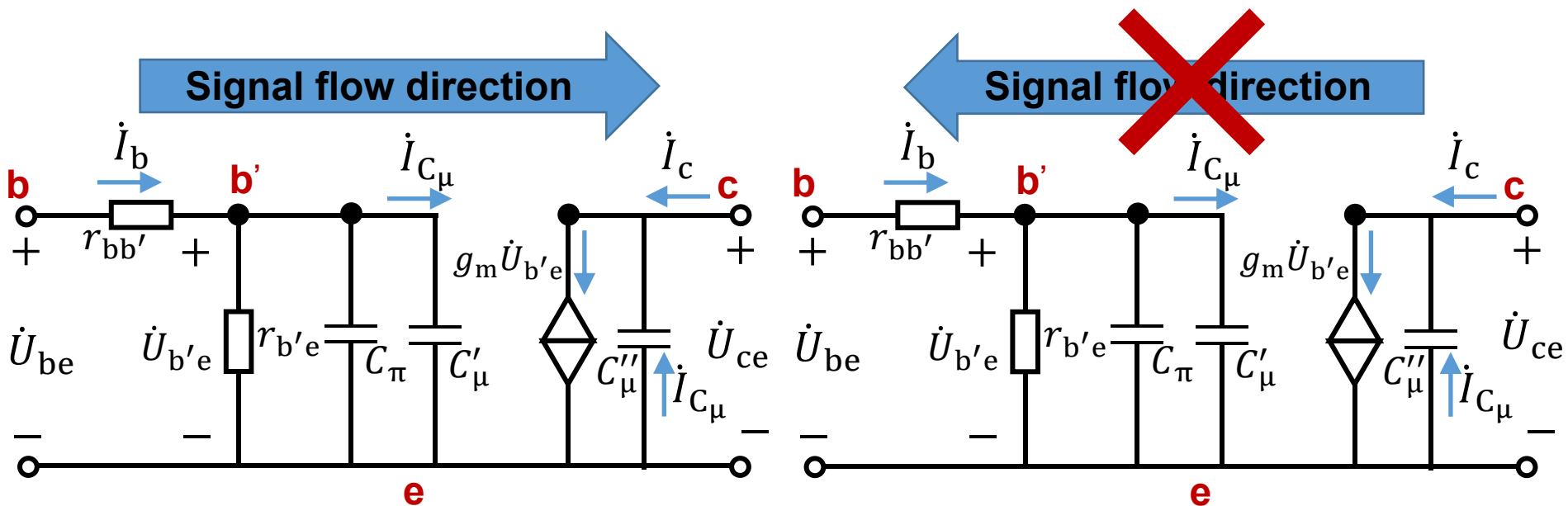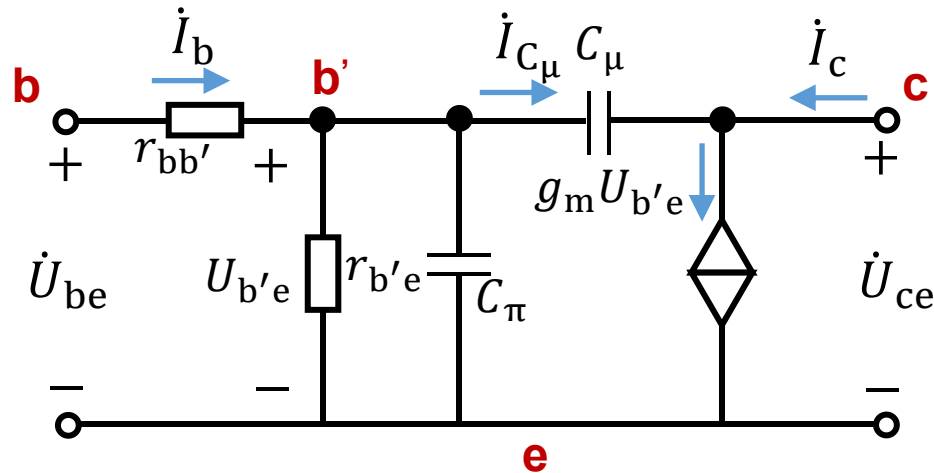
Unilateralization of hybrid - π model 混合 π 模型单向化



Simplified hybrid - π model 简化混合 π 模型

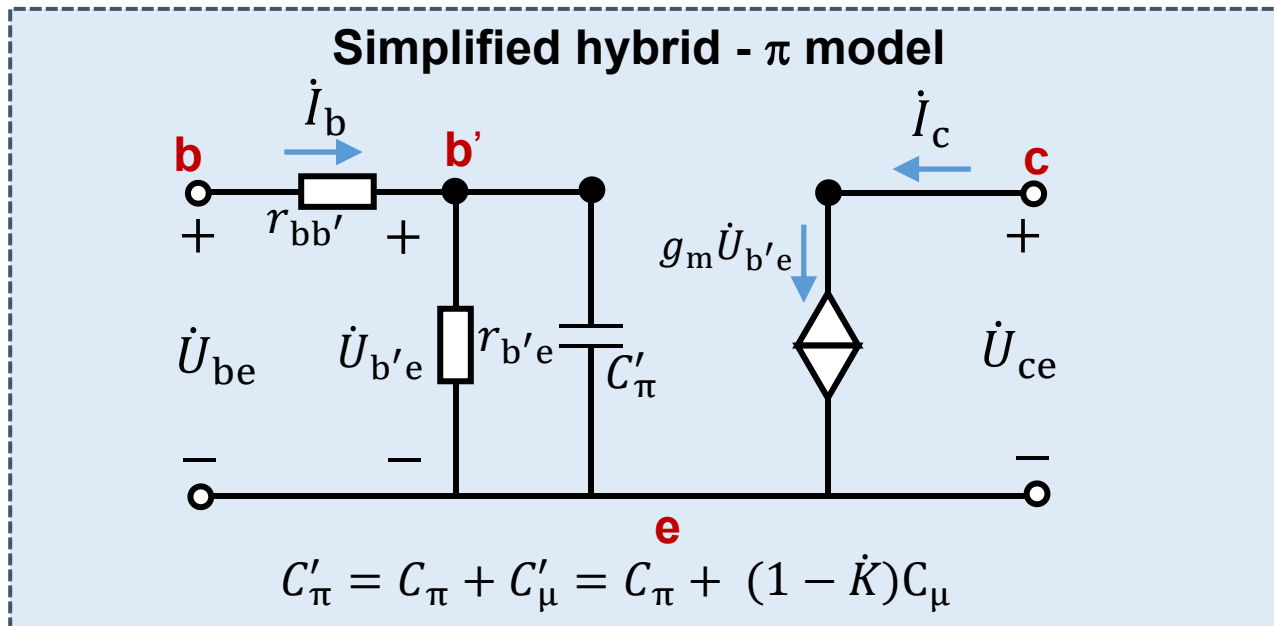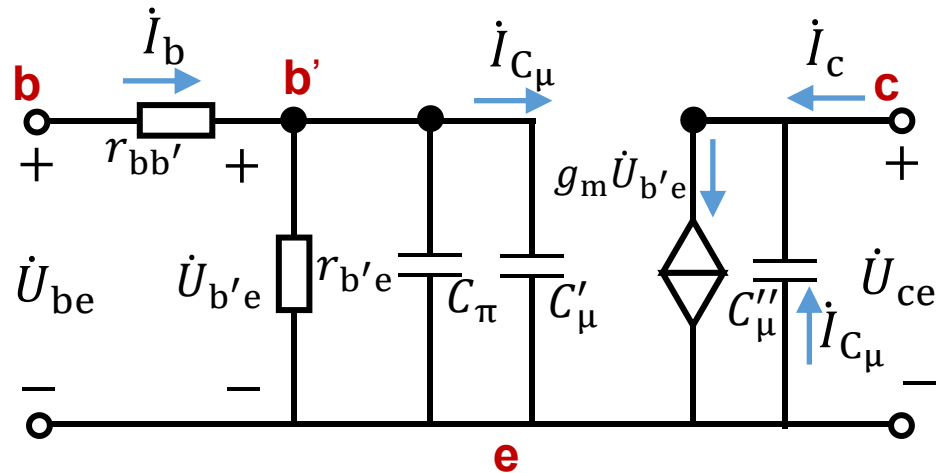

Simplified hybrid - π model

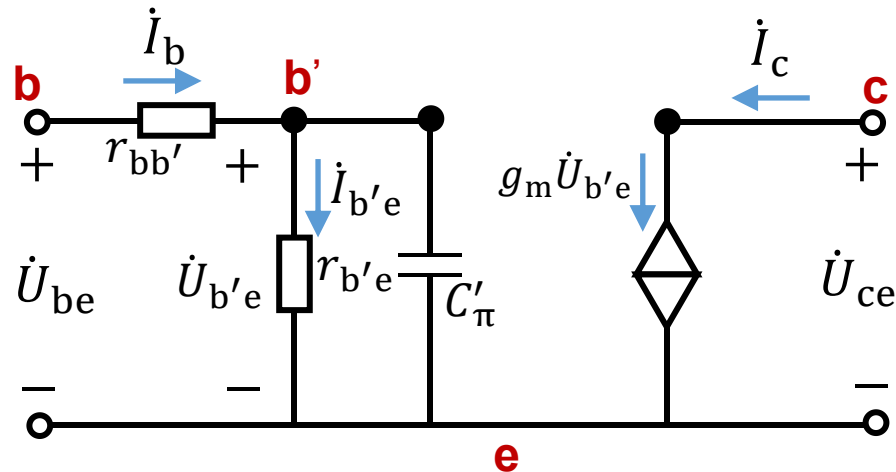

$$r_{b'e} = \beta_0 \frac{U_T}{|I_{CQ}|}, U_T = 26\text{mV}$$

β_0 : current gain at low frequency


$$C'_\pi = C_\pi + C'_\mu = C_\pi + (1 - \dot{K})C_\mu$$

$r_{bb'}$, C_μ are known How to get C_π ?

$$\begin{cases} \dot{I}_c = g_m \dot{U}_{b'e} = \beta_0 \dot{I}_{b'e} \\ \dot{U}_{b'e} = \dot{I}_{b'e} r_{b'e} \end{cases}$$

$$g_m = \frac{\beta_0}{r_{b'e}} \approx \frac{I_{CQ}}{U_T}$$

Simplified hybrid - π model

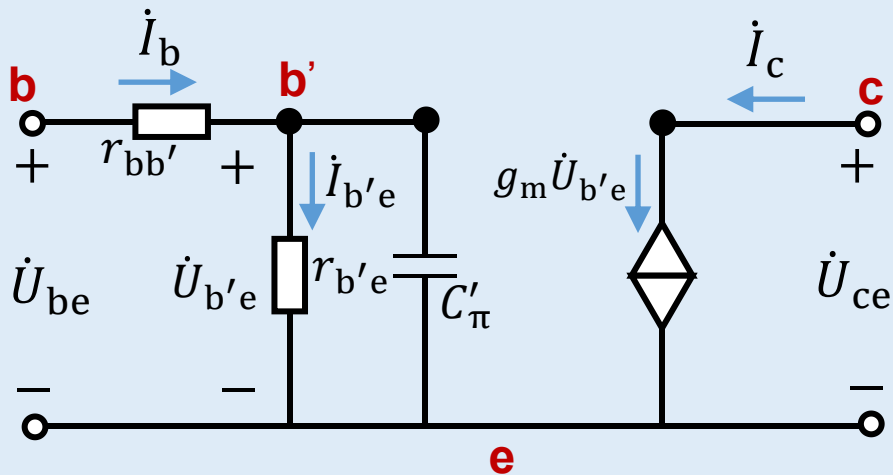


$$r_{b'e} = \beta_0 \frac{U_T}{|I_{CQ}|}, U_T = 26\text{mV}$$

$$C'_\pi = C_\pi + (1 - \dot{K})C_\mu$$

$$g_m = \frac{\beta_0}{r_{b'e}} \approx \frac{I_{CQ}}{U_T}$$

$$i_c = g_m U_{b'e} = \beta_0 i_{b'e}$$

Simplified h -model

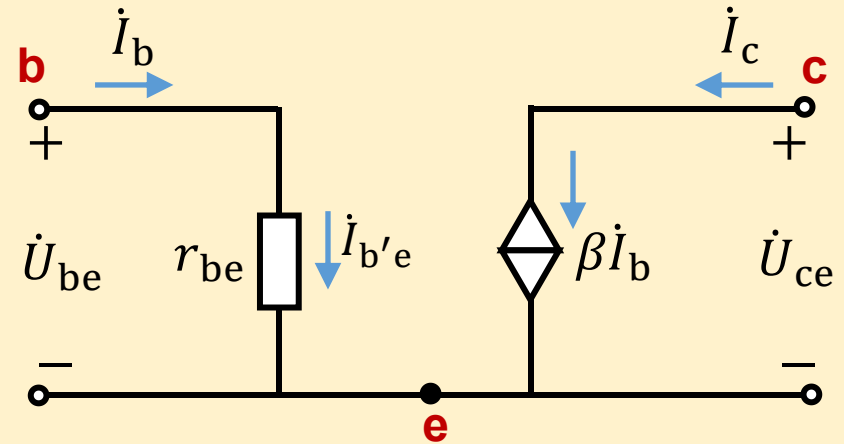

$$r_{be} = r_{bb'} + \beta_0 \frac{U_T}{|I_{CQ}|}$$

$$\beta_0 = \frac{i_c}{i_b}$$

$$i_c = \beta_0 i_b$$

5.3 Current amplification factor at high frequency


The current amplification factor is defined as

$$\dot{\beta} = \frac{\dot{I}_c}{\dot{I}_b} \bigg|_{U_{CE} = \text{constant}}$$

$$\because \dot{K} = 0,$$

$$\therefore C'_\pi = C_\pi + (1 - \dot{K})C_\mu = C_\pi + C_\mu$$
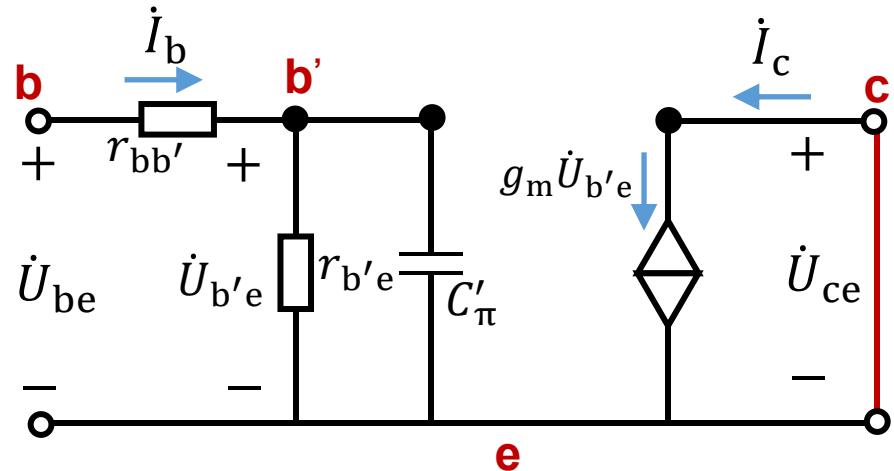
$$\begin{cases} \dot{I}_c = g_m \dot{U}_{b'e} = \frac{\beta_0}{r_{b'e}} \dot{U}_{b'e} \\ \dot{I}_b = \frac{\dot{U}_{b'e}}{r_{bb'}} + \frac{\dot{U}_{b'e}}{\frac{1}{j\omega C'_\pi}} \end{cases}$$



$$\Rightarrow \dot{\beta} = \frac{\beta_0}{1 + j\omega r_{b'e} C'_\pi}$$

$$\dot{\beta} = \frac{\beta_0}{1 + j \frac{f}{f_\beta}}, f = \frac{\omega}{2\pi}, f_\beta = \frac{\omega_\beta}{2\pi} = \frac{1}{2\pi r_{b'e} C'_\pi}$$

f_β : common-e cut-off frequency 共射截止频率


The amplitude and phase frequency characteristics of $\dot{\beta}$

$$|\dot{\beta}| = \frac{\beta_0}{\sqrt{1 + \frac{f^2}{f_\beta^2}}}$$

$$\varphi = -\arctan \frac{f}{f_\beta}$$

$$f_\beta = \frac{1}{2\pi r_{b'e} C'_\pi}$$
$$= \frac{1}{2\pi r_{b'e} (C_\pi + C_\mu)}$$

We can get C_π from f_β !

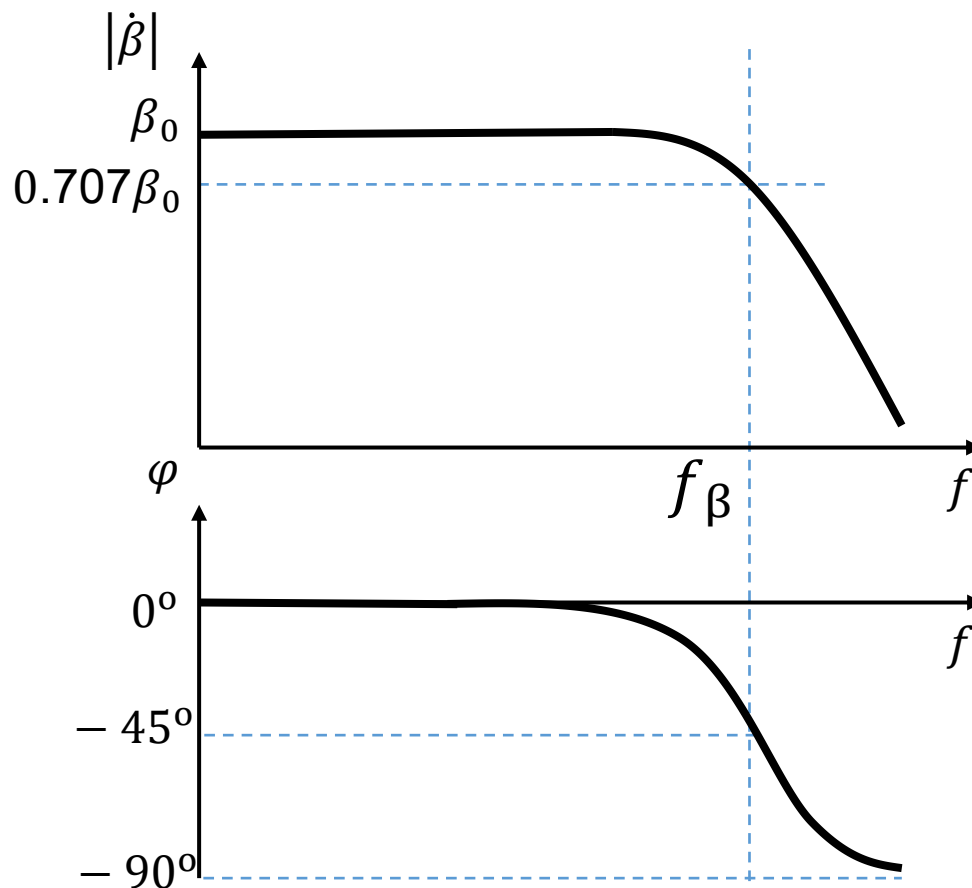

Bode plot of $\dot{\beta}$ 波特图

Use log scale for $|\dot{\beta}|$ and f 对数坐标

Use dB 分贝 $1\text{dB}=20\lg$


$$20\lg|\dot{\beta}| = 20\lg\beta_0 - 20\lg\sqrt{1 + \frac{f^2}{f_\beta^2}}$$

$20\lg\sqrt{2} \approx 3\text{ dB}$

$$\varphi = -\arctan\frac{f}{f_\beta}$$

$$\because |\dot{\beta}| = 1 \text{ or } 20\lg|\dot{\beta}| = 0, f = f_T$$
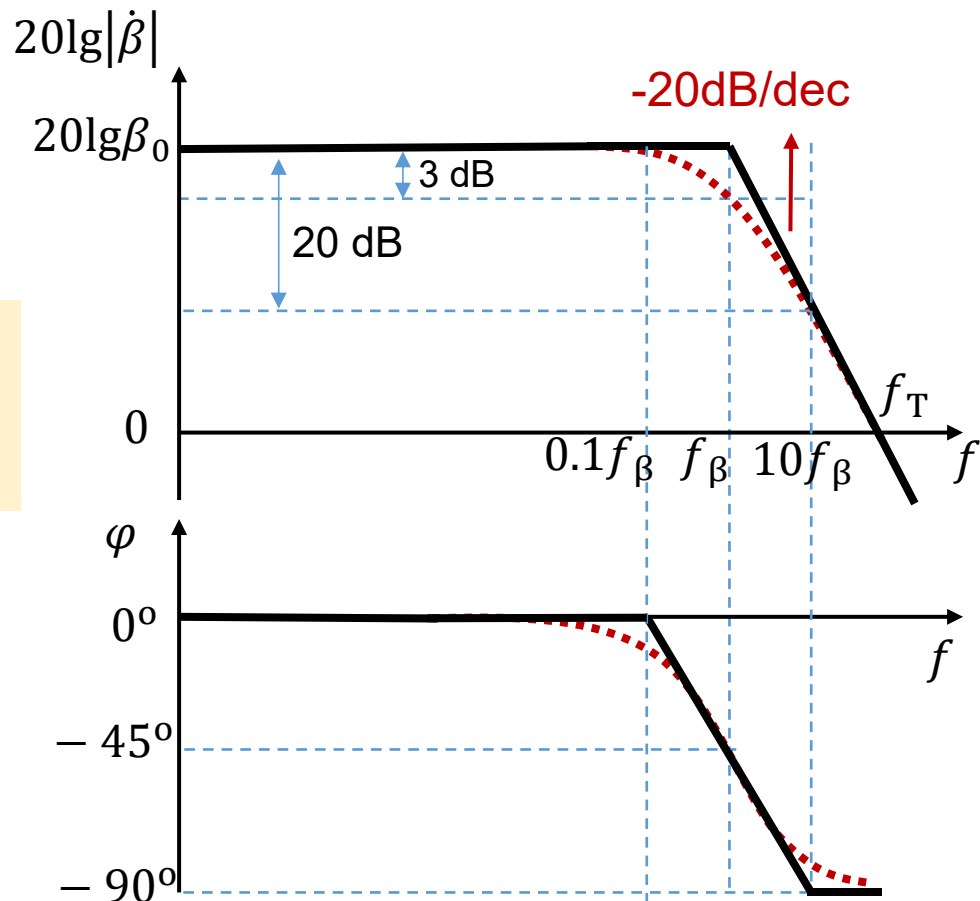
$$\therefore f_T \approx \beta_0 f_\beta$$



The common-base current amplification factor $\dot{\alpha}$

$$\dot{\alpha} = \frac{\dot{\beta}}{1 + \dot{\beta}}, \quad \dot{\beta} = \frac{\beta_0}{1 + j \frac{f}{f_\beta}}, \quad \dot{\alpha} = \frac{\frac{\beta_0}{1 + \beta_0}}{1 + j \frac{f}{(1 + \beta_0)f_\beta}}$$


$$\dot{\alpha} = \frac{\alpha_0}{1 + j \frac{f}{f_\alpha}}$$

Common-b cut-off frequency 共基极截止频率


$$f_\alpha = (1 + \beta_0)f_\beta$$

Common-b amplifier is more suitable for high frequency amplifier circuit

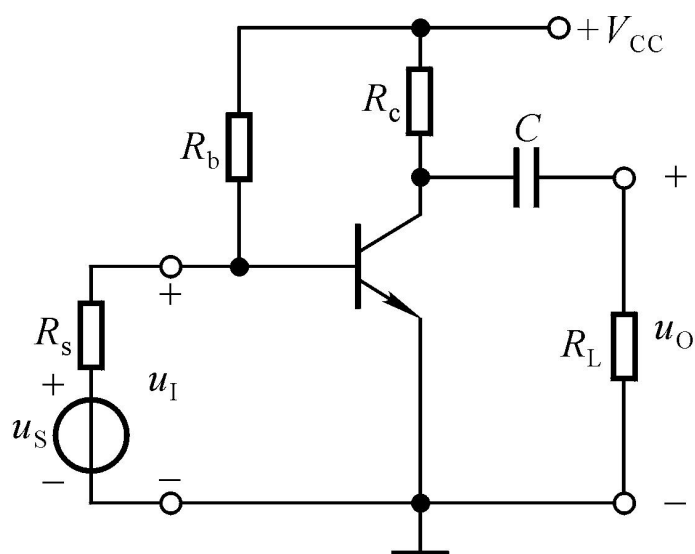5.4 Frequency response of amplifier circuit






The AC circuit for: 0- ∞ Hz

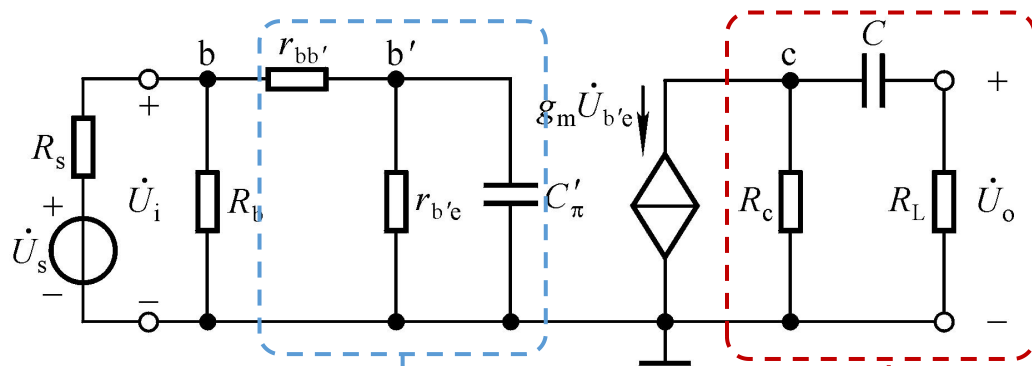

Low frequency pass circuit

High frequency pass circuit

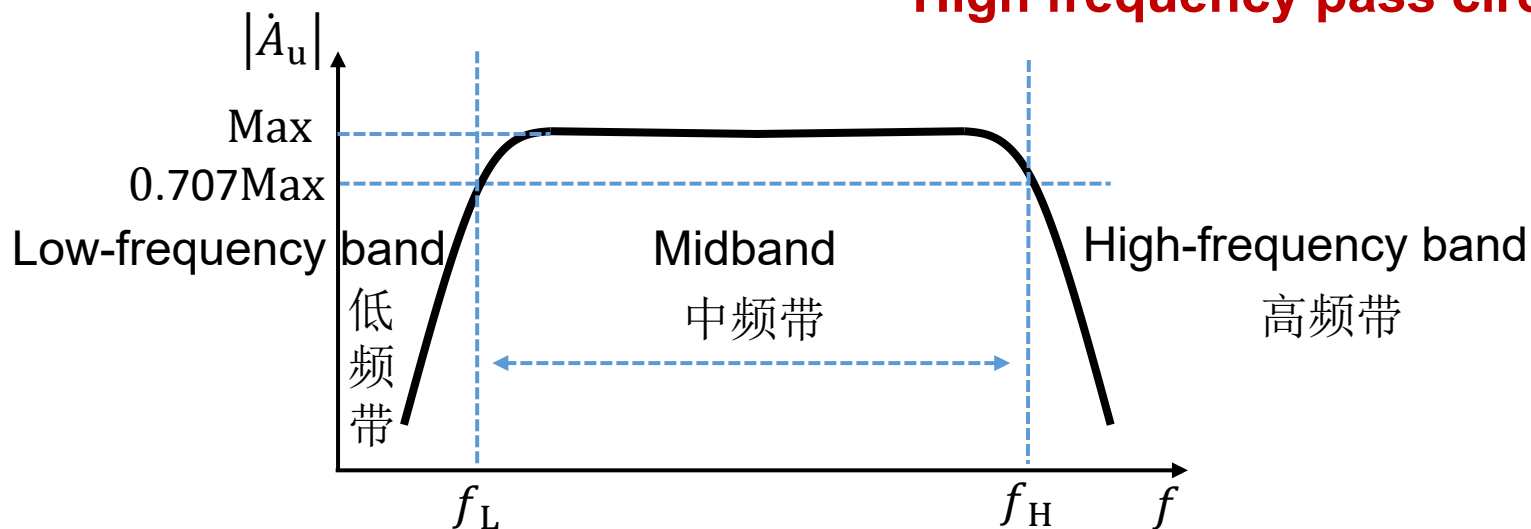


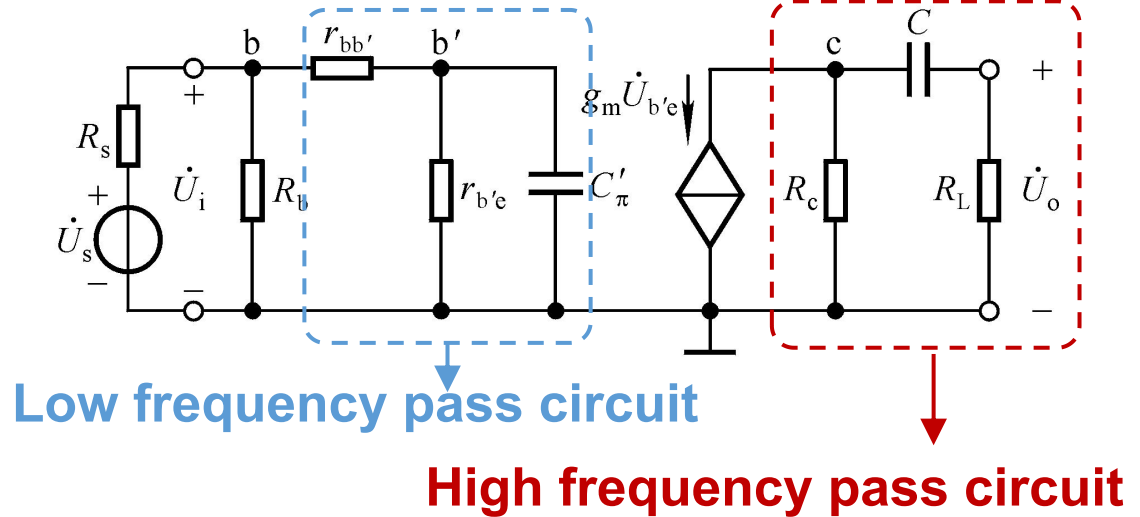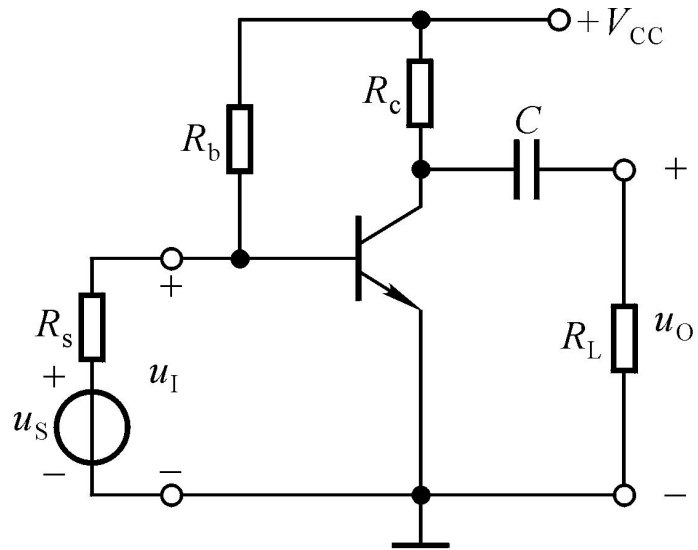

Analyze this circuit in three situations:

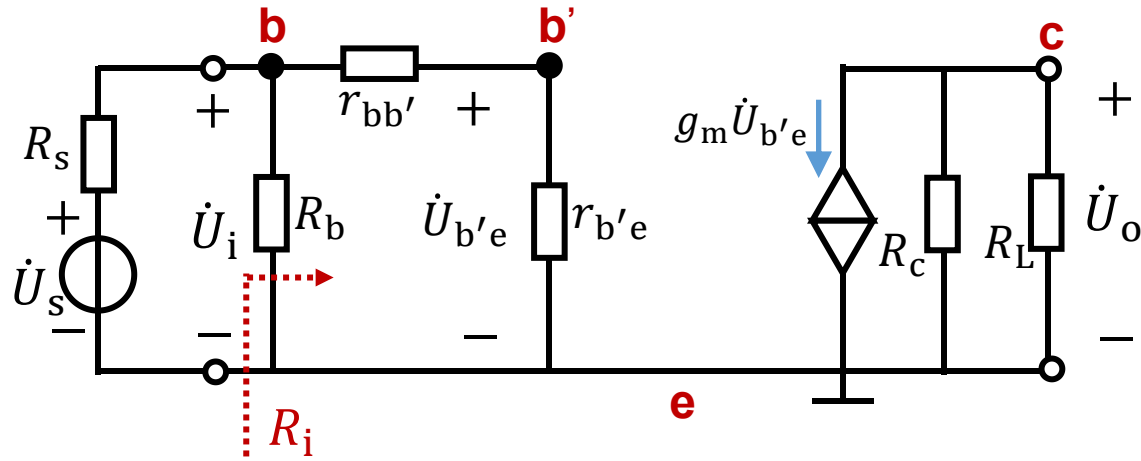- 1) Low frequency: ignore C'_π (open), and consider C
- 2) Medium frequency: ignore C'_π (open), and C (short)
- 3) High frequency: ignore C (short), and consider C'_π


Medium frequency: ignore C'_π (open), and C (short)




$$\dot{A}_{\text{usm}} = \frac{\dot{U}_o}{\dot{U}_s} = \frac{\dot{U}_i}{\dot{U}_s} \cdot \frac{\dot{U}_{b'e}}{\dot{U}_i} \cdot \frac{\dot{U}_o}{\dot{U}_{b'e}} = \frac{R_i}{R_s + R_i} \cdot \frac{r_{b'e}}{r_{be}} \cdot (-g_m R'_L)$$

$$R_i = R_b // r_{be} \quad R'_L = R_c // R_L$$

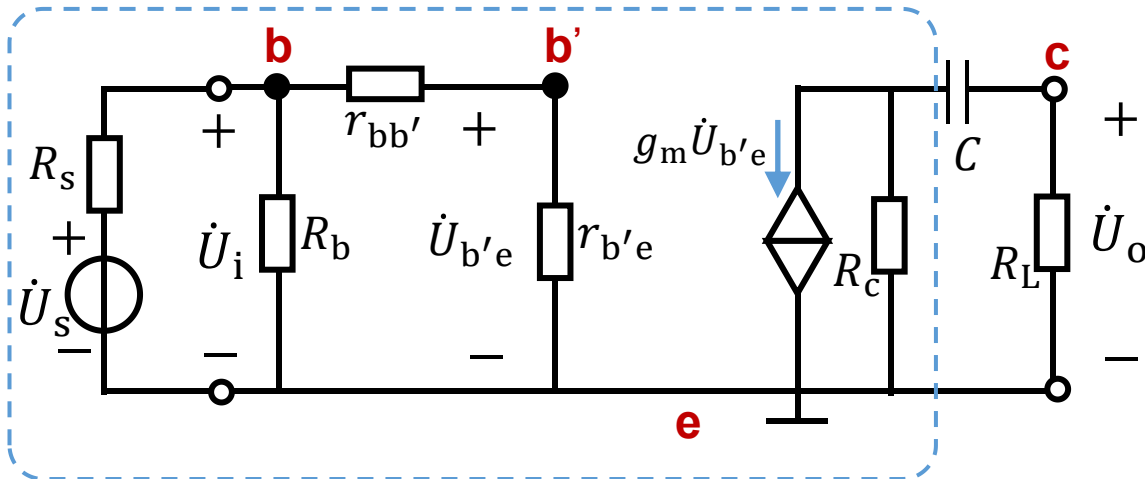
Low frequency: ignore C'_π (open), and consider C



Equivalent circuit

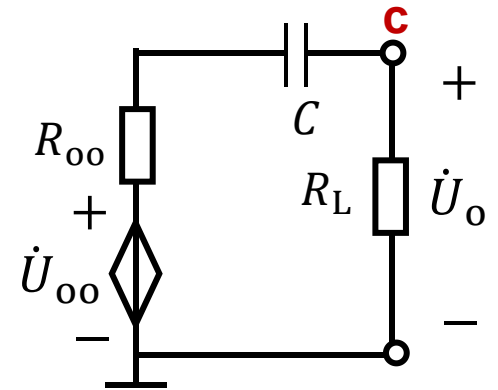

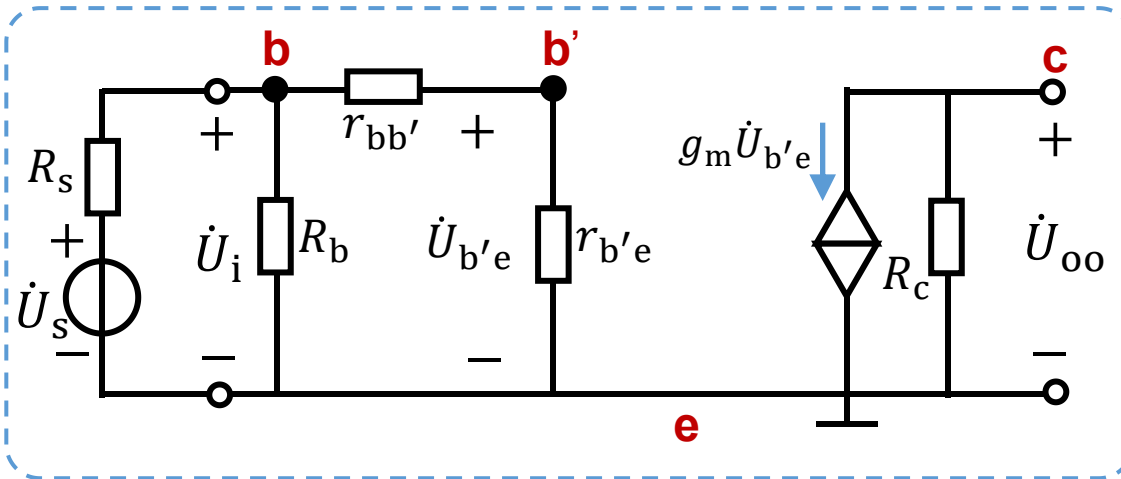
$$\dot{A}_{usl} = \frac{\dot{U}_o}{\dot{U}_s} = \frac{\dot{U}_o}{\dot{U}_{oo}} \frac{\dot{U}_{oo}}{\dot{U}_s}$$




$$\frac{\dot{U}_{oo}}{\dot{U}_s} = \frac{R_i}{R_s + R_i} \cdot \frac{r_{b'e}}{r_{be}} \cdot (-g_m R_c), \quad R_{oo} = R_c$$

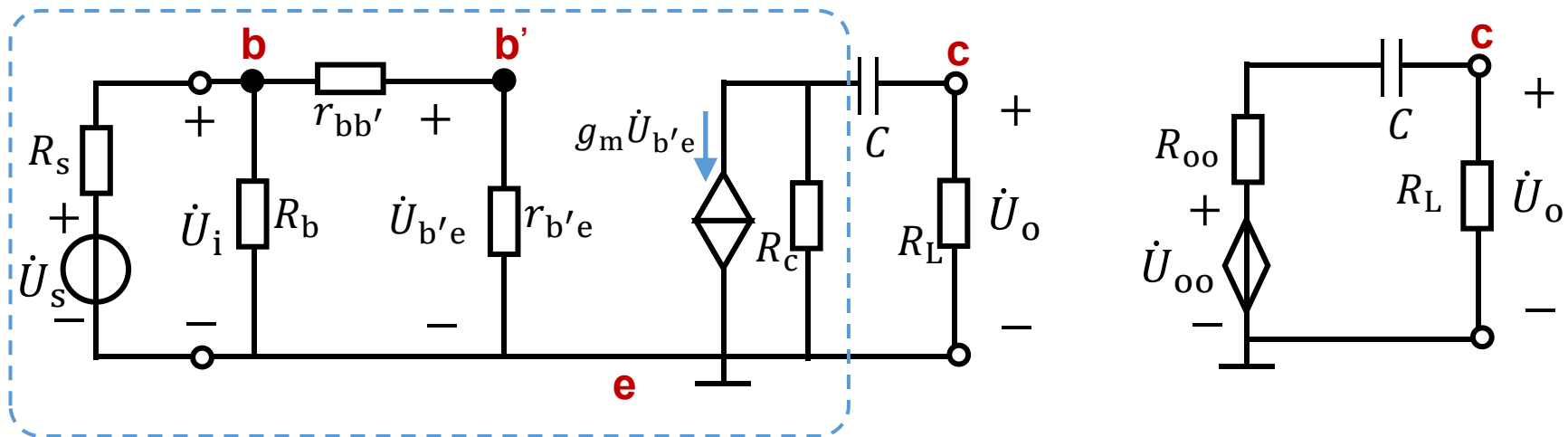Low frequency: ignore C'_π (open), and consider C



$$\begin{aligned}\dot{A}_{usl} &= \frac{\dot{U}_o}{\dot{U}_s} = \frac{\dot{U}_{oo}}{\dot{U}_s} \frac{\dot{U}_o}{\dot{U}_{oo}} = \frac{R_i}{R_s + R_i} \cdot \frac{r_{b'e}}{r_{be}} \cdot (-g_m R_c) \frac{R_L}{R_c + R_L + \frac{1}{j\omega C}} \\ &= \frac{R_i}{R_s + R_i} \cdot \frac{r_{b'e}}{r_{be}} \cdot \left(-g_m \frac{R_c R_L}{R_c + R_L} \right) \frac{1}{1 + \frac{1}{j\omega(R_c + R_L)C}}\end{aligned}$$

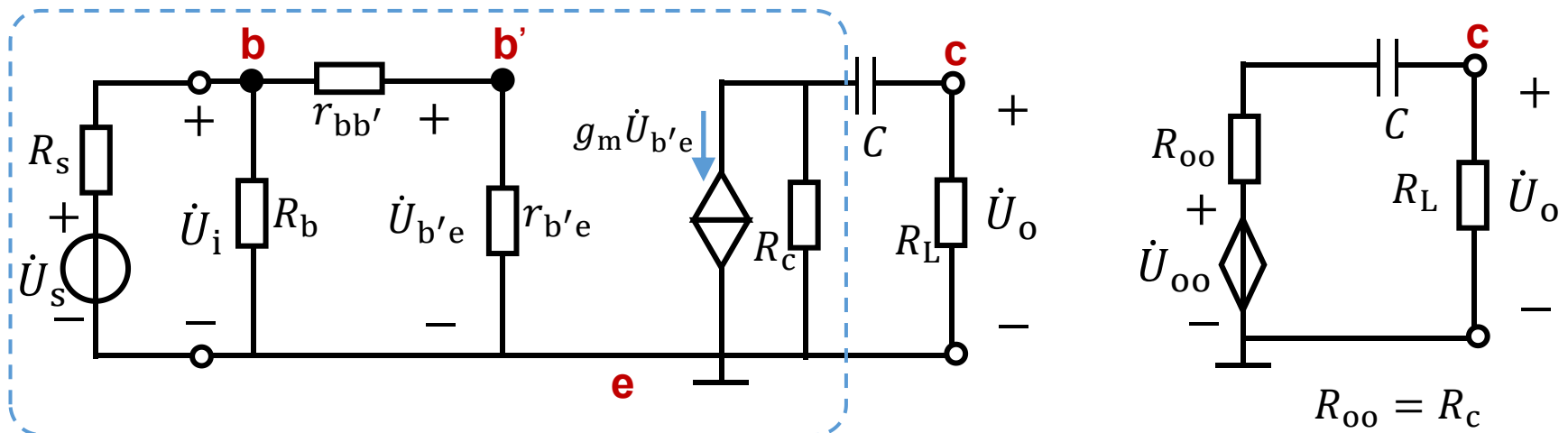Low frequency: ignore C'_π (open), and consider C




$$\dot{A}_{usl} = \frac{\dot{U}_o}{\dot{U}_s} = \frac{R_i}{R_s + R_i} \cdot \frac{r_{b'e}}{r_{be}} \cdot \left(-g_m \frac{R_c R_L}{R_c + R_L} \right) \frac{1}{1 + \frac{1}{j\omega(R_c + R_L)C}}$$

$$= \frac{R_i}{R_s + R_i} \cdot \frac{r_{b'e}}{r_{be}} \cdot (-g_m R'_L) \frac{j^f / f_L}{1 + j^f / f_L}$$

$$R'_L = \frac{R_c R_L}{R_c + R_L}$$

$$f_L = \frac{1}{2\pi(R_c + R_L)C}$$

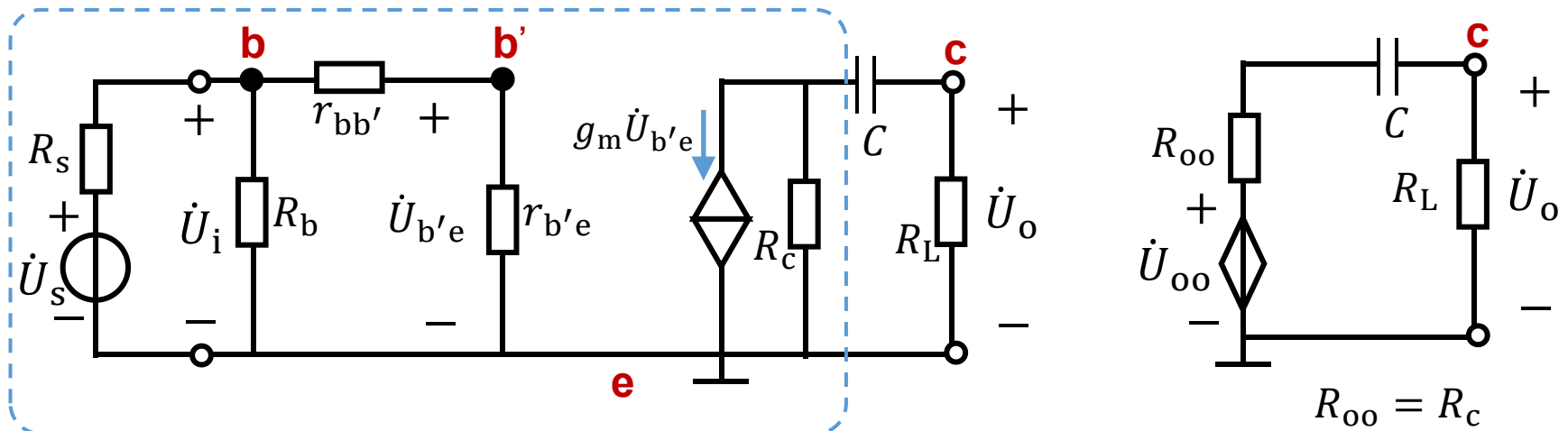Low frequency: ignore C'_π (open), and consider C




$$\dot{A}_{usl} = \frac{\dot{U}_o}{\dot{U}_s} = \underbrace{\frac{R_i}{R_s + R_i} \cdot \frac{r_{b'e}}{r_{be}} \cdot (-g_m R'_L)}_{\dot{A}_{usm}} \underbrace{\frac{j^f / f_L}{1 + j^f / f_L}}_{\text{High pass}}$$

$$\dot{A}_{usl} = \dot{A}_{usm} \frac{j^f / f_L}{1 + j^f / f_L}$$




Low frequency: Amplitude and phase frequency characteristics

$$20\lg|\dot{A}_{usl}| = 20\lg|\dot{A}_{usm}| + 20\lg \frac{\frac{f}{f_L}}{\sqrt{1 + \frac{f^2}{f_L^2}}}$$

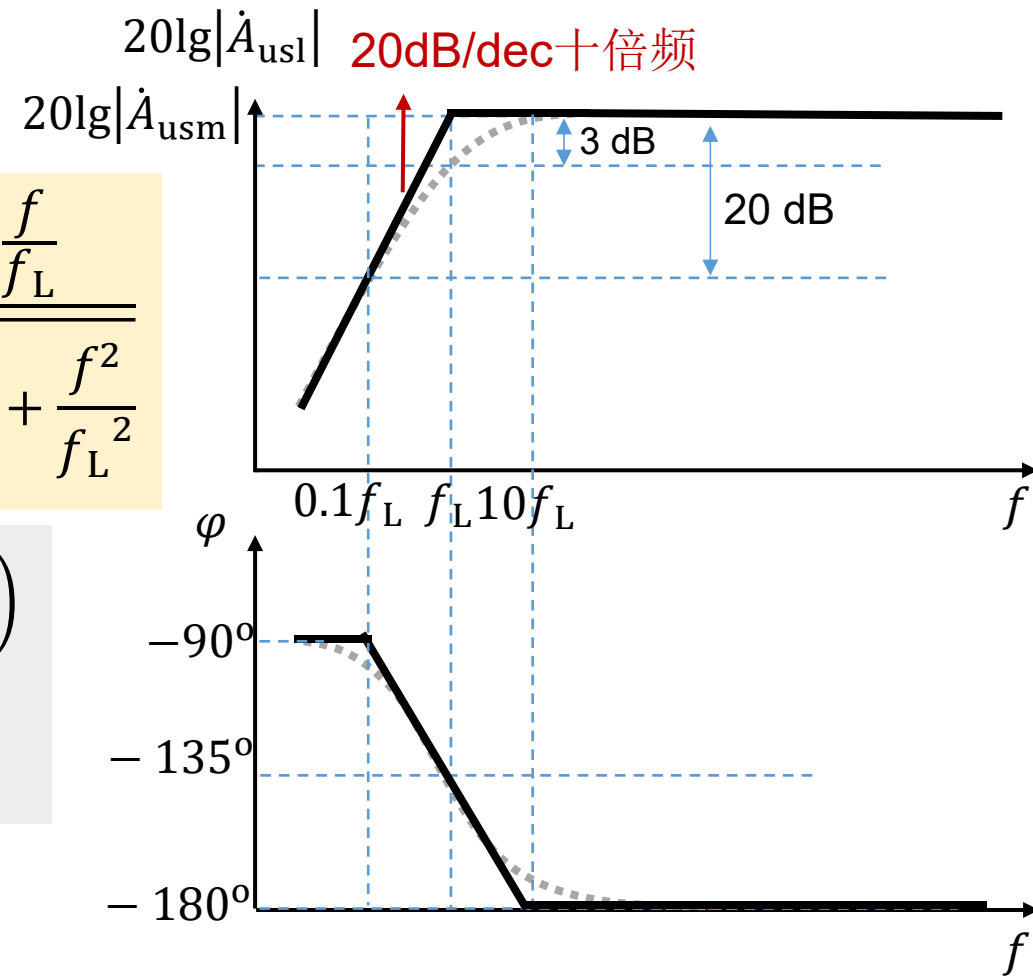
$$\begin{aligned}\varphi &= -180^\circ + \left(90^\circ - \arctan \frac{f}{f_L}\right) \\ &= -90^\circ - \arctan \frac{f}{f_L}\end{aligned}$$



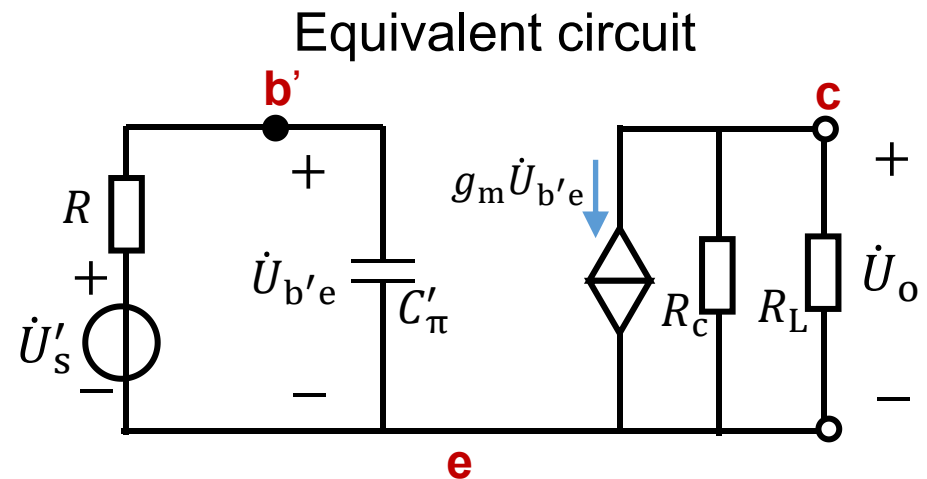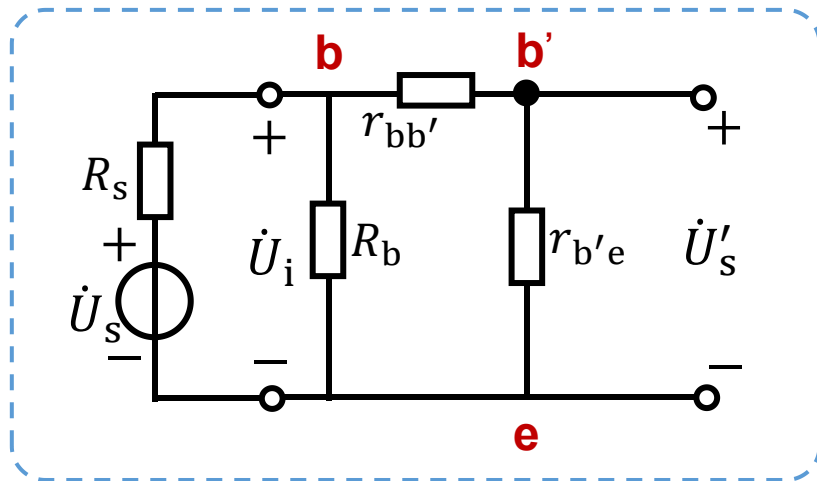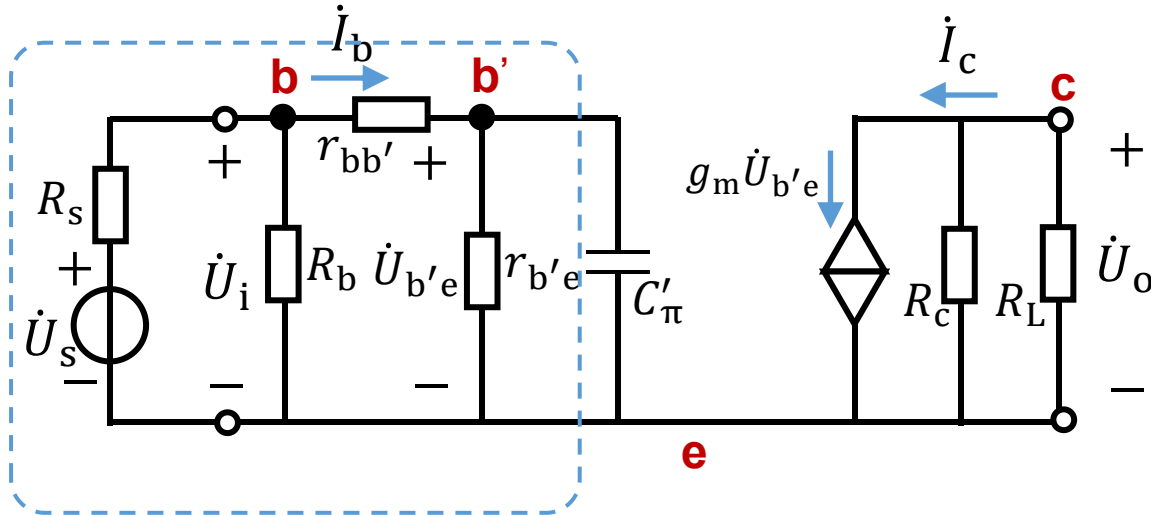High frequency: ignore C (short), and consider C'_π (open)




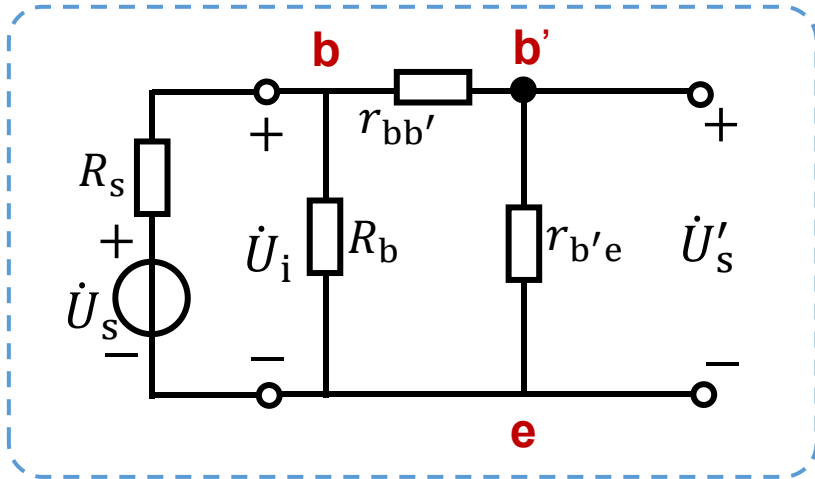High frequency: ignore C (short) , and consider C'_π (open)



$$\dot{U}'_s = \frac{R_i}{R_s + R_i} \cdot \frac{r_{b'e}}{r_{be}} \cdot \dot{U}_s$$


$$R_i = R_b // r_{be}$$

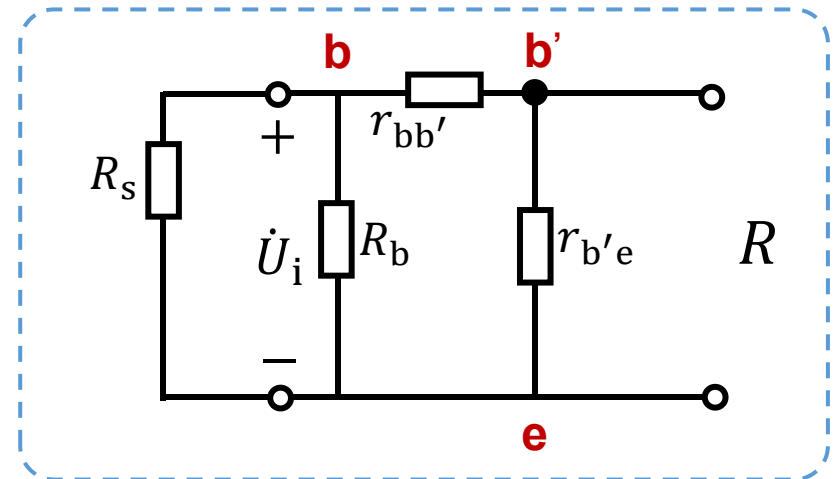

$$R = r_{b'e} // (r_{bb'} + R_s // R_b)$$

High frequency: ignore C (short) , and consider C'_π (open)

Equivalent circuit

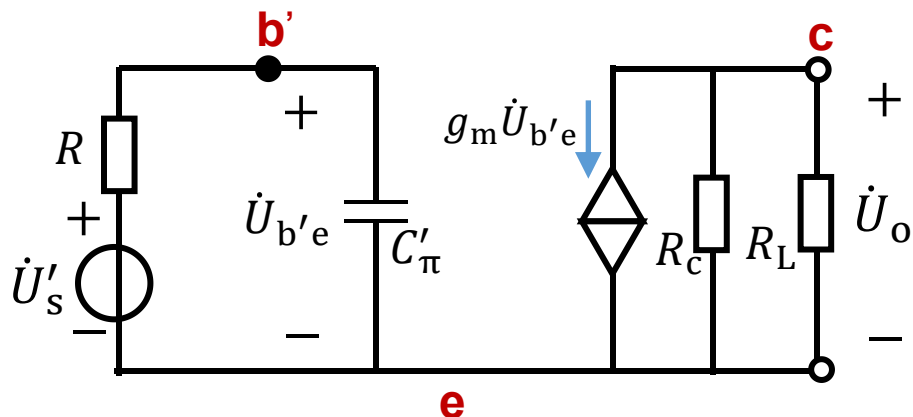

$$\left\{ \begin{array}{l} \dot{U}'_s = \frac{R_i}{R_s + R_i} \cdot \frac{r_{b'e}}{r_{be}} \cdot \dot{U}_s \\ R = r_{b'e} // (r_{bb'} + R_s // R_b) \end{array} \right.$$


$$\begin{aligned} \dot{A}_{ush} &= \frac{\dot{U}_o}{\dot{U}_s} = \frac{\dot{U}'_s}{\dot{U}_s} \cdot \frac{\dot{U}_o}{\dot{U}'_s} = \frac{R_i}{R_s + R_i} \cdot \frac{r_{b'e}}{r_{be}} \cdot \frac{\dot{U}_o}{\dot{U}'_s} \\ &= \frac{R_i}{R_s + R_i} \cdot \frac{r_{b'e}}{r_{be}} \cdot \frac{1/j\omega RC'_\pi}{1 + 1/j\omega RC'_\pi} \cdot (-g_m R'_L) \end{aligned}$$

$$\left\{ \begin{array}{l} \dot{U}_o = (-g_m \dot{U}_{b'e}) R'_L \\ \dot{U}_{b'e} = \frac{1/j\omega C'_\pi}{R + 1/j\omega C'_\pi} \dot{U}'_s \end{array} \right.$$

$$= \frac{R_i}{R_s + R_i} \cdot \frac{r_{b'e}}{r_{be}} \cdot (-g_m R'_L) \frac{1}{1 + jf/f_H}, f_H = \frac{1}{2\pi RC'_\pi} \quad C'_\pi = C_\pi + (1 - \dot{K})C_\mu$$

High frequency: ignore C (short) , and consider C'_π (open)

Equivalent circuit

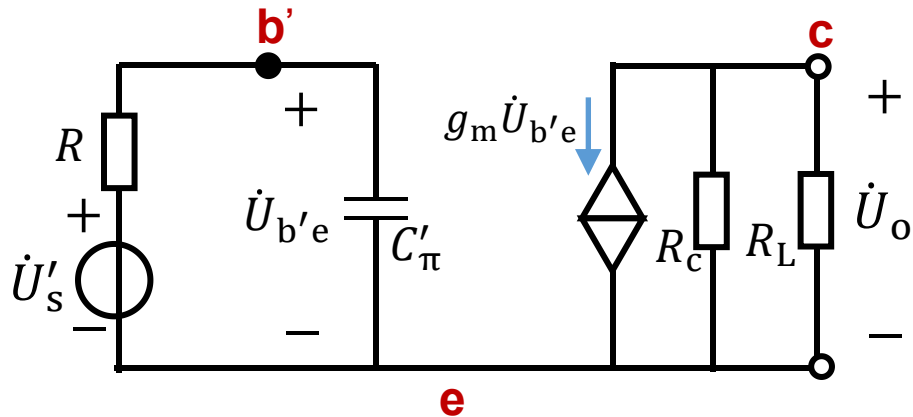

$$f_H = \frac{1}{2\pi R C'_\pi}$$

$$R = r_{b'e} // (r_{bb'} + R_s // R_b)$$

$$C'_\pi ?$$


$$C'_\pi = C_\pi + (1 - \dot{K})C_\mu$$

$$\left\{ \begin{array}{l} \dot{U}_o = (-g_m \dot{U}_{b'e}) R'_L \\ \dot{K} = \frac{\dot{U}_o}{\dot{U}_{b'e}} \end{array} \right.$$

$$\dot{K} = -g_m R'_L$$

$$C'_\pi = C_\pi + (1 + g_m R'_L) C_\mu$$

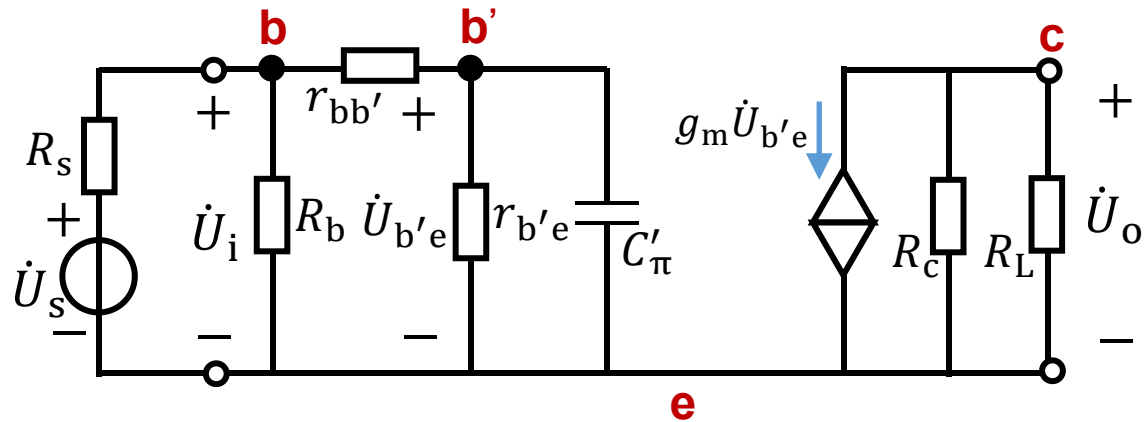High frequency: ignore C (short) , and consider C'_π (open)




$$\dot{A}_{ush} = \frac{\dot{U}_o}{\dot{U}_s} = \underbrace{\frac{R_i}{R_s + R_i} \cdot \frac{r_{b'e}}{r_{be}} \cdot (-g_m R'_L)}_{\dot{A}_{usm}} \underbrace{\frac{1}{1 + jf/f_H}}_{\text{Low pass}}$$

$$\dot{A}_{ush} = \dot{A}_{usm} \frac{1}{1 + jf/f_H}$$

High frequency: Amplitude and phase frequency characteristics

$$20\lg|\dot{A}_{ush}| = 20\lg|\dot{A}_{usm}| - 20\lg\sqrt{1 + \frac{f^2}{f_H^2}}$$
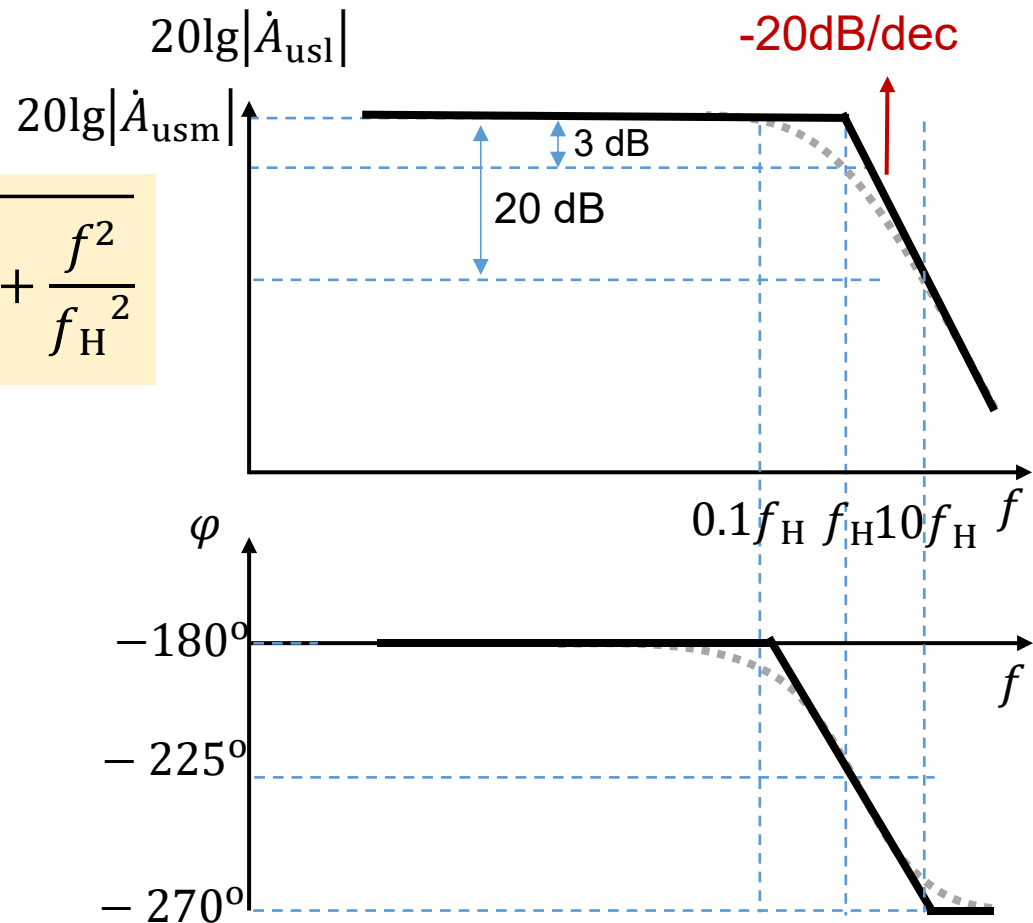
$$\varphi = -180^\circ - \arctan \frac{f}{f_H}$$




Full band: frequency response

$$\begin{aligned}\dot{A}_{us} &= \dot{A}_{usm} \frac{j^f/f_L}{1 + j^f/f_L} \frac{1}{1 + j^f/f_H} \\ &= \dot{A}_{usm} \frac{1}{1 + f_L/jf} \frac{1}{1 + j^f/f_H}\end{aligned}$$

High pass Low pass

Bandwidth $f_{bw} = f_H - f_L$

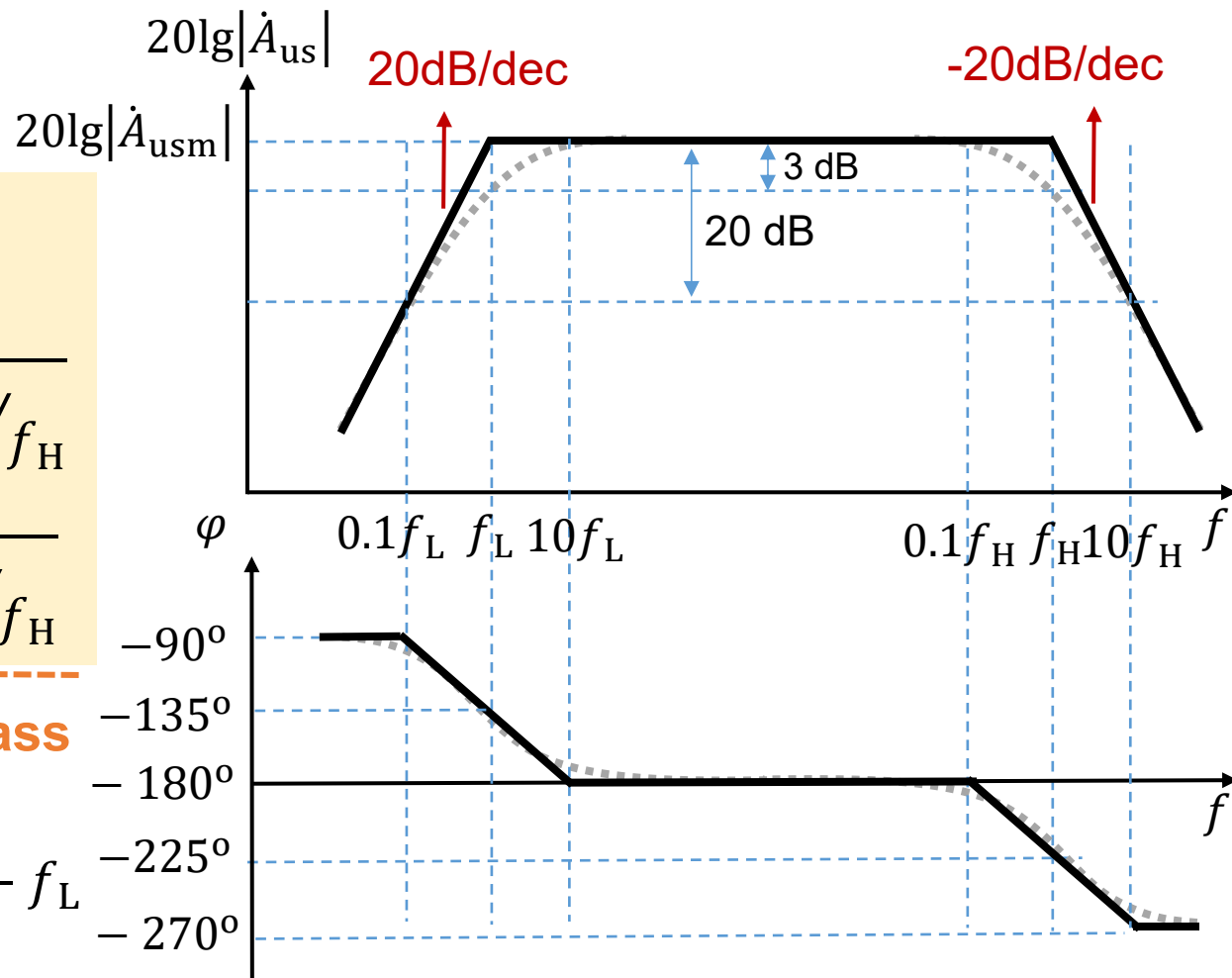


Bandwidth gain product: 带宽增益积

$$\text{Bandwidth } f_{bw} = f_H - f_L \approx f_H \left\{ \begin{array}{l} f_H = \frac{1}{2\pi[r_{b'e} // (r_{bb'} + R_s // R_b)] C'_\pi} \\ C'_\pi = C_\pi + (1 + g_m R'_L) C_\mu \end{array} \right.$$

$$\text{Voltage gain } \dot{A}_{usm} = \frac{R_i}{R_s + R_i} \cdot \frac{r_{b'e}}{r_{be}} \cdot (-g_m R'_L)$$

$$\left\{ \begin{array}{l} g_m R'_L \uparrow \rightarrow C'_\pi \uparrow \rightarrow f_H \downarrow \\ g_m R'_L \uparrow \rightarrow |\dot{A}_{usm}| \uparrow \end{array} \right.$$

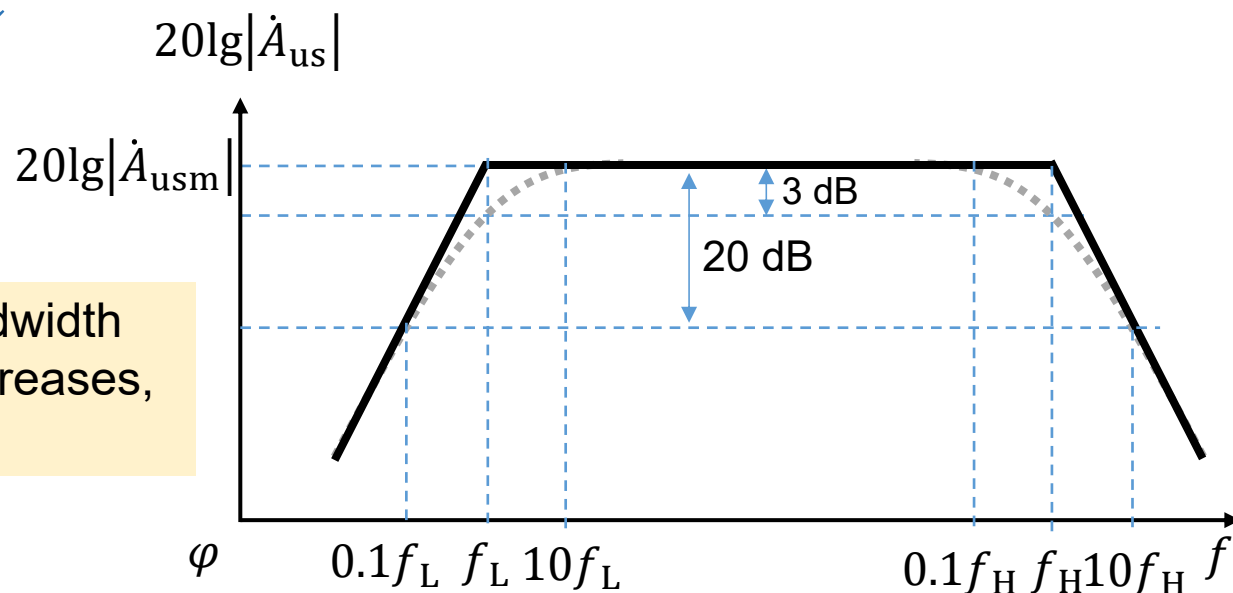

When gain increases, bandwidth decreases; When gain decreases, bandwidth increases.

Bandwidth gain product: 带宽增益积

$$\begin{aligned} & |\dot{A}_{usm} f_{bw}| \\ & \approx |\dot{A}_{usm} f_H| \\ & = \frac{R_i}{R_s + R_i} \cdot \frac{r_{b'e}}{r_{be}} \cdot \frac{g_m R'_L}{2\pi [r_{b'e} // (r_{bb'} + R_s // R_b)] C'_\pi} \end{aligned}$$

$$C'_\pi = C_\pi + (1 + g_m R'_L) C_\mu, \quad R_i = R_b // r_{be}, \quad R'_L = R_c // R_L$$

If $r_{be} \ll R_b$, $R_s \ll R_b$, $g_m R'_L \gg 1$, $g_m R'_L C_\mu \gg C_\pi$, we have:

$$R_i \approx r_{be}, \quad C'_\pi \approx g_m R'_L C_\mu,$$

$$|\dot{A}_{usm} f_{bw}| \approx \frac{1}{2\pi (r_{bb'} + R_s) C_\mu}$$

Bandwidth gain product: 带宽增益积

$$|\dot{A}_{\text{usm}} f_{\text{bw}}| \approx \frac{1}{2\pi (r_{\text{bb}'} + R_s) C_{\mu}}$$

$|\dot{A}_{\text{usm}} f_{\text{bw}}|$ only depends on the property of amplifier: $r_{\text{bb}'}$ and C_{μ} .

When amplifier is fixed, the bandwidth gain product of the amplifier circuit is fixed.

To improve the high frequency performance:

- Use amplifier with smaller $r_{\text{bb}'}$ and C_{μ} values.
- Use common-base amplifier circuit

5.5 Frequency response of multistage amplifier circuit

A simple case: two-stage amplifier circuit

The first stage voltage gain: $\dot{A}_{u1}$, second stage: $\dot{A}_{u2} = \dot{A}_{u1}$.


Two-stage voltage gain: $\dot{A}_u = \dot{A}_{u1} \cdot \dot{A}_{u2}$

$$|\dot{A}_u|e^{j\varphi} = |\dot{A}_{u1}|e^{j\varphi_1} \cdot |\dot{A}_{u2}|e^{j\varphi_2} = |\dot{A}_{u1}| \cdot |\dot{A}_{u2}|e^{j(\varphi_1+\varphi_2)}$$

$$|\dot{A}_u| = |\dot{A}_{u1}| \cdot |\dot{A}_{u2}|$$

$$\left\{ \begin{array}{l} \text{Amplitude } 20\lg|\dot{A}_u| = 20\lg|\dot{A}_{u1}| + 20\lg|\dot{A}_{u2}| = 40\lg|\dot{A}_{u1}| \\ \text{Phase } \varphi = \varphi_1 + \varphi_2 \end{array} \right.$$

Amplitude $20\lg|\dot{A}_u| = 20\lg|\dot{A}_{u1}| + 20\lg|\dot{A}_{u2}| = 40\lg|\dot{A}_{u1}|$

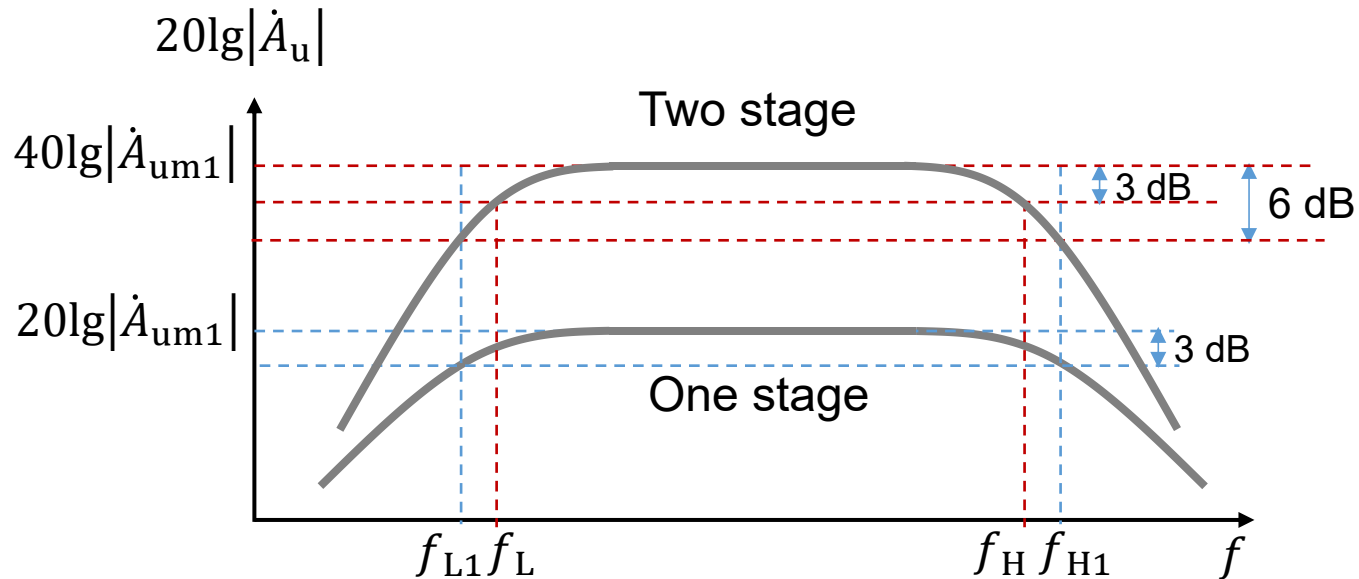

When $f = f_{L1}$ or $f = f_{H1}$, $20\lg|\dot{A}_{u1}| = 20\lg|\dot{A}_{um1}| - 3\text{dB}$

$$20\lg|\dot{A}_u| = 40\lg|\dot{A}_{u1}| = 40\lg|\dot{A}_{um1}| - 6\text{dB}$$

The bandwidth of two-stage amplifier circuit becomes narrower!

Q: f_L ? f_H ?

How to get the relation between f_{L1} (f_{H1}) and f_L (f_H) ?

One stage:

$$\left\{ \begin{array}{ll} 20\lg|\dot{A}_{uh1}| = 20\lg|\dot{A}_{um1}| - 20\lg \sqrt{1 + \frac{f^2}{f_{H1}^2}} & \text{High-f region} \\ 20\lg|\dot{A}_{ul1}| = 20\lg|\dot{A}_{um1}| + 20\lg \frac{\frac{f}{f_{L1}}}{\sqrt{1 + \frac{f^2}{f_{L1}^2}}} & \text{Low-f region} \end{array} \right.$$

Two stage: $20\lg|\dot{A}_u| = 40\lg|\dot{A}_{u1}|$


$$\left\{ \begin{array}{ll} 20\lg|\dot{A}_{uh}| = 40\lg|\dot{A}_{um1}| - 40\lg \sqrt{1 + \frac{f^2}{f_{H1}^2}} & \text{High-f region} \\ 20\lg|\dot{A}_{ul}| = 40\lg|\dot{A}_{um1}| + 40\lg \frac{\frac{f}{f_{L1}}}{\sqrt{1 + \frac{f^2}{f_{L1}^2}}} & \text{Low-f region} \end{array} \right.$$

How to get the relation between f_{L1} (f_{H1}) and f_L (f_H) ?

When $f = f_L$ or $f = f_H$,

$$\left\{ \begin{array}{l} 40\lg \sqrt{1 + \frac{f_H^2}{f_{H1}^2}} = 3 \text{ dB} = 20\lg\sqrt{2} \\ 40\lg \frac{\frac{f_L}{f_{L1}}}{\sqrt{1 + \frac{f_L^2}{f_{L1}^2}}} = -3 \text{ dB} = -20\lg\sqrt{2} \end{array} \right.$$

Phase: $\varphi = \varphi_1 + \varphi_2$

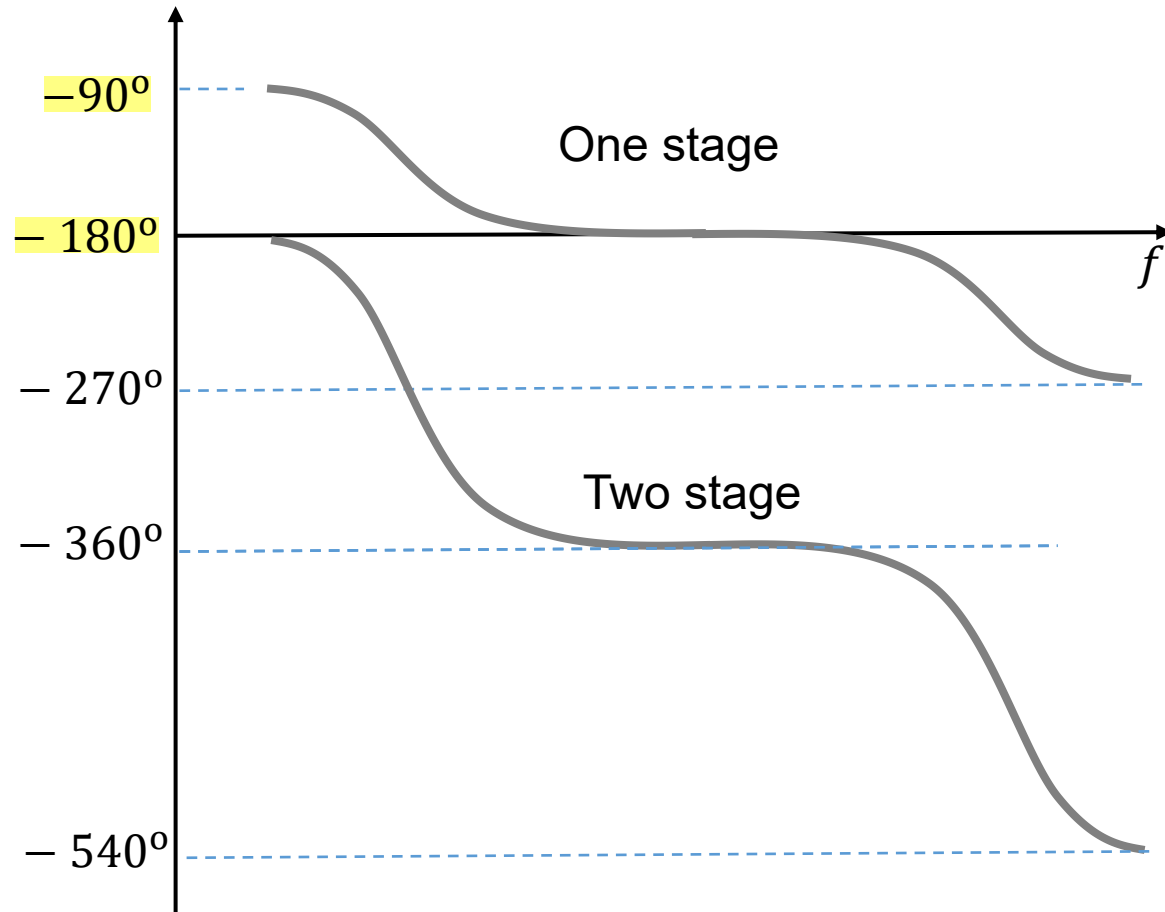

N-stage amplifier circuit

N-stage voltage gain: $\dot{A}_u = \dot{A}_{u1} \cdot \dot{A}_{u2} \cdots \dot{A}_{uN}$

$$|\dot{A}_u|e^{j\varphi} = |\dot{A}_{u1}|e^{j\varphi_1} \cdot |\dot{A}_{u2}|e^{j\varphi_2} \cdots |\dot{A}_{uN}|e^{j\varphi_N} = |\dot{A}_{u1}| \cdot |\dot{A}_{u2}| \cdots |\dot{A}_{uN}|e^{j(\varphi_1+\varphi_2+\cdots+\varphi_N)}$$

$$\left\{ \begin{array}{ll} \text{Amplitude} & 20\lg|\dot{A}_u| = 20\lg|\dot{A}_{u1}| + 20\lg|\dot{A}_{u2}| + \cdots + 20\lg|\dot{A}_{uN}| \\ \text{Phase} & \varphi = \varphi_1 + \varphi_2 + \cdots + \varphi_N \end{array} \right.$$

$$\left\{ \begin{array}{ll} \text{Amplitude} & 20\lg|\dot{A}_u| = \sum_{k=1}^N 20\lg|\dot{A}_{uk}| \\ \text{Phase} & \varphi = \sum_{k=1}^N \varphi_k \end{array} \right.$$

N-stage amplifier circuit

$$\left\{ \begin{array}{l} \text{Amplitude} \\ \text{Phase} \end{array} \right. \quad \begin{array}{l} 20\lg|\dot{A}_u| = \sum_{k=1}^N 20\lg|\dot{A}_{uk}| \\ \varphi = \sum_{k=1}^N \varphi_k \end{array}$$


Cut-off frequency: f_L and f_H

$$\left\{ \begin{array}{l} \frac{1}{f_H} = 1.1 \sqrt{\sum_{k=1}^N \frac{1}{f_{Hk}^2}} \\ f_L = 1.1 \sqrt{\sum_{k=1}^N f_{Lk}^2} \end{array} \right.$$

Bode plot of N-stage amplifier circuit


= Linear superposition of the Bode plot of each stage

多级放大电路波特图画法：等于每一级电路波特图的线性叠加

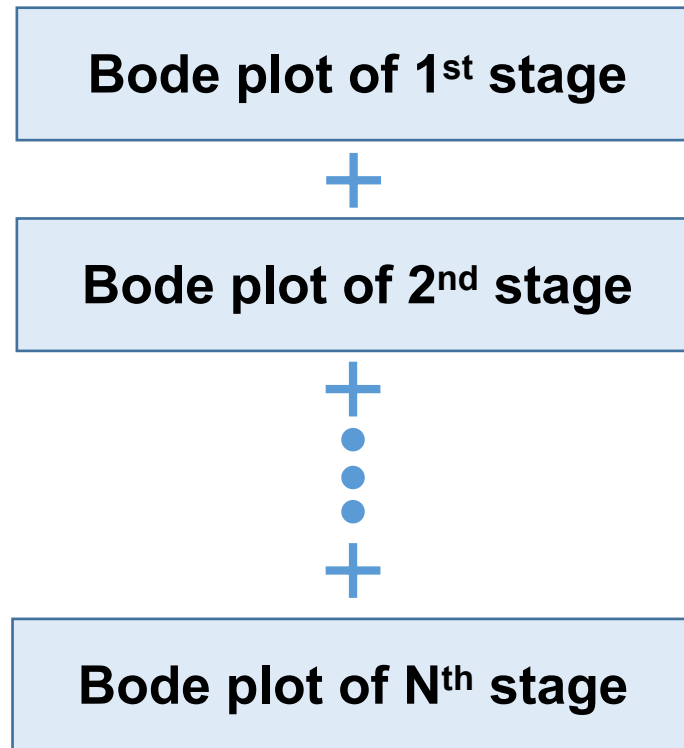


Q1: An amplifier circuit is made of two identical stages. The bode plot of each stage is shown in the figure below.

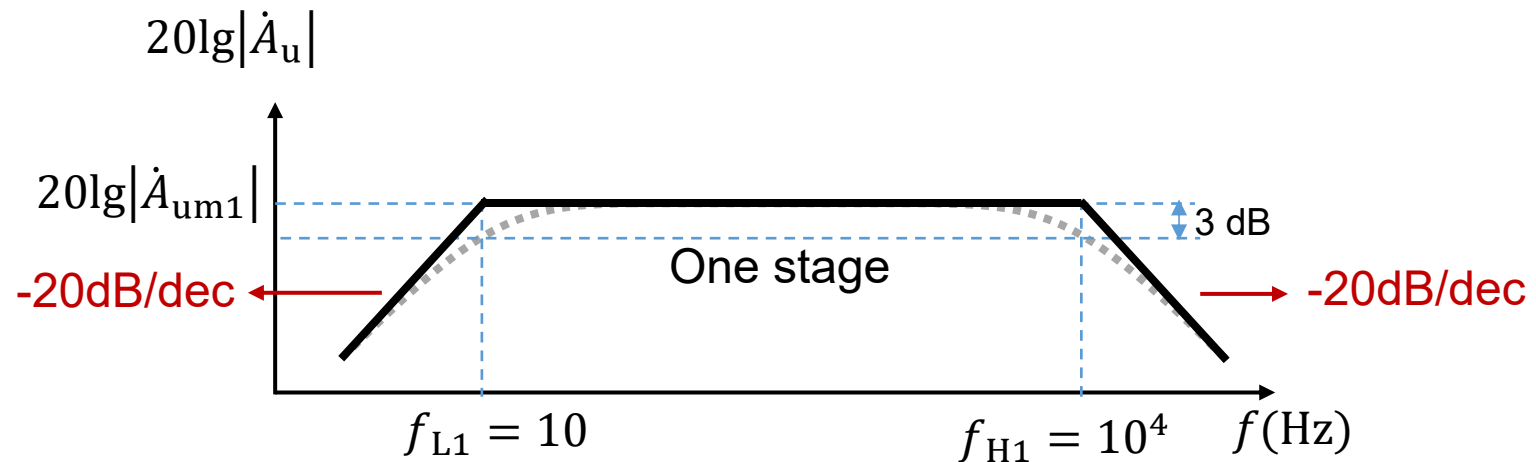- (1) Please draw the bode plot of the two-stage amplifier circuit;
- (2) Lower and upper cut-off frequency of the two stage amplifier circuit;
- (3) The voltage gain of the two-stage amplifier circuit for full wave band.



Answer (1):

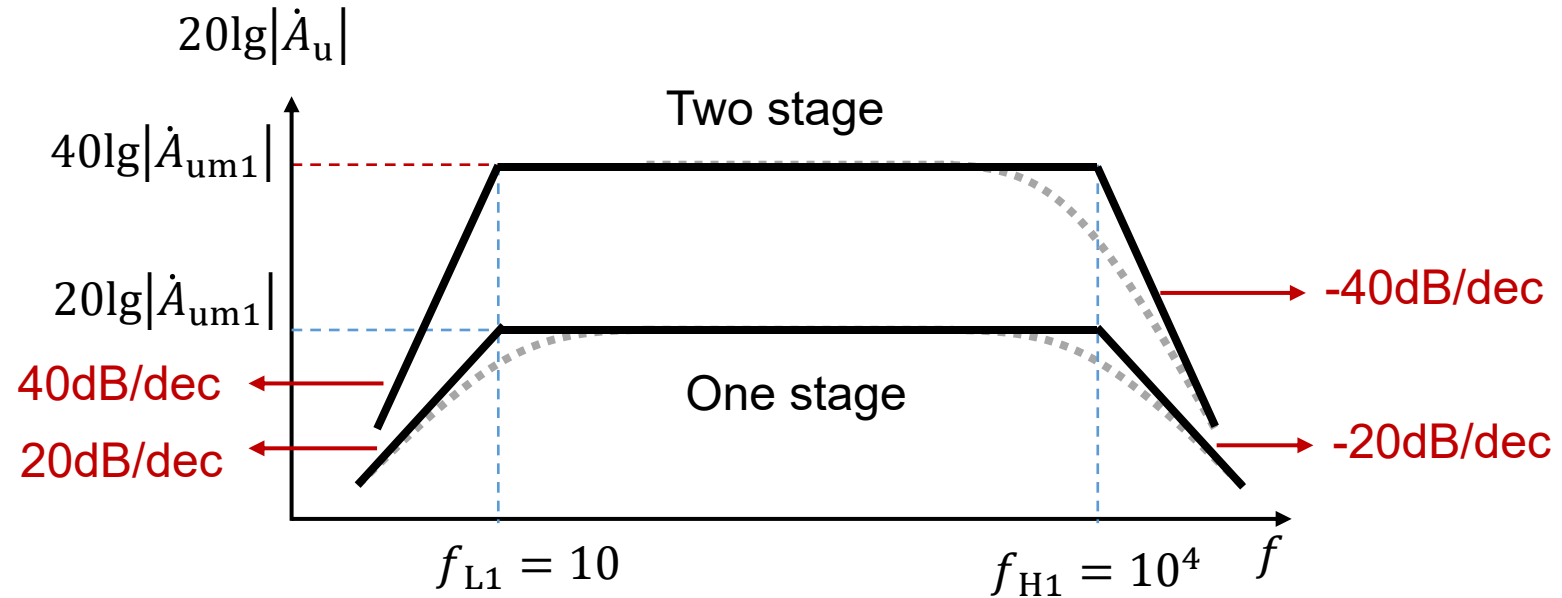


(2) Upper cut-off frequency for each stage: 10^4 , 10^4 Hz

Upper cut-off frequency:

$$\frac{1}{f_H} \approx 1.1 \sqrt{\sum_{k=1}^N \frac{1}{f_{Hk}^2}} = 1.1 \sqrt{\left(\frac{1}{10^4}\right)^2 + \left(\frac{1}{10^4}\right)^2}; \quad f_H = 0.58 \times 10^4 \text{ Hz}$$

Answer (2):

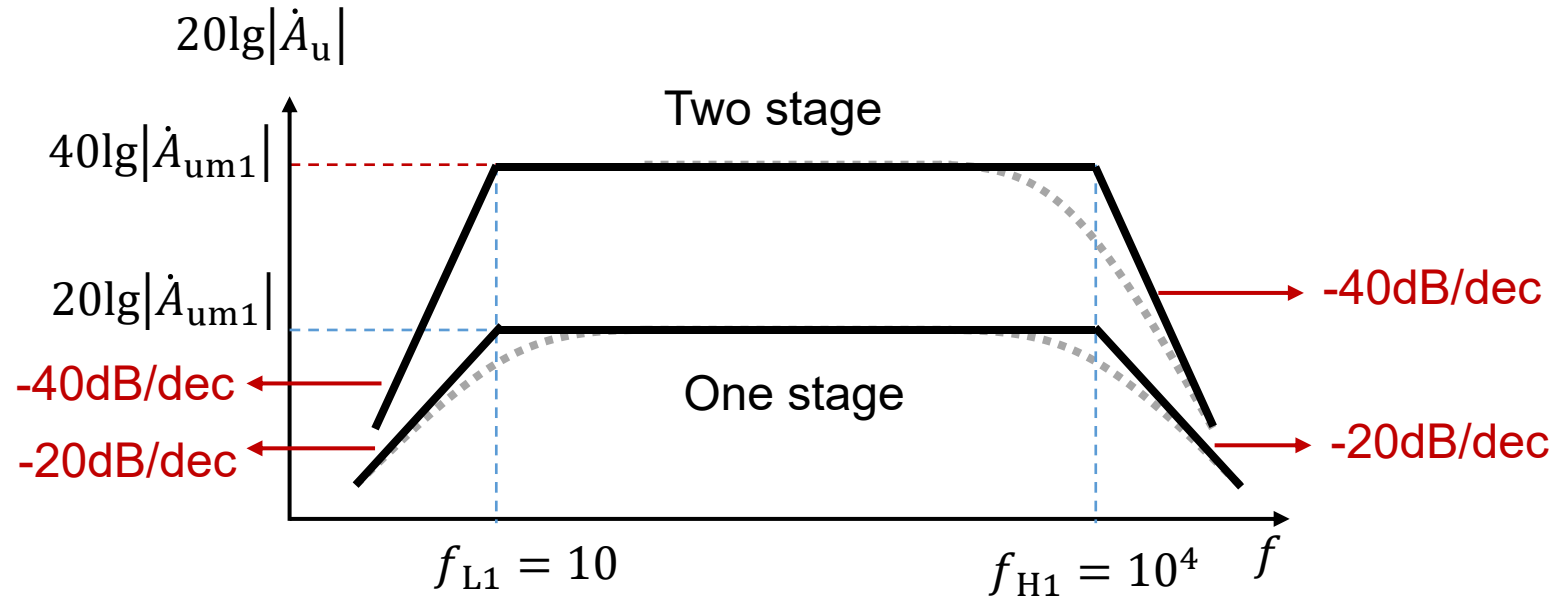


Lower cut-off frequency for each stage: 10 Hz, 10 Hz

Lower cut-off frequency:

$$f_L \approx 1.1 \sqrt{\sum_{k=1}^N f_{Lk}^2} = 1.1 \sqrt{10^2 + 10^2} = 15.6 \text{ Hz}$$

Answer (3):

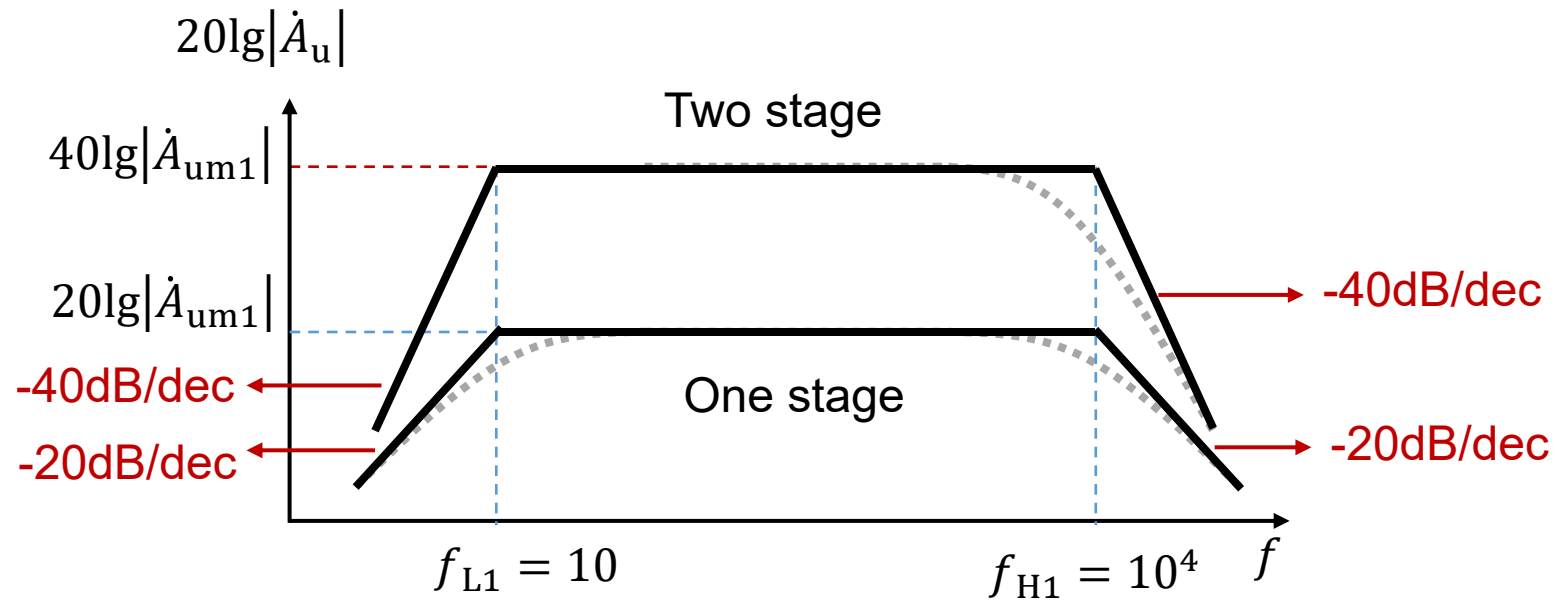


$$20\lg\dot{A}_{us} =$$

$$= 40\lg|\dot{A}_{um1}| + 20\lg\frac{1}{1 + f_{L1}/jf} + 20\lg\frac{1}{1 + f_{L2}/jf} + 20\lg\frac{1}{1 + jf/f_{H1}} + 20\lg\frac{1}{1 + jf/f_{H2}}$$

$$= 40\lg|\dot{A}_{um1}| + 40\lg\frac{1}{1 + f_{L1}/jf} + 40\lg\frac{1}{1 + jf/f_{H1}}$$



$$= 40\lg|\dot{A}_{um1}| + 40\lg\frac{1}{1 + 10/jf} + 40\lg\frac{1}{1 + jf/10^4}$$

Answer (3): another approach

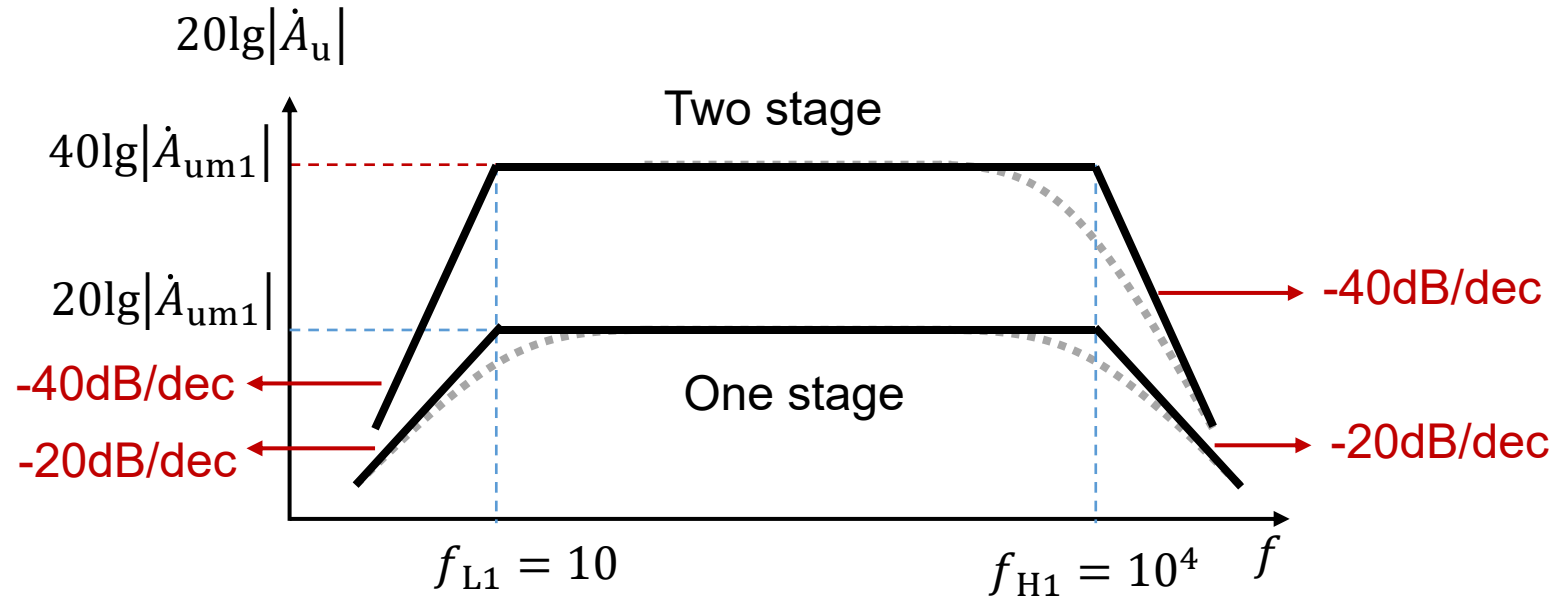


$$\begin{aligned}
 \dot{A}_{us} &= \dot{A}_{um1}^2 \frac{1}{1 + f_{L1}/jf} \frac{1}{1 + f_{L2}/jf} \frac{1}{1 + jf/f_{H1}} \frac{1}{1 + jf/f_{H2}} \\
 &= \dot{A}_{um1}^2 \frac{1}{1 + 10/jf} \frac{1}{1 + 10/jf} \frac{1}{1 + jf/10^4} \frac{1}{1 + jf/10^4} \\
 &= \dot{A}_{um1}^2 \left(\frac{1}{1 + 10/jf} \right)^2 \left(\frac{1}{1 + jf/10^4} \right)^2
 \end{aligned}$$

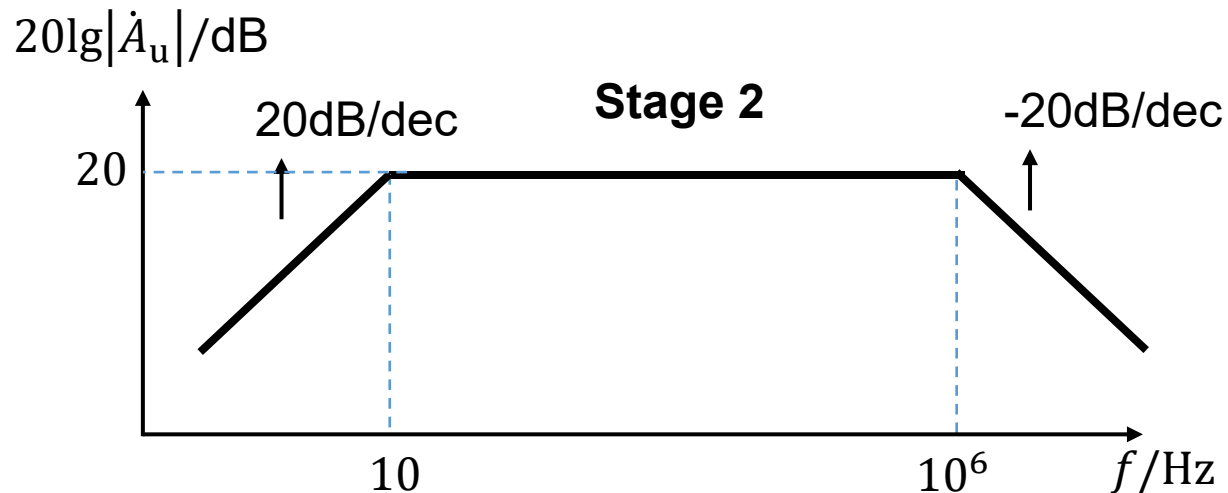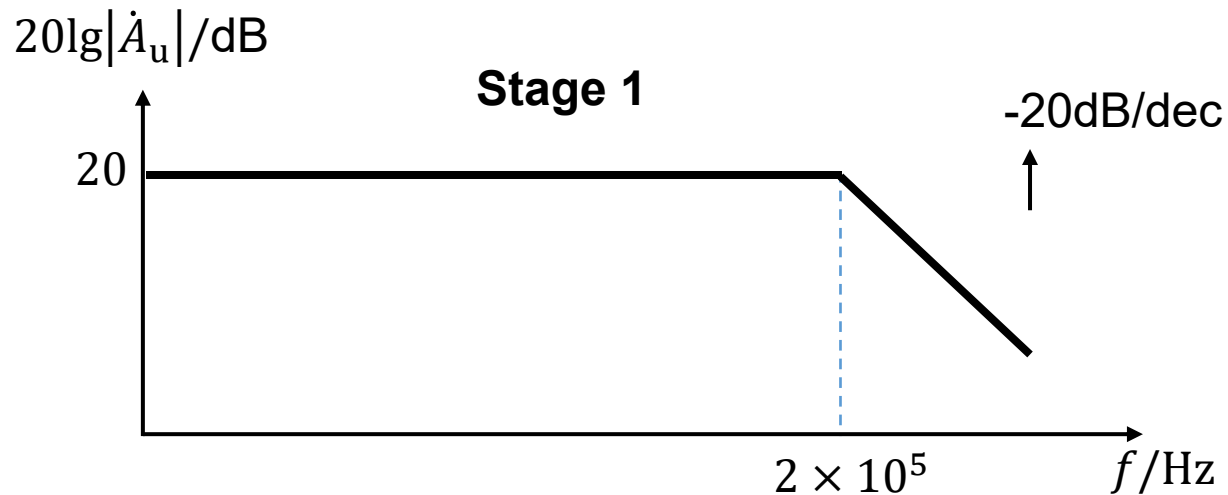
Q2: An amplifier circuit is made of **two stages**. The bode plot of each stage is shown in the figure below. Please draw the bode plot of the **two-stage amplifier circuit**.




Answer:

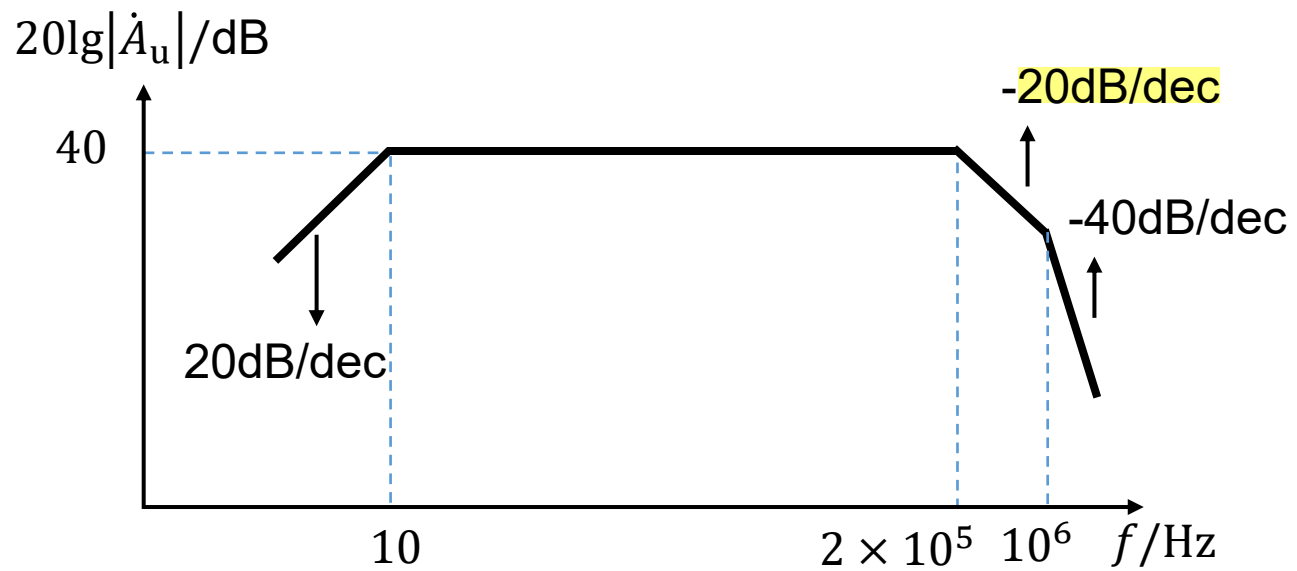

(2) lower and upper cut-off frequency?

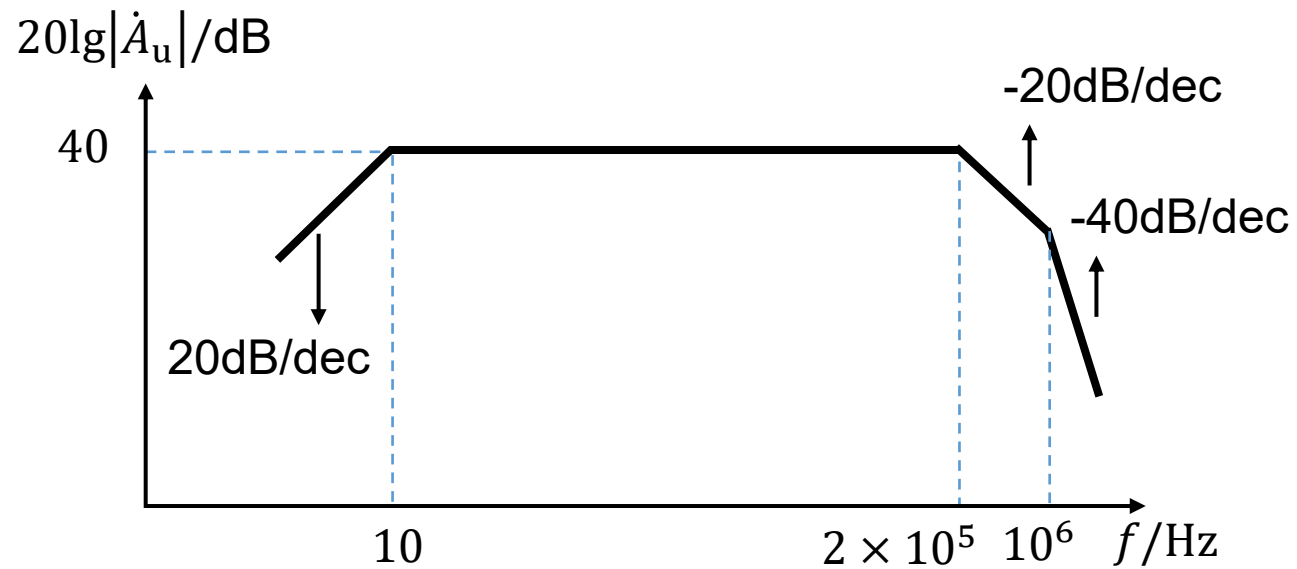

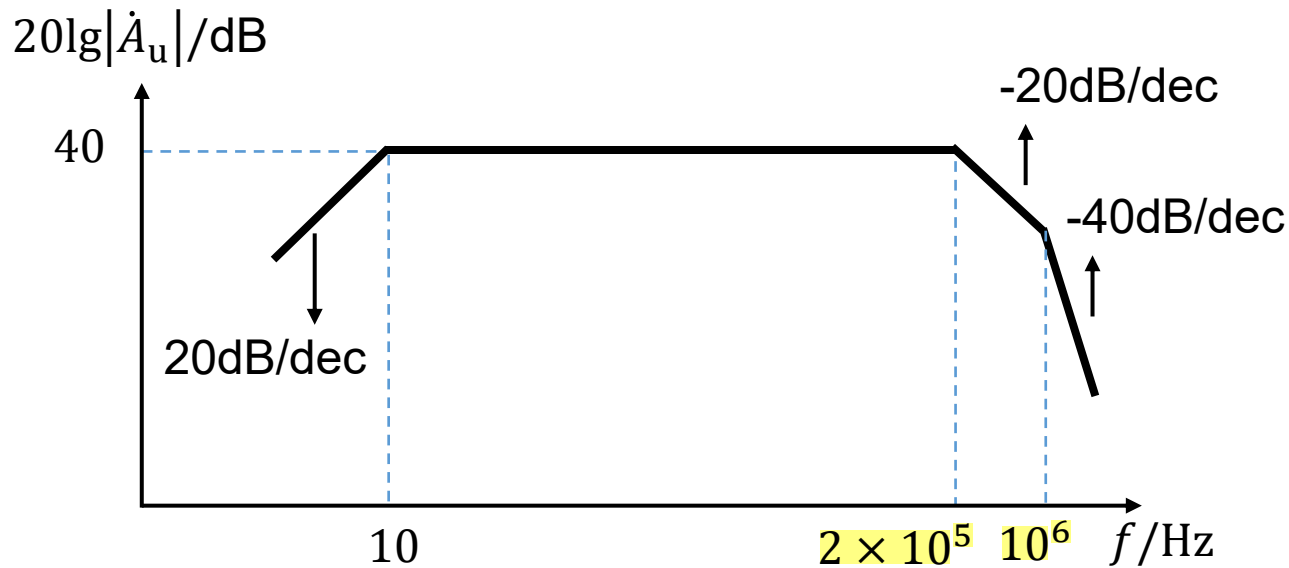


Lower cut-off frequency: 10 Hz

Upper cut-off frequency for each stage: 2×10^5 , 10^6 Hz

Upper cut-off frequency:
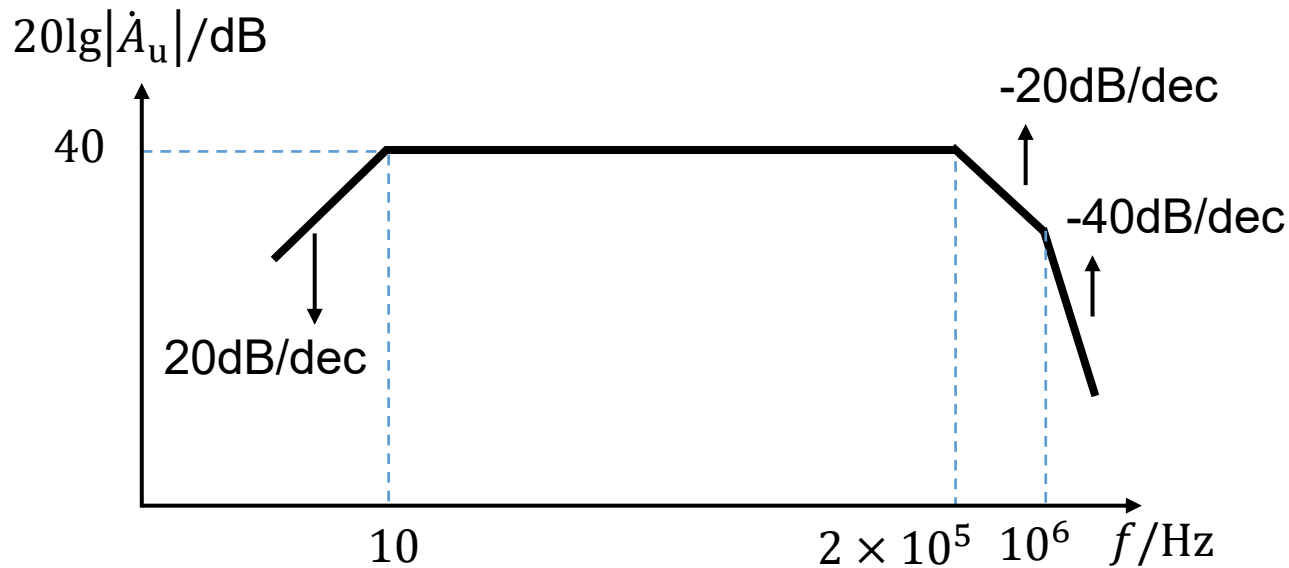
$$\frac{1}{f_H} = 1.1 \sqrt{\sum_{k=1}^N \frac{1}{f_{Hk}^2}} = 1.1 \sqrt{\left(\frac{1}{2 \times 10^5}\right)^2 + \left(\frac{1}{10^6}\right)^2} \quad f_H = 1.78 \times 10^5 \text{ Hz}$$



(3) Expression of voltage gain for full wave band

$$\begin{aligned}\dot{A}_{us} &= \dot{A}_{usm} \frac{1}{1 + f_L/jf} \frac{1}{1 + jf/f_{H1}} \frac{1}{1 + jf/f_{H2}} \\ &= 100 \frac{1}{1 + 10/jf} \frac{1}{1 + jf/2 \times 10^5} \frac{1}{1 + jf/10^6}\end{aligned}$$

Homework5: refer to black board

Deadline: 2025-05-07 11:59pm