


EE332

Digital System Design

Dr. Yi Zeng
Assistant Professor,
Department of Electrical and Electronic Engineering
Office: S236, South Tower of COE
Email: zengyi@sustech.edu.cn

Chapter 6: Modeling at the RT Level

 - A register transfer level (RTL) design consists of a set of registers connected by combinational logic.



6.1 Combinational circuit

- A combinational circuit, by definition, is a circuit whose output, after the initial transient period, is a function of current input.
- It has no internal state and therefore is “memoryless” about the past event (or past inputs).

signal A, B, Cin, Cout : bit;

...

process (A, B, Cin) **is**

begin

 Cout <= (A and B) or ((A xor B) and Cin);

end;

To describe a combinational circuit


- The variables or signals in the process must not have initial values.
- A signal or a variable must be assigned a value before being referenced.
- The arithmetic operators (such as +, -, *, etc), relational operators (such as <, >, =, etc), and logic operators (such as and, or, not, etc) can be used in an expression.

when a control signal is 1, $z \leq a + b$;
 Otherwise, $z \leq a + c$;


Operator sharing

- One way to reduce the overall size of synthesized hardware is to identify the resources that can be used by different operations. This is known as *resource sharing*.
 
```
sel <= c1 xor c2;
z <= a + b when sel='1' else
  a + c;
```


 
```
sel <= c1 xor c2;
d <= b when sel='1' else
  c;
z <= a + d;
```



- Performing resource sharing normally introduces some overhead and may penalize performance.



– In the above examples, assume T_{adder} , T_{mux} , $T_{boolean}$,

- For the circuit not sharing the adders:

$$T = \max (T_{adder}, T_{boolean}) + T_{mux}$$

- For the circuit sharing the adders:
  
$$T = T_{adder} + T_{boolean} + T_{mux}$$



Shaping the circuit

- Using VHDL code, it is possible to outline the general shape of the circuit.

Reduced-xor circuit

$$y = a_7 \oplus a_6 \oplus a_5 \oplus a_4 \oplus a_3 \oplus a_2 \oplus a_1 \oplus a_0$$

```
signal a: std_logic_vector (7 downto 0);
```


```
signal y: std_logic;
```

```
...
```


```
y <= a(7) xor a(6) xor a(5) xor a(4) xor a(3)  
      xor a(2) xor a(1) xor a(0);
```

从左到右执行

 $y \leq (((((((a_7 \oplus a_6) \oplus a_5) \oplus a_4) \oplus a_3) \oplus a_2) \oplus a_1) \oplus a_0);$


 
$$y \leq ((a_7 \oplus a_6) \oplus (a_5 \oplus a_4)) \oplus ((a_3 \oplus a_2) \oplus (a_1 \oplus a_0));$$



Example: Combinational adder-based multiplier

The algorithm includes three tasks:

- Multiply the digits of the multiplier (b_4, b_3, b_2, b_1 and b_0) by the multiplicand $A = (a_4, a_3, a_2, a_1, a_0)$ one at a time to obtain $b_4 \cdot A, b_3 \cdot A, b_2 \cdot A, b_1 \cdot A$ and $b_0 \cdot A$.

$$b_i * A = (a_4 \cdot b_i, a_3 \cdot b_i, a_2 \cdot b_i, a_1 \cdot b_i, a_0 \cdot b_i)$$

- Shift $b_i * A$ to left by i position.
- Add the shifted $b_i * A$ terms to obtain the final product.

						a_4	a_3	a_2	a_1	a_0
x						b_4	b_3	b_2	b_1	b_0
						a_4b_0	a_3b_0	a_2b_0	a_1b_0	a_0b_0
					a_4b_1	a_3b_1	a_2b_1	a_1b_1	a_0b_1	
			a_4b_2	a_3b_2	a_2b_2	a_1b_2	a_0b_2			
		a_4b_3	a_3b_3	a_2b_3	a_1b_3	a_0b_3				
+		a_4b_4	a_3b_4	a_2b_4	a_1b_4	a_0b_4				
	y_9	y_8	y_7	y_6	y_5	y_4	y_3	y_2	y_1	y_0

Initial description of an adder-based multiplier

```
library IEEE;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_arith.all;  
use ieee.std_logic_unsigned.all;
```

entity **mult5** is

```
port (a, b : in std_logic_vector(4 downto 0);  
      y: out std_logic_vector(9 downto 0));
```


```
end entity mult5;
```

architecture comb1_arch of mult5 is

```
constant WIDTH : integer := 5;
```

```
signal au, bv0, bv1, bv2, bv3, bv4: std_logic_vector(WIDTH-1 downto 0);
```
 
```
signal p0, p1, p2, p3, p4, prod: std_logic_vector(2*WIDTH-1 downto 0);
```



使用中间信号来寄存输入输出，避开输入只能放在右边输出只能放在左边的限制

```

begin
    au <= a;
    bv0 <= (others => b(0));
    bv1 <= (others => b(1));
    bv2 <= (others => b(2));
    bv3 <= (others => b(3));
    bv4 <= (others => b(4));
    p0 <= "00000" & (bv0 and au);
    p1 <= "0000" & (bv1 and au);
    p2 <= "000" & (bv2 and au);
    p3 <= "00" & (bv3 and au);
    p4 <= '0' & (bv4 and au);
    prod <= ((p0+p1)+(p2+p3));
    y <= prod;
end architecture comb1 arch;

```

a VHDL construct to assign a value to an object of array data type.

same {

- v <= "1011";
- v <= ('1', '0', '1', '1');
- v <= (3=>'1', 2=>'0', 1=>'1', 0=>'1');
- v <= (3|1|0=>'1', 2=>'0');
- v <= (2=>'0', others=>'1');
- v <= (others=>'0');

第3位为1，第2位为0，第1位为1，第0位为1

[illegible]

X	a_4 b_4	a_3 b_3	a_2 b_2	a_1 b_1	a_0 b_0	multiplicand multiplier
			a_4b_0	a_3b_0	a_2b_0	a_1b_0 a_0b_0
			$pp0_5$	$pp0_4$	$pp0_3$	$pp0_2$ $pp0_1$ $pp0_0$ partial product pp0
	+		a_4b_1	a_3b_1	a_2b_1	a_1b_1 a_0b_1
			$pp1_5$	$pp1_4$	$pp1_3$	$pp1_2$ $pp1_1$ $pp1_0$ partial product pp1
	+		a_4b_2	a_3b_2	a_2b_2	a_1b_2 a_0b_2
			$pp2_5$	$pp2_4$	$pp2_3$	$pp2_2$ $pp2_1$ $pp2_0$ partial product pp2
	+		a_4b_3	a_3b_3	a_2b_3	a_1b_3 a_0b_3
			$pp3_5$	$pp3_4$	$pp3_3$	$pp3_2$ $pp3_1$ $pp3_0$ partial product pp3
	+		a_4b_4	a_3b_4	a_2b_4	a_1b_4 a_0b_4
			$pp4_5$	$pp4_4$	$pp4_3$	$pp4_2$ $pp4_1$ $pp4_0$ partial product pp4
	y_9	y_8	y_7	y_6	y_5	y_4 y_3 y_2 y_1 y_0

改进：将十位加法器优化成六位加法器

More efficient description of an adder-based multiplier

```
architecture comb2_arch of mult5 is  
constant WIDTH : integer := 5;  
signal au, bv0, bv1, bv2, bv3, bv4: std_logic_vector (WIDTH-1  
    downto 0);  
signal pp0, pp1, pp2, pp3, pp4: std_logic_vector (WIDTH downto 0);  
signal prod: std_logic_vector (2*WIDTH-1 downto 0);
```

begin

au <= a;

bv0 <= (**others** => b(0));

bv1 <= (**others** => b(1));

bv2 <= (**others** => b(2));

bv3 <= (**others** => b(3));

bv4 <= (**others** => b(4));

pp0 <= '0' & (bv0 **and** au);

pp1 <= ('0' & pp0(WIDTH **downto** 1))+ ('0' & (bv1 **and** au));

pp2 <= ('0' & pp1(WIDTH **downto** 1))+ ('0' & (bv2 **and** au));

pp3 <= ('0' & pp2(WIDTH **downto** 1))+ ('0' & (bv3 **and** au));

pp4 <= ('0' & pp3(WIDTH **downto** 1))+ ('0' & (bv4 **and** au));

prod <= pp4 & pp3(0) & pp2(0) & pp1(0) & pp0(0);

y <= prod;

end architecture comb2_arch;

$$\begin{array}{r}
 \begin{array}{cccccc}
 & a_4 & a_3 & a_2 & a_1 & a_0 & \text{multiplicand} \\
 X & b_4 & b_3 & b_2 & b_1 & b_0 & \text{multiplier}
 \end{array} \\
 \hline
 & & a_4b_0 & a_3b_0 & a_2b_0 & a_1b_0 & a_0b_0 \\
 & & \hline
 & & pp0_5 & pp0_4 & pp0_3 & pp0_2 & pp0_1 & pp0_0 & \text{partial product pp0} \\
 & + & a_4b_1 & a_3b_1 & a_2b_1 & a_1b_1 & a_0b_1 \\
 & \hline
 & & pp1_5 & pp1_4 & pp1_3 & pp1_2 & pp1_1 & pp1_0 & \text{partial product pp1} \\
 & + & a_4b_2 & a_3b_2 & a_2b_2 & a_1b_2 & a_0b_2 \\
 & \hline
 & & pp2_5 & pp2_4 & pp2_3 & pp2_2 & pp2_1 & pp2_0 & \text{partial product pp2} \\
 & + & a_4b_3 & a_3b_3 & a_2b_3 & a_1b_3 & a_0b_3 \\
 & \hline
 & & pp3_5 & pp3_4 & pp3_3 & pp3_2 & pp3_1 & pp3_0 & \text{partial product pp3} \\
 & + & a_4b_4 & a_3b_4 & a_2b_4 & a_1b_4 & a_0b_4 \\
 & \hline
 & & pp4_5 & pp4_4 & pp4_3 & pp4_2 & pp4_1 & pp4_0 & \text{partial product pp4} \\
 & \hline
 y_9 & y_8 & y_7 & y_6 & y_5 & y_4 & y_3 & y_2 & y_1 & y_0
 \end{array}$$

缺点：时延较长

6.2 Sequential circuit


- A sequential circuit is a circuit that has an internal state, or memory.
- Its output is a function of current input as well as the internal state. Thus the output is affected by current input values as well as past input values.
- A synchronous sequential circuit, in which all memory elements are controlled by a global synchronizing signal, greatly simplifies the design process and is the most important design methodology.
- Flip-flops and latches are two commonly used one-bit memory devices.

6.2.1 Latch

- A latch is a level-sensitive memory device.


```

 signal S, d, q: bit
.....
process (S, d) is
begin
    if (S='1') then
        q <= d;
    end if;
end process;
  
```




Truth table

S	q*
0	q
1	d

 

Conceptual diagram

 

Gate-level diagram

- In general, latches are synthesized from incompletely specified conditional expressions in a combinational description.
- Latch inferences occur normally with **if** statements or **case** statements.
- To avoid having a latch inferred, assign a value to the signal under all conditions.

```
signal S, d, q: bit
.....
process (S, d) is
begin
    if (S='1') then q <= d;
    else q <= '0';
    end if;
end process;
```

asynchronous reset or preset

- An asynchronous reset (or preset) will change the output of a latch to 0 (or 1) immediately.

```
signal S, RST, d, q: bit
```

```
.....
```

```
process (S, RST, d) is  
begin
```

```
    if (RST = '1') then
```


```
        q <= '0';
```

```
    elsif (S='1') then
```

```
        q <= d;
```

```
    end if;
```

```
end process;
```

 

优先级 : $RST > S > d$

优先级高的先出现在if statement中

6.2.2 Flip-Flops (f/f)

- A flip-flop is an edge-triggered memory device.
- To detect the rising edge (or falling edge), or the event occurred for a signal, we can make use of the attribute of a signal.

signal CLK : bit;

.....

CLK'event true if CLK changes its value.


CLK'event **and** CLK = '1' true for the CLK rising edge

CLK'event **and** CLK = '0' true for the CLK falling edge

- The **event** attribute on a signal is the most commonly used edge-detecting mechanism. It operates on a signal and returns a Boolean value. The result is true if the signal shows a change in value.

An example of a simple flip-flop

 
- An edge triggered flip-flop will be generated from a VHDL description if a signal assignment is executed on the rising (or falling) edge of another signal.



```
entity dff is
port (d, CLK: in bit; q: out bit);
end entity dff;
architecture behavior of dff is
begin
process (CLK) is    和锁存器不同，敏感列表中没有d
begin
    if (CLK'event and CLK='1') then
        q <= d;
    end if;
end process;
end architecture behavior;
```

Synchronous sets and resets

 - Synchronous inputs set (preset) or reset (clear) the output of flip-flops when they are asserted. The assignment will only take effect while the clock edge is active.




synchronous reset: S_RST不会出现在flip-flop的端口中

```
signal CLK, d, q, S_RST: bit;  
.....  
process (CLK) is  
begin  
    if (CLK'event and CLK='1') then  
        if (S_RST = '1') then  
            q <= '0';  
        else  
            q <= d;  
        end if;  
    end if;  
end process;
```

Asynchronous sets and resets

- Asynchronous inputs set (preset) or reset (clear) the output of flip-flops whenever they are asserted independent of the clock.
 
```
signal CLK , A_RST, d, q: bit;  
.....  
process (CLK, A_RST) is  
begin  
    if (A_RST = '1') then  
        q <= '0';  
    elsif (CLK'event and CLK='1') then  
        q <= d;  
    end if;  
end process;
```



A f/f with more than one asynchronous input

```
signal CLK , RST, PRST, EN: bit;
signal d, q: bit;
```

.....

```
architecture two_seg of dff_en is
```

```
signal q_reg, q_next : bit;
```

```
begin
```

```
process (CLK, PRST, RST) is
```

```
begin
```

```
    if (PRST = '1') then
```

```
        q_reg <= '1';
```

```
    elsif (RST = '1') then
```

```
        q_reg <= '0';
```

```
    elsif (CLK'event and CLK='1') then
```

```
        q_reg <= q_next;
```

```
    end if;
```


```
end process;
```

process中定义 状态方程

```
q_next <= d when EN = '1' else  驱动方程
q_reg;
```

```
q <= q_reg;  输出方程
```


```
end architecture two_seg;
```

 


PRESET优先级高于RESET
当PRESET=1, 与门输出被锁定为0

 6.2.3 VHDL templates for sequential circuits

- An RTL circuit can be described in two segments:
 - A synchronous section updates the register information at the rising edge of the clock.
 - $q_reg \leq q_next;$
 - A combinational section describes combinational logics, for example, update q_next ;



 

A synchronous section

or

A synchronous section
with asynchronous
inputs

+

A combinational section

```
if (CLK'event AND CLK='1') then
```

```
    q_reg <= q_next;
    -- CLK is the clock input to reg q
```

```
end if;
```

```
if (async_sig = '1') then
```

```
    q_reg <= '0';
    -- active high asynchronous reset
```

```
elsif (CLK's event AND CLK='1') then
```

```
    q_reg <= q_next;
    -- CLK is the clock input to reg Q
```

```
end if;
```

```
q_next <= expression;
-- other combinational logics.
```

An example

entity PULSER is

port (CLK, PB : in bit ;
PB_pulse : out bit);

end PULSER;

architecture BHV of PULSER is

signal q1_reg, q2_reg,
q1_next, q2_next : bit;

begin

process (CLK) is
begin

if (CLK'event and CLK='1') then

q1_reg <= q1_next;

q2_reg <= q2_next;

end if;


end process;

q1_next <= PB;

q2_next <= q1_reg;

PB_pulse <= (not q1_reg) nor q2_reg;

end architecture BHV;

 

6.2.4 Registers


-- 4-bit simple register

```

signal CLK , ASYNC : bit;
singal Din, Dout :
    bit_vector (3 down to 0);
.....

```
 
```
process (CLK, ASYNC) is  
begin  
    if (ASYNC = '1') then  
        Dout <= "1100";  
    elsif (CLK'event and CLK='1') then  
        Dout <= Din;  
    end if;  
end process;
```



-- 4-bit serial-in and serial-out shift register

signal CLK ,d, q : bit;

.....

architecture two_seg of shift_register is

signal r_reg, r_next: bit_vector (3 downto 0);

begin

process (CLK) is

begin

if (CLK'event and CLK='1') then

r_reg <= r_next;

end if;

end process;

r_next <= d & r_reg(3 downto 1);

q <= r_reg(0);

end architecture two_seg;

