

EE332
Digital System Design

Dr. Yi Zeng
Assistant Professor,
Department of Electrical and Electronic Engineering
Office: S236, South Tower of COE
Email: zengyi@sustech.edu.cn

4.3 More on process

- Upon initialization all processes are executed once, or suspended on some form of the wait statement reached.
- Thereafter, processes are executed in a data-driven manner: activated
 - by events on signals in the sensitivity list of the process or
 - by waiting for the occurrence of specific event using the wait statement.

当wait语句被触发时，将从wait语句的下一句开始执行，到同一个wait语句之后停止

Example:
Signal
assignment
with
process



```
library IEEE;
use IEEE.std_logic_1164.all;
entity sig_var is
port (x, y, z : in std_logic; res1, res2 : out std_logic);
end entity sig_var;
architecture behavior of sig_var is
signal sig_s1, sig_s2 : std_logic;
begin
  proc1: process (x, y, z) is
    variable var_s1, var_s2 : std_logic;
    begin
      L1: var_s1 := x and y;
      L2: var_s2 := var_s1 xor z;
      L3: res1 <= var_s1 nand var_s2;
    end process proc1;
  proc2: process (x, y, z) is
    begin
      L1: sig_s1 <= x and y;
      L2: sig_s2 <= sig_s1 xor z;
      L3: res2 <= sig_s1 nand sig_s2;
    end process proc2;
end architecture behavior;
```

执行和赋值都是即刻完成的

执行L2时，并没有拿到本轮中计算得到的sig_s1的值

- All of the ports of the entity and the signals declared within an architecture are visible within a process.
- These port and signals can be read or assigned values from within a process; this is how processes can communicate among themselves.

Example:
Communicating
processes

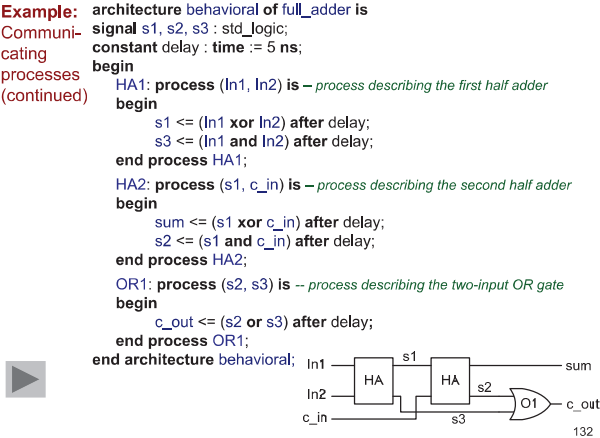
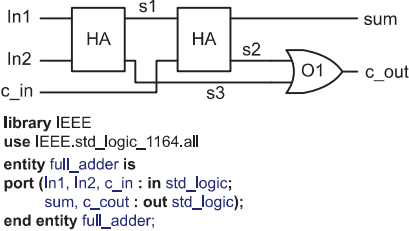


Chapter 5: Modeling Structure

- Describing a system in terms of the interconnections of its components.
- Motivation
 - represent a digital system in hierarchical structure.
 - share components between developers.


5.1: Component

NAND2 Gate

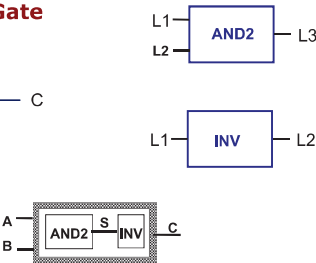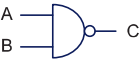

Architecture:
Structure style

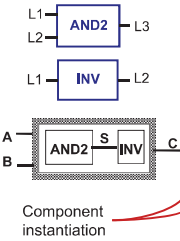Component declaration:
a component instance
needs to be bound to an
entity



A1 A2是必须的

```
entity NAND2 is
port (A, B : in bit; C : out bit);
end entity NAND2;

architecture STRUCTURE of NAND2 is
  component AND2 is
    port (L1, L2 : in bit; L3 : out bit);
  end component AND2;
  component INV is
    port (L1 : in bit; L2 : out bit);
  end component INV;
  signal S : BIT;
begin
  A1: AND2 port map (L1 => A, L2 => B, L3 => S);
  A2: INV port map (L1=>S, L2=> C);
end architecture STRUCTURE;
```

Component instantiation

port_name → Actual signal name
A1 : AND2 port map (L1 => A, L2 => B, L3 => S);

Name association - the syntax "port_name =>" is provided so that the order of the signals listed after PORT MAP keywords need NOT follow the order of the ports in the corresponding COMPONENT declaration.

A1 : AND2 port map (A, B, S);

Positional association - if the signal names following the PORT MAP keywords are given in the same order in the COMPONENT declaration, then "port_name =>" is not needed.

Component Entity: AND2 and INV


```
entity AND2 is
port (L1, L2 : in bit;
      L3 : out bit);
end entity AND2;

architecture dataflow of AND2 is
begin
  L3 <= L1 and L2;
end architecture dataflow;

entity INV is
port (L1 : in bit;
      L2 : out bit);
end entity INV;

architecture dataflow of INV is
begin
  L2 <= not L1;
end architecture dataflow;
```

Full Adder: Entity and architecture

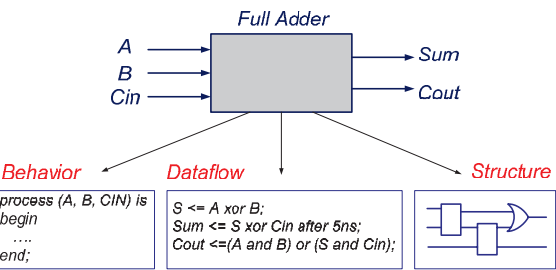

Full Adder: Data flow style architecture

```
entity Full_Adder is
port (A, B, Cin : in bit;
      Sum, Cout : out bit);
end entity Full_Adder;

architecture DATAFLOW of Full_Adder is
signal S: bit;
begin
  S <= A xor B;
  Sum <= S xor Cin after 5 ns;
  Cout <= (A and B) or (S and Cin);
end architecture DATAFLOW;
```

Time period between cause and effect. Signal pulse shorter than this time period is ignored.

Full Adder: Behavioral style architecture

case语句需要放在process里



```
architecture behavioral of full_adder is
begin
  HA1: process (In1, In2, c_in) is
  begin
    case In1&In2&c_in is
      when "000" =>
        sum <= '0'; c_out <= '0';
      when "111" =>
        sum <= '1'; c_out <= '1';
      when "001" | "010" | "100" =>
        sum <= '1'; c_out <= '0';
      when others =>
        sum <= '0'; c_out <= '1';
    end case;
  end process HA1;
end architecture behavioral;
```

In1	In2	c_in	sum	c_out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full Adder: structural style architecture


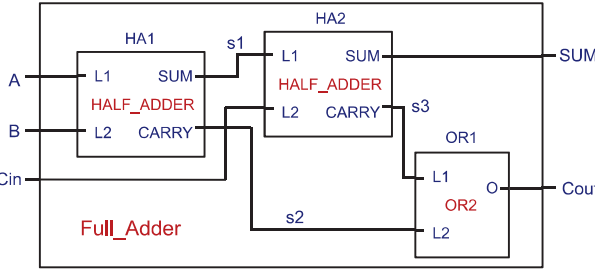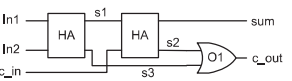
```
architecture STRUCTURE of Full_Adder is
component HALF_ADDER is
port (L1, L2 : in bit; SUM, CARRY : out bit);
end component HALF_ADDER;
component OR2 is
port (L1, L2 : in bit; O: out bit);
end component OR2;
signal s1, s2, s3 : BIT
begin
  -- see next page;
end architecture STRUCTURE;
```



```
architecture STRUCTURE of Full_Adder is
-- Declare components and intermediate signal here. See last page;
begin
  HA1: HALF_ADDER port map (L1=>A, L2=>B, SUM=>s1, CARRY=>s2);
  HA2: HALF_ADDER port map (L1=>s1, L2=>CIN, SUM=>SUM, CARRY=>s3);
  OR1: OR2 port map (L1=>s3, L2=>s2, O=>COUT);
end architecture STRUCTURE;
```

Component Entity: Half_Adder

```
entity Half_Adder is
port (L1, L2 : in bit;
      Sum: out bit;
      Carry: out bit);
end entity Half_Adder;
```



```
architecture STRUCTURE of Half_Adder is
component XOR2 is
port (I0, I1: in BIT; O: out bit);
end component XOR2;
component AND2 is
port (I0, I1: in BIT; O: out bit);
end component AND2;
begin
  U1: XOR2 port map (I0 => L1, I1 => L2, O => Sum);
  U2: AND2 port map (I0 => L1, I1 => L2, O => Carry);
end architecture STRUCTURE;
```

Component Entity: OR2, AND2, XOR2

```
entity OR2 is
port (L1, L2: in bit; O: out bit);
end entity OR2;
```

```
architecture BHV of OR2 is
begin
  O <= L1 or L2 after 10 ns;
end architecture BHV;
```


```
entity AND2 is
port (I0, I1: in bit; O: out bit);
end entity AND2;
```

```
architecture dataflow of AND2 is
begin
  O <= I0 and I1;
end architecture dataflow;
```


```
entity XOR2 is
port (I0, I1: in bit; O: out bit);
end entity XOR2;
```

```
architecture BHV of XOR2 is
begin
  O <= I0 xor I1 after 10 ns;
end architecture BHV;
```

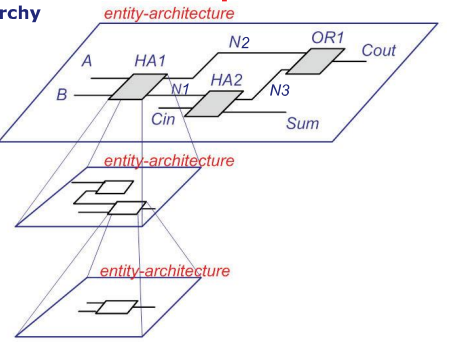Structural Decomposition: A design Hierarchy




Structural Decomposition: Design Tree

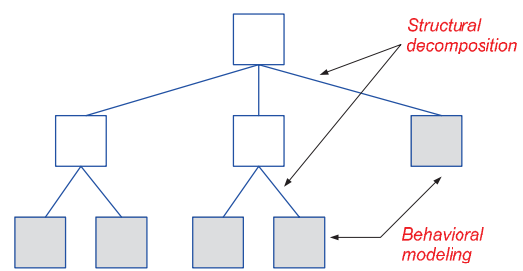

146

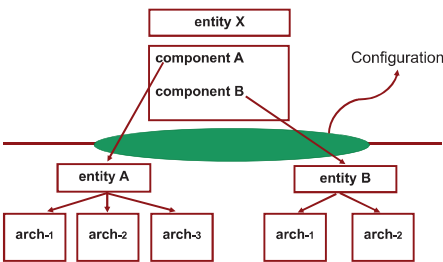5.2. Configuration

- When there is more than one architecture for an entity, configuration explicitly specifies which architecture is to be used for the entity during component instantiation.



147

- The process of association of an architecture description with a component in a structure model is referred to as *binding* an architecture to a component.
- Default binding rules:
 - The entity with the same name as the component is bound to the component.
 - If there are multiple architectures for the entity, the last compiled architecture for the entity is used.
 - The entity-architecture description may locate in the same file as that of instantiating the component, or in some other files in the working directory.

148

```
entity HALF_Adder is
port (L1, L2 : in bit;
      SUM, CARRY : out bit);
end entity Half_Adder;

architecture STRUCTURE of HALF_Adder is
  component XOR_GATE is
    port (I0, I1 : in BIT; O : out BIT);
  end component XOR_GATE;
  component AND2 is
    port (I0, I1 : in BIT; O : out BIT);
  end component AND2;
begin
  U1: XOR_GATE port map (L1, L2, SUM);
  U2: AND2 port map (L1, L2, CARRY);
end architecture STRUCTURE;

architecture BEHAVIOR of HALF_ADDER is
begin
  SUM <= L1 xor L2;
  CARRY <= L1 and L2;
end architecture BEHAVIOR;
```

Two architectures


One

The other one

149

```
architecture STRUCTURE of Full_Adder is
  component HALF_ADDER is
    port (L1, L2 : in bit; SUM, CARRY : out bit);
  end component HALF_ADDER;
  component OR_GATE is
    port (L1, L2 : in bit; O : out bit);
  end component OR_GATE;
  for HA1: HALF_ADDER use entity HALF_ADDER(BEHAVIOR);
  for HA2: HALF_ADDER use entity HALF_ADDER(STRUCTURE);
  signal N1, N2, N3 : BIT;
begin
  OR1: OR2 port map (L1=>N3, L2=>N2, O=>COUT);
  HA1: HALF_ADDER port map (L1=>A, L2=>B, SUM=>N1, CARRY=>N2);
  HA2: HALF_ADDER port map (L1=>N1, L2=>CIN, SUM=>SUM,
    CARRY=>N3);
end architecture STRUCTURE;
```

Configuration specifications

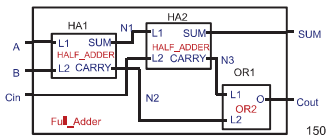

150

- If the entity-architecture descriptions locate in some other directories, the configuration specification have to includes the library name.
 - for HA1: HALF_ADDER use entity mydesign.HALF_ADDER(arch1);
 - for HA2: HALF_ADDER use entity mydeisgn.HALF_ADDER(arch2);
- If there is only one architecture in an entity, the architecture name can be omitted.
 - for OR1: OR_GATE use entity work.OR_GATE;
- Keywords: **all**, **others**
 - Library name
 - for all: HALF_ADDER use entity work.HALF_ADDER(arch1);
 - for HA1: HALF_ADDER use entity work.HALF_ADDER(arch1);
 - for others: HALF_ADDER use entity work.HALF_ADDER(arch2);

Architecture name
Entity name
Library name


151

5.3. Modeling a test bench

- Motivation
 - Test designs prior to construction and use of the circuit.
- To test a compiled VHDL design, we can either
 - provide stimuli interactively through the command window of a simulator, or
 - write a VHDL program (a VHDL test bench).

152

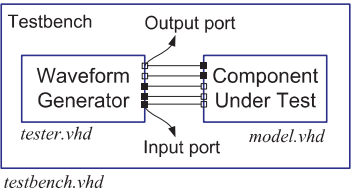- A test bench
 - does not have external ports.
 - contains two part:
 - a component representing the circuit under test
 - waveform generators which produce waveforms to the input of the component under test.



153

5.3.1 Functional verification of combinational designs

- Determine if a design meets a system's functional specifications.
- Not concern with any timing delays that results from mapping synthesized logic to a target programmable logic device.
- Allow to find logic errors early in the design flow and prevent wasting time performing synthesis, place and route, and time simulation.

154

Language and approach to be used

- Full range of VHDL language constructs and features can be used for test bench.
- Exhaustive verification
 - Counting approach treating all inputs as a single vector starting from 0 and subsequently incremented through all its possible binary combinations.
 - Functionality approach taking into account the functionality of the design being tested when determining the order for applying input combination

155

5.3.2 A simple test bench

```
library ieee;    -- load the ieee 1164 library
use ieee.std_logic_1164.all;    -- make the package 'visible'

entity test_half_adder is    -- the top level entity of the test bench has no
    -- external ports.
end entity test_half_adder;

architecture test of test_half_adder is
    component half_adder is    -- declare the component under test
        port (x, y: in std_logic; sum, carry: out std_logic);
    end component half_adder;

    for UUT: half_adder use entity configuration specifications
        work_half_adder(concurrent_behavior);
    synthesis之后会出错
```

156


-- Stimulus signals -- to connect test bench to UUT input ports
signal x_tb, y_tb: std_logic;
-- Observed signals -- to connect test bench to UUT output ports
signal sum_tb, carry_tb: std_logic;

begin

-- Create an instance of the half_adder circuit.
UUT: half_adder port map (x => x_tb, y => y_tb, sum =>
 sum_tb, carry => carry_tb);


-- Signal assignment statements generating stimulus values
x_tb <= '1', '0' after 5 ns, '1' after 10 ns, '0' after 15 ns;
y_tb <= '1', '0' after 10 ns;

end architecture test;

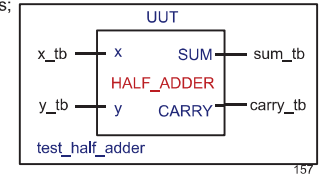

157

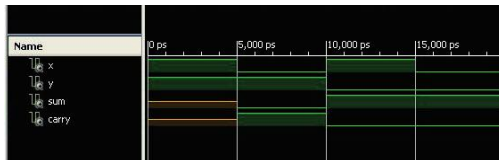Waveforms from simulation of half-adder test bench



158

5.3.3 Single process test bench

```
library ieee;
use ieee.std_logic_1164.all;

entity test_half_adder is
end entity test_half_adder;

architecture behavior of test_half_adder is
    component half_adder is
        port (x, y: in std_logic; sum, carry: out std_logic);
    end component half_adder;
    for UUT: half_adder use entity
        work_half_adder(concurrent_behavior);

    signal x_tb, y_tb: std_logic;
    signal sum_tb, carry_tb: std_logic;
```

159

begin

UUT: half_adder port map (x => x_tb, y => y_tb, sum => sum_tb,
 carry => carry_tb);

-- define a process to apply input stimulus and verify outputs.

tb: process is

constant PERIOD: time := 20 ns;

begin -- apply every possible input combination

x_tb <= '0'; -- apply input combination 00 and check outputs

y_tb <= '0';


wait for PERIOD; -- Wait for outputs to be available after
 -- applying this stimulus

assert ((sum_tb = '0') and (carry_tb = '0'))

report "Test failed for input combination 00" severity ERROR;

assert (布 表达式)

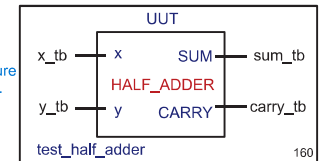如果布尔表达式为false，执行report
severity 有四种严重级别: note, warning, error, failure
error和failure会立即停止，note和warning不会停止



160

```
x_tb <= '1'; -- apply input combination 10 and check outputs
y_tb <= '0';
wait for PERIOD;
assert ((sum_tb = '1') and (carry_tb = '0'))
report "Test failed for input combination 01" severity ERROR;
x_tb <= '0';
y_tb <= '1';
wait for PERIOD;
assert ((sum_tb = '1') and (carry_tb = '0'))
report "Test failed for input combination 10" severity ERROR;
x_tb <= '1';
y_tb <= '1';
wait for PERIOD;
assert ((sum_tb = '0') and (carry_tb = '1'))
report "Test failed for input combination 11" severity ERROR;
wait; -- indefinitely suspend process
end process;
end architecture behavior;
```

161

Wait statement (Sequential statement)

- explicitly specify the conditions under which a process may resume execution after being suspended.
- Basic forms of the wait statement
 - wait for time-expression ; wait for 20 ns;
 - wait on signal ; wait on clk, reset, status;
 - wait until condition ; wait until A > B;
 - wait ;

最好不要在synthesis和implementation中使用

162

Assert statement

- VHDL's assert statement provides a quick and easy way to check expected values and display messages from your test bench. An assert statement has the following general format:

assert condition_expression -- a Boolean value

report text_string -- the text is displayed if the Boolean
-- value is false


severity severity_level; -- severity level can be one of
-- predefined levels: NOTE,
-- WARNING, ERROR, or FAILURE.

163

5.3.4 Test benches that compute stimulus and expected results

```
tb: process is -- define a process to apply input stimulus and verify outputs.
constant PERIOD: time := 20 ns;
constant n : integer := 2;
begin -- apply every possible input combination
for i in 0 to 2**n - 1 loop
(x_tb, y_tb) <= to_unsigned(i, n);
wait for PERIOD;
assert ((sum_tb = (x_tb xor y_tb)) and (carry_tb = (x_tb and y_tb)))
report "Test failed" severity ERROR;
end loop;
wait;
end process;
```

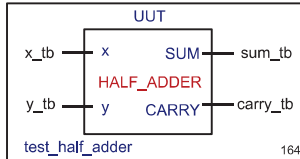example:
i = 2, n = 2
to_unsigned(i, n) = 10
x_tb = 1, y_tb = 0



164

Loop statement

- A loop statement is used to iterate through a set of sequential statement.
- General form of a loop statement
[loop-label] iteration-scheme loop
sequential-statements
end loop [loop-label]

- Three types of iteration schemes:

(A) for i in 0 to 2**n - 1 loop
(x_tb, y_tb) <= to_unsigned(i, n);
wait for PERIOD;
...
end loop;

range
loop identifier

- The object *i* is implicitly declared within the for loop to belong to the integer type whose value are in the range 0 to $2^n - 1$.
- The loop identifier cannot be assigned any value inside the for loop

```
type COLOR is (RED, GREEN, BLUE);
...
for PAPER in COLOR loop
-- PAPER will take all value in type COLOR
-- from RED to BLUE.
end loop;
```

166

(B) J := 0; SUM := 10;
WHILE_LOOP: while J < 20 loop
SUM := SUM * 2;
J := J + 3;
end loop WHILE_LOOP;

不能用于电路设计
只在testbench中使用

(C) J := 0; SUM := 1;
L2: loop
J := J + 21;
SUM := SUM * 10;
exit when SUM > 100;
end loop L2;

Exit statement

- The exit statement can be used only inside a loop.
- It causes execution to jump out of the innermost loop or the loop whose label is specified.
- General form of an exit statement
exit [loop-label] [when condition]

```
SUM := 1;
L2: loop
J := 0;
L3: loop
J := J + 21;
exit when J > 40;
SUM := SUM * 10;
if SUM > 100 then exit L2;
end if;
end loop L3;
end loop L2;
```

```
loop
wait on A, B;
exit when A=B;
end loop;
```

168

Next statement

- The next statement can be used only inside a loop.
- It results in skipping the remaining statements in the current iteration; execution resumes with the first statement in the next iteration of this loop, if one exists.
- General form of a next statement
next [loop-label] [when condition]

```
for J in 10 downto 5 loop
if SUM < TOTAL_SUM then
SUM := SUM + 2;
elsif SUM = TOTAL_SUM then
next;
else null;
end if;
K := K + 1;
end loop;
```

169

signed and unsigned data type

- In VHDL and the std_logic_1164 package, the arithmetic operations are defined only over the integer data type.
signal a, b, sum: integer;
...
sum <= a+b;
- Data types signed and unsigned are defined in IEEE numeric_std package. Both data types are an array of element with the std_logic data type. They are interpreted as a signed number or unsigned number.
- std_logic_vector, signed, and unsigned are all defined as an array of elements with the std_logic data type, but they are three independent data types.

170

- To use the signed and unsigned data type, we must include:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

signal x, y: signed(15 downto 0);
```

to_unsigned(i, n)

- convert the integer *i* value to an unsigned vector of length *n*
- (x_tb, y_tb) <= to_unsigned(i, n);
 - the unsigned vector value returned in this example is assigned to an aggregate made up of the scalar input signals.
 - each of these scalar is type std_logic.
 - each element of an unsigned vector is also type std_logic.

171

Table: Overloaded operators in the IEEE numeric_std package

Operator	Description	Data type of a	Data type of b	Data type of result
abs a	absolute value	signed		
-a	negation	signed		
a * b, a / b, a mod b, a rem b, a + b, a - b	arithmetic operation	unsigned, natural signed, integer	unsigned, nature unsigned signed, integer signed	unsigned unsigned signed signed
a = b, a /= b, a < b, a <= b, a > b, a >= b	relational operation	unsigned, natural signed, integer	unsigned, nature unsigned signed, integer signed	boolean boolean boolean boolean

```
signal a, b, c, d, e: unsigned (7 downto 0);
...
a <= b + c;    d <= b + 1;    e <= (5 + a + b) - c;
```

"011" >= "1000"; -- return FALSE if type is std_logic_vector or unsigned
-- return TRUE if type is signed

172

Table: Functions in the IEEE numeric_std package

Function	description	Data type of a	Data type of b	Data type of result
shift_left(a, b) shif_right(a, b) rotate_left(a, b) rotate_right(a, b)	shift left shift right rotate left rotate right	unsigned, signed	natural	same as a
resize(a,b)	resize array	unsigned, signed	natural	same as a
std_match(a,b)	compare '-'	unsigned, signed, std_logic_vector, std_logic	same as a	boolean
to_integer(a)		unsigned, signed		integer
to_unsigned(a,b)	data type conversion	natural	natural	unsigned
to_signed(a,b)		integer	natural	signed

173

5.3.5 Post-synthesis and timing verifications for combinational designs

- Post-synthesis verification
 - to verify that the synthesizer has successfully translated a design description to gate-level logic.
 - the same test bench used for functional verification could be used.
- Timing verification
 - to verify gate delays and propagation delays of signal paths of the logic mapped to the target programmable logic device.
 - If the delay between application of each stimulus and verification of the corresponding UUT outputs was appropriately chosen in the original functional verification test bench, the same test bench could be used for timing verification.

176

- std_logic_vector, unsigned and signed are known as *closely related data types*. Conversion between these types is done by a procedure known as *type casting*.

Table: Type conversion of numeric data types

Data type of a	To data type	Conversion function/type casting
unsigned, signed	std_logic_vector	std_logic_vector(a)
signed, std_logic_vector	unsigned	unsigned(a)
unsigned, std_logic_vector	signed	signed(a)
unsigned, signed	integer	to_integer(a)
natural	unsigned	to_unsigned(a, size)
integer	signed	to_signed(a, size)

signal u1, u2: unsigned (7 downto 0);
signal v1, v2: std_logic_vector(7 downto 0);
...
u1 <= unsigned(v1);
v2 <= std_logic_vector(u2);

174

```
library ieee;  
use ieee.std_logic_1164.all  
use ieee.numeric_std.all  
...  
signal s1, s2, s3, s4, s5, s6: std_logic_vector (3 downto 0);  
signal u1, u2, u3, u4, u5, u6: unsigned(3 downto 0);  
signal sg: signed(3 downto 0);  
...  
u3 <= u2 + u1; -- ok  
u4 <= u2 + 1; -- ok  
u5 <= sg; -- not ok  
u6 <= 5; -- not ok  
u5 <= unsigned(sg); -- ok  
u6 <= to_unsigned(5,4); -- ok  
u7 <= sg + u1; -- not ok  
u7 <= unsigned(sg) + u1; -- ok  
s3 <= u3; -- not ok  
s4 <= 5; -- not ok  
s3 <= std_logic_vector(u3); -- ok  
s4 <= std_logic_vector(to_unsigned(5,4));  
-- ok  
s5 <= s2 + s1; -- not ok  
s6 <= s2 + 1; -- not ok  
s5 <= std_logic_vector(unsigned(s2) +  
-- unsigned(s1)); -- ok  
s6 <= std_logic_vector(unsigned(s2) +  
-- 1); -- ok
```

175